
Transmission Line Filters Beyond Stubs and Traps

Steve Stearns, K6OIK

Technical Fellow
Northrop Grumman
Electromagnetic Systems Laboratory
San Jose, CA
k6oik@arri.net
stearns@ieee.org

ARRL Pacificon Presentations by K6OIK





Archived at
<http://www.fars.k6ya.org>

- 1999 Mysteries of the Smith Chart
- 2000 Jam-Resistant Repeater Technology: Signal Separation, Identification, Routing, Control, and Automatic Logging
- 2001 Mysteries of the Smith Chart ✓
- 2002 How-to-Make Better RFI Filters Using Stubs
- 2003 Twin-Lead J-Pole Design
- 2004 Antenna Impedance Models – Old and New ✓
- 2005 Novel and Strange Ideas in Antennas and Impedance Matching
- 2006 Novel and Strange Ideas in Antennas and Impedance Matching 2 ✓
- 2007 New Results on Antenna Impedance Models and Matching ✓
- 2008 Antenna Modeling for Radio Amateurs ✓
- 2009 (convention held in Reno)
- 2010 Facts About SWR, Reflected Power, and Power Transfer on Real Transmission Lines with Loss
- 2011 Conjugate Match Myths ✓
- 2012 Transmission Line Filters Beyond Stubs and Traps ✓

Topics

- **Antenna books**
- **Software for modeling antennas and circuits**
- **What motivated this talk**
 - General Class License question G7C06
 - K6OIK 2-meter pager rejection filter presented in 2002
 - RFI mitigation for multi-station operations at Field Day
- **Transmission line and stub properties**
- **Lossless, reflection filters**
 - Simple trap
 - Filters having multiple pass and rejection frequencies
 - Variety of useful RFI filters for Amateur operations
 - Sub-band filters for Field Day
- **Sub-harmonic stub filters**
- **Reflectionless stub filters**
- **Commensurate stub filters**
- **Re-entrant filters**
- **References**

Favorite Antenna Books

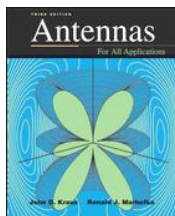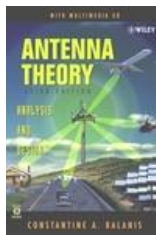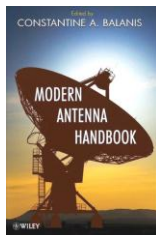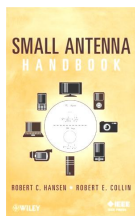





■ Books for antenna engineers and students

- R.C. Hansen and R.E. Collin, *Small Antenna Handbook*, Wiley, 2011, ISBN 0470890835
- *Modern Antenna Handbook*, C.A. Balanis editor, Wiley, 2008, ISBN 0470036346
- *Antenna Engineering Handbook*, 4th ed., J.L. Volakis editor, McGraw-Hill, 2007, ISBN 0071475745. First published in 1961, Henry Jasik editor
- C.A. Balanis, *Antenna Theory*, 3rd ed., Wiley, 2005, ISBN 047166782X. First published in 1982 by Harper & Row
- J.D. Kraus and R.J. Marhefka, *Antennas*, 3rd ed., McGraw-Hill, 2001, ISBN 0072321032. First published in 1950
- S.J. Orfanidis, *Electromagnetic Waves and Antennas*, draft textbook online at <http://www.ece.rutgers.edu/~orfanidi/ewa/>
- E.A. Laport, *Radio Antenna Engineering*, McGraw-Hill, 1952 <http://snulbug.mtview.ca.us/books/RadioAntennaEngineering>
- G.V. Ayzenberg, *Shortwave Antennas*, 1962, transl. from Russian, DTIC AD0706545. <http://www.dtic.mil/dtic/tr/fulltext/u2/706545.pdf>

■ Antenna research papers

- IEEE AP-S Digital Archive, 2001-2009 (1 DVD), JD0307
- IEEE AP-S Digital Archive, 2001-2006 (1 DVD), JD0304
- IEEE AP-S Digital Archive, 2001-2003 (1 DVD), JD0301
- IEEE AP-S Digital Archive, 1952-2000 (2 DVDs), JD0351


Favorite Antenna Books continued

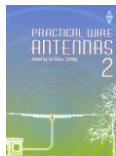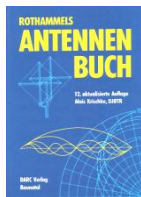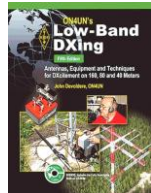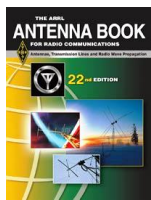


Books for Radio Amateurs

- *ARRL Antenna Book*, 22nd ed., H.W. Silver (N0AX) editor, American Radio Relay League, 2011, ISBN 087259694X
- J. Devoldere (ON4UN), *ON4UN's Low-Band Dxing*, 5th ed., American Radio Relay League, 2011, ISBN 087259856X
- *Rothammel's Antennenbuch*, 12th ed., A. Kruschke (DJ0TR) editor, DARC Verlag, 2006, ISBN 388692033X
- *Practical Wire Antennas 2*, I. Poole (G3YWX) editor, Radio Society of Great Britain, 2005, ISBN 1905086040
- J. Sevick (W2FMI), *The Short Vertical Antenna and Ground Radial*, CQ Communications, 2003, ISBN 0943016223
- L. Moxon (G6XN), *HF Antennas for All Locations*, 2nd ed., Radio Society of Great Britain, 1983, ISBN 1872309151

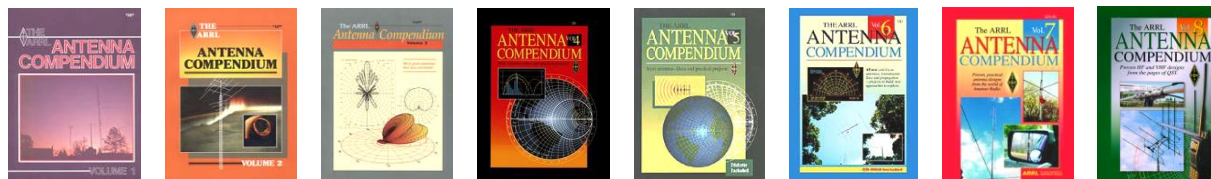
ARRL Antenna Compendium series – Volumes 1 through 8



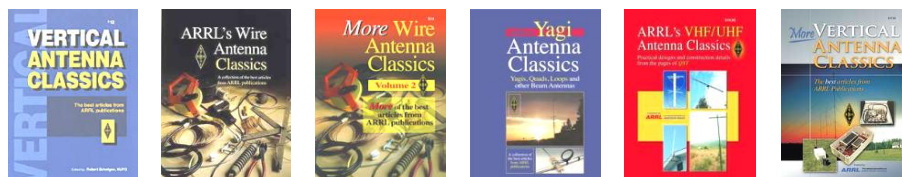ARRL Antenna Classics series – six titles





New Antenna Books of Interest

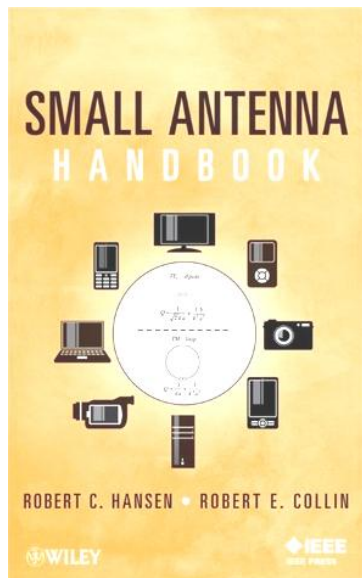


R.C. Hansen and R.E. Collin, *Small Antenna Handbook*, Wiley, 2011, ISBN 0470890835

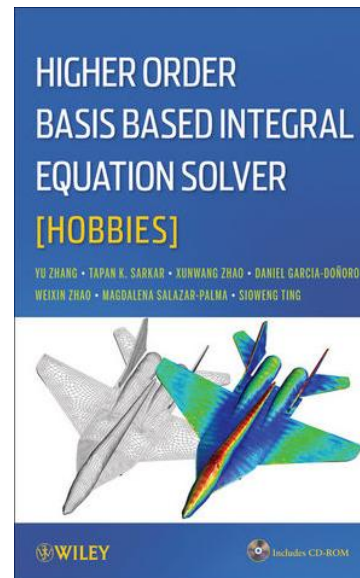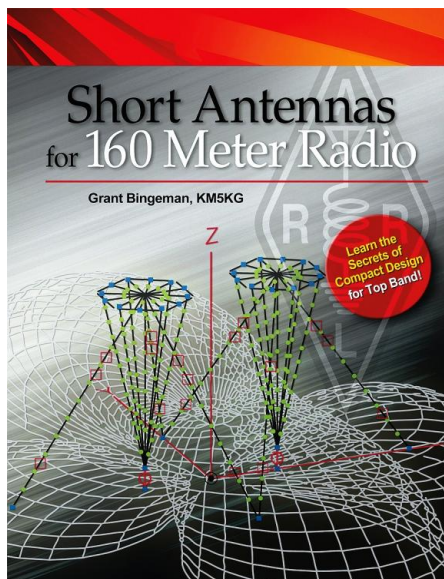G. Bingeman, KM5KG, *Short Antennas for 160 Meter Radio*, ARRL, 2012, ISBN 9780872595798



Y. Zhang et al., *Higher Order Basis Based Integral Equation Solver [HOBBIES]*, Wiley, 2012, ISBN 1118140656

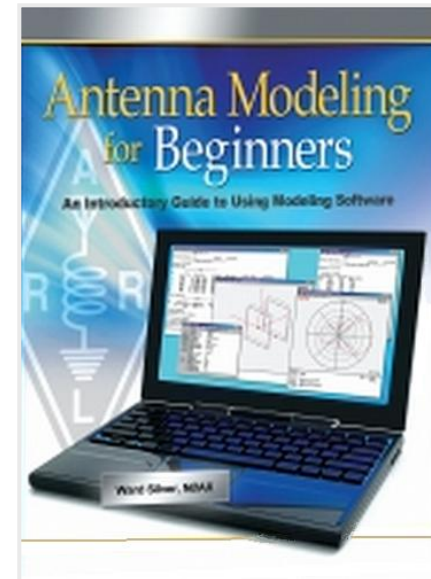H.W. Silver, N0AX, *Antenna Modeling for Beginners*, ARRL, 2012, ISBN 9780872593961



Software

Antenna Modeling Programs for Radio Amateurs

- **EZNEC** <http://www.eznec.com>
 - EZNEC v.5 demo program Free
 - EZNEC-ARRL v.3 & v.4 \$50 (on ARRL Antenna Book CD-ROM)
 - EZNEC v.5 \$90
 - EZNEC+ v.5 \$140
 - EZNEC Pro/2 v.5 \$500
 - EZNEC Pro/4 v.5 \$650 (sold only to NEC-4 licensees)
- **4nec2** <http://home.ict.nl/~arivoors/>
 - Free, 11,000 segments, two optimizers
- **NEC-4** <https://ipo.llnl.gov/data/assets/docs/nec.pdf>
 - Noncommercial user license \$300
- **FEKO Lite** <http://www.feko.info>
 - Free LITE version
- **WIPL-D Lite** <http://www.wipl-d.com>
 - Free Demo version, more capable Lite version from Artech House \$450
- **HOBBIES** <http://em-hobbies.com>
 - Similar to WIPL-D Lite but more capability, \$162 to \$210


General RF Circuit Design, Analysis, and Optimization

■ Software for Radio Amateurs

- *Quite Universal Circuit Simulator* (QUCS) 0.0.16, 2011, \$0 (free)
 - Download from <http://qucs.sourceforge.net>
- *Ansoft Serenade SV 8.5* (student version), Ansoft, 2000, \$0 (free). No longer available.
- *ARRL Radio Designer 1.5*, ARRL, 1995. No longer available.

■ Professional electronic design automation (EDA) software

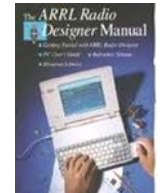- *Advanced Design System* (ADS), Agilent
- *Microwave Office* (MWO), Applied Wave Research
- *Designer*, ANSYS




Software for Smith Charting and Network Design

■ Match network analysis with Smith Chart display


- *SimSmith* by Ward Harriman AE6TY, 2011, \$0 (free)
 - Download from http://ae6ty.com/Smith_Charts.html
- *Smith* by Fritz Dellsperger HB9AJY, 2010, \$0 (free)
 - Download from <http://fritz.dellsperger.net>
- *QuickSmith* by Nathan Iyer KJ6FOJ, 2009, \$0 (free)
 - Download from <http://www.nathaniyer.com/qsdw.htm>
- *linSmith* by James Coppens ON6JC/LW3HAZ, \$0 (free)
 - Download from <http://jcoppens.com/soft/linsmith/index.en.php>
- *SuperSmith* by J. Bromley K7JEB and J. Tonne W4ENE, \$0 (free)
 - Download from <http://www.tonnesoftware.com/supersmith.html>
- *XLZIZL* by Dan Maguire AC6LA, 2005. No longer available.
- *WinSMITH* 2.0, Noble Publishing, 1995. No longer available.
- *MicroSmith* 2.3, ARRL, 1992. No longer available.

Smith Chart Programs for Ladder Network Design


Smith 3.10

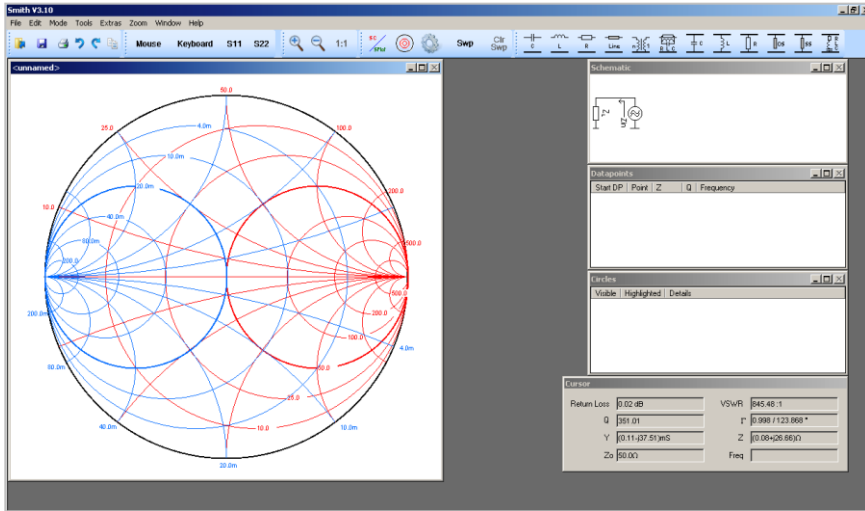


SimSmith 4.4

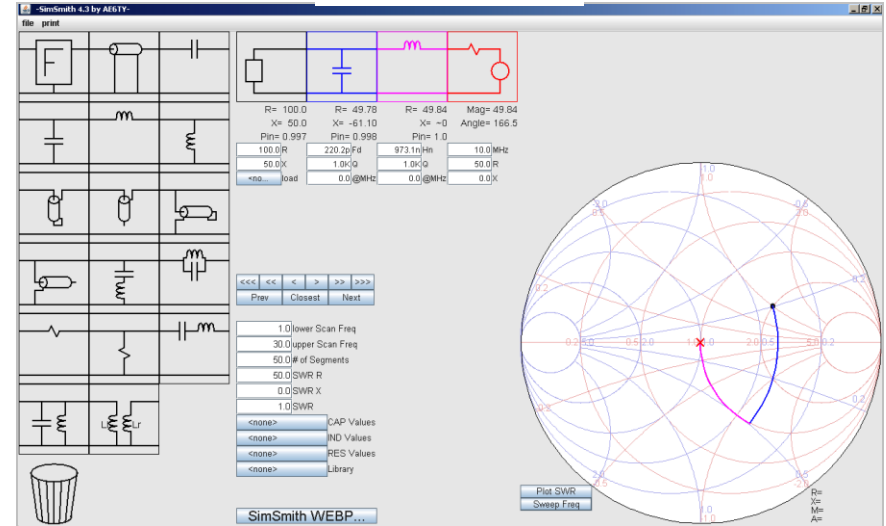

QuickSmith 4.5

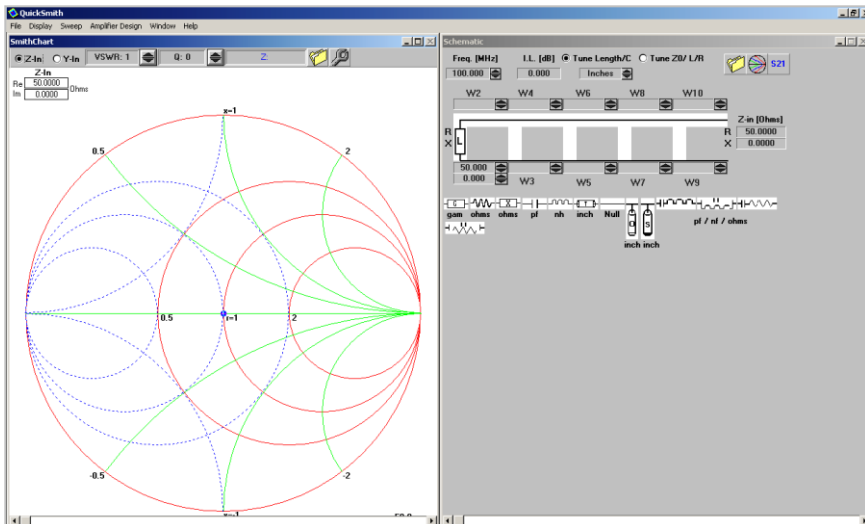

winSMITH 2.0

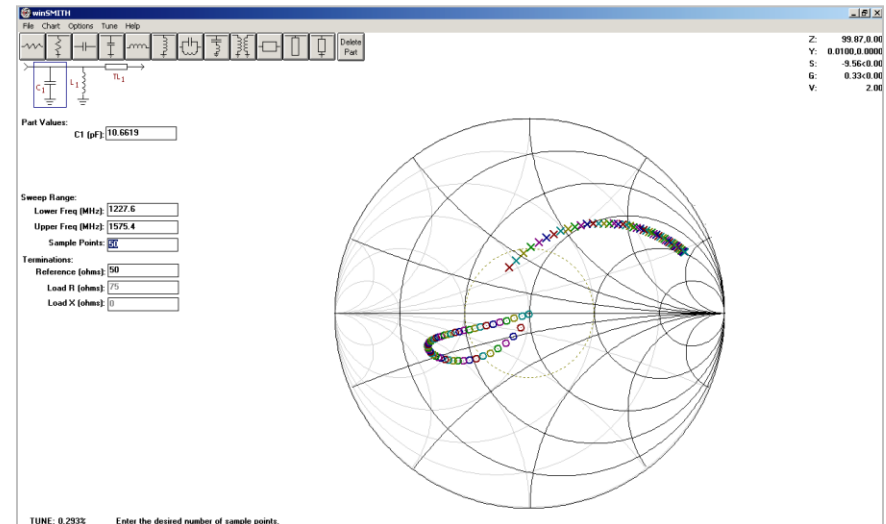

Questions for 2012

- **Given:** Several frequencies, rationally related and relatively prime, divided into “pass” and “stop” sets
- **Goal:** A filter that passes the pass frequencies and rejects the stop frequencies
- For the following questions, assume the filter is made using stubs made from lossless line
- **Q1:** What is the smallest number of stubs needed?
- **Q2:** What is the smallest number of distinct characteristic impedances needed?
- **Q3:** What is the smallest input SWR that can be achieved across all frequencies?
- **Q4:** What is the smallest total line length needed?

Answers

- **Q1: What is the smallest number of stubs needed?**
 - Answer is one
 - ⇒ sub-harmonic stub filter
- **Q2: What is the smallest number of distinct characteristic impedances needed?**
 - Answer is one
 - ⇒ sub-harmonic stub filter
 - ⇒ non-commensurate stub filter
- **Q3: What is the smallest input SWR that can be achieved across all frequencies?**
 - Answer is one (1:1)
 - ⇒ reflectionless complementary stub filter
- **Q4: What is the smallest total line length needed?**
 - Answer is zero, or more precisely, arbitrarily small
 - ⇒ commensurate stub filter


Why This Talk?

Question G7C06


- **What should be the impedance of a low-pass filter as compared to the impedance of the transmission line into which it is inserted?**
 - A. Substantially higher
 - **B. About the same**
 - C. Substantially lower
 - D. Twice the transmission line impedance

For reflection filters, the answer is true only in the passband
For dissipation filters the answer can be true in general.


A Band-Pass Reflection Filter

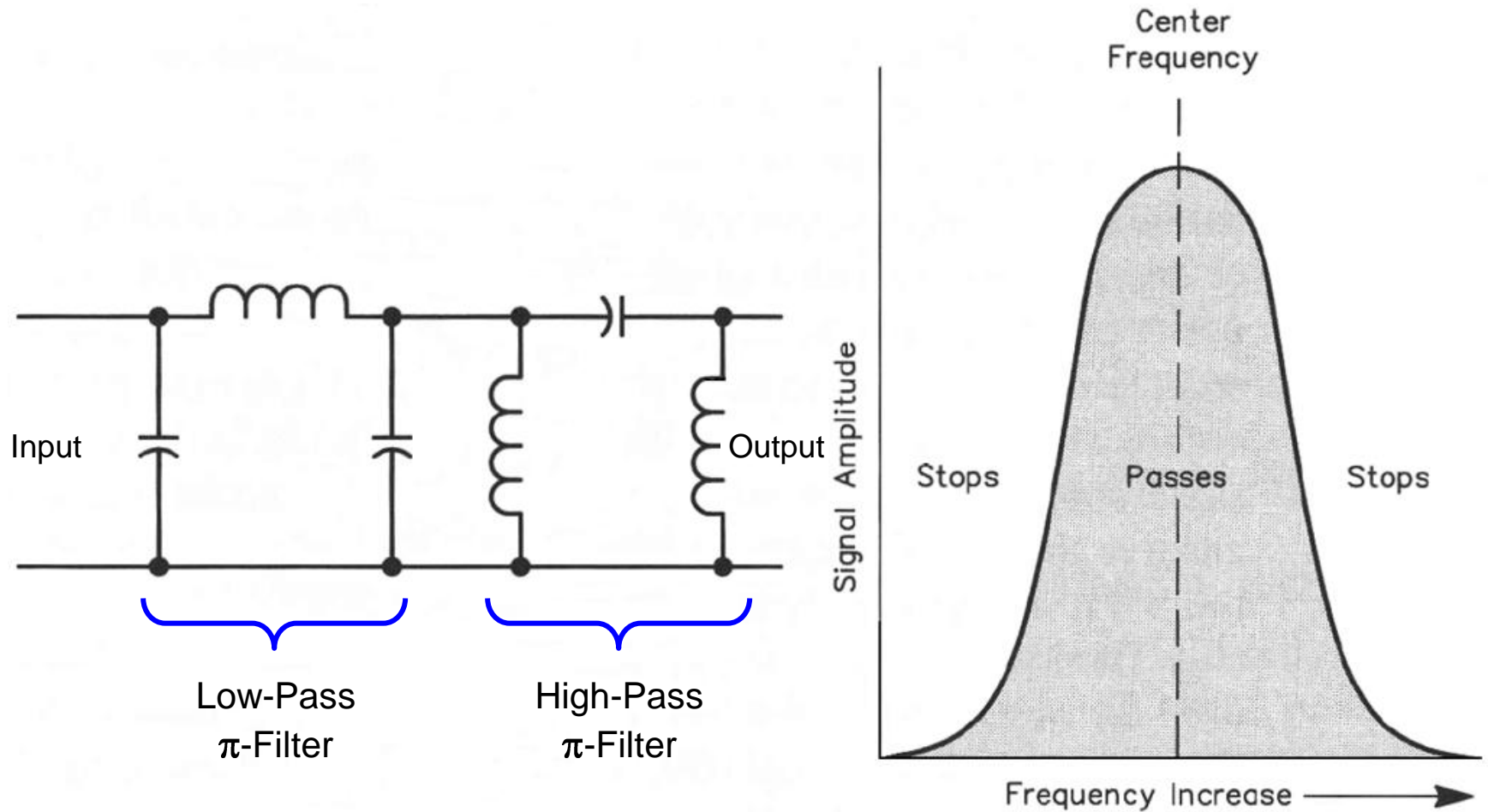


Smith Chart

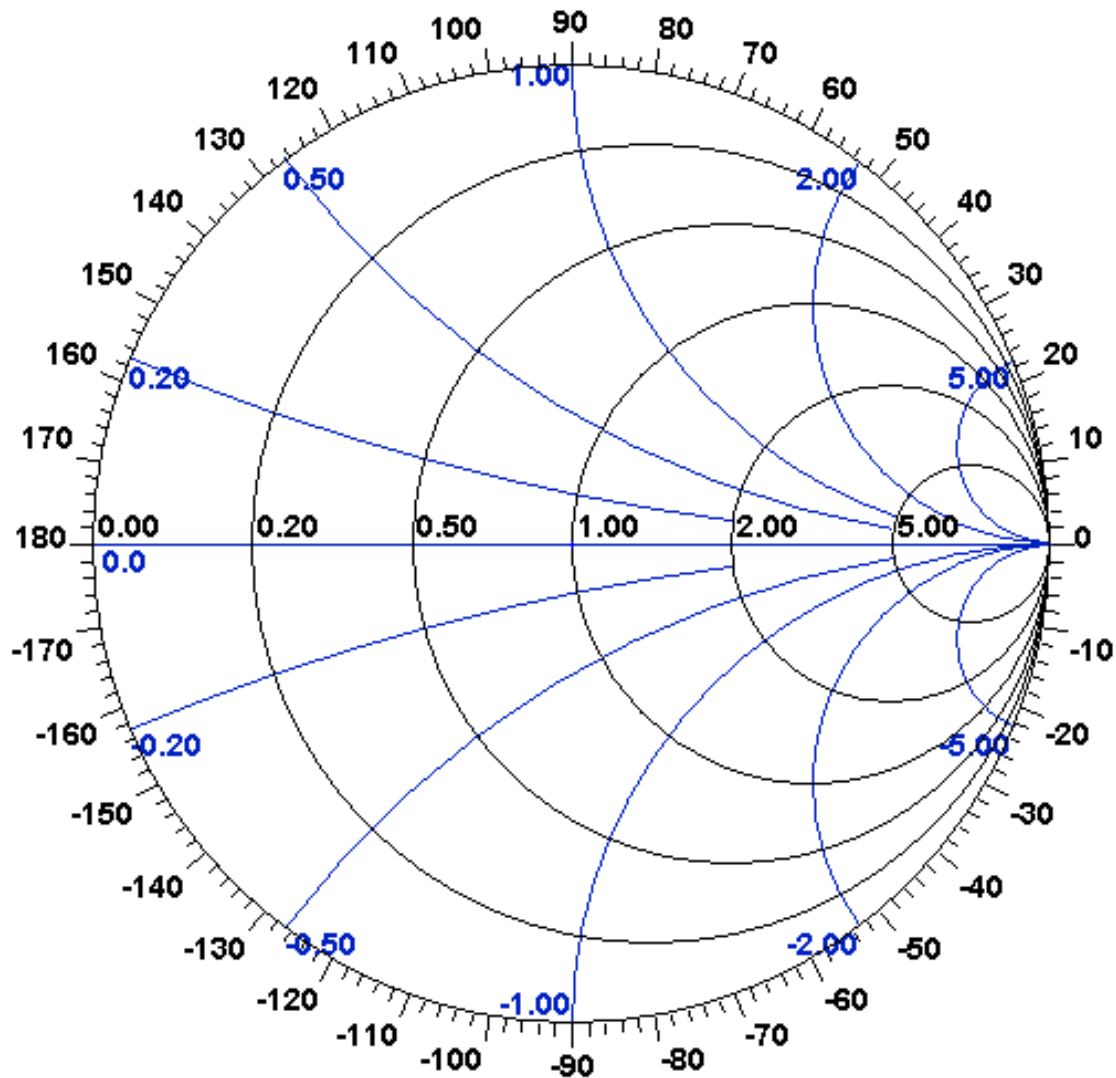


Smith Chart + Data

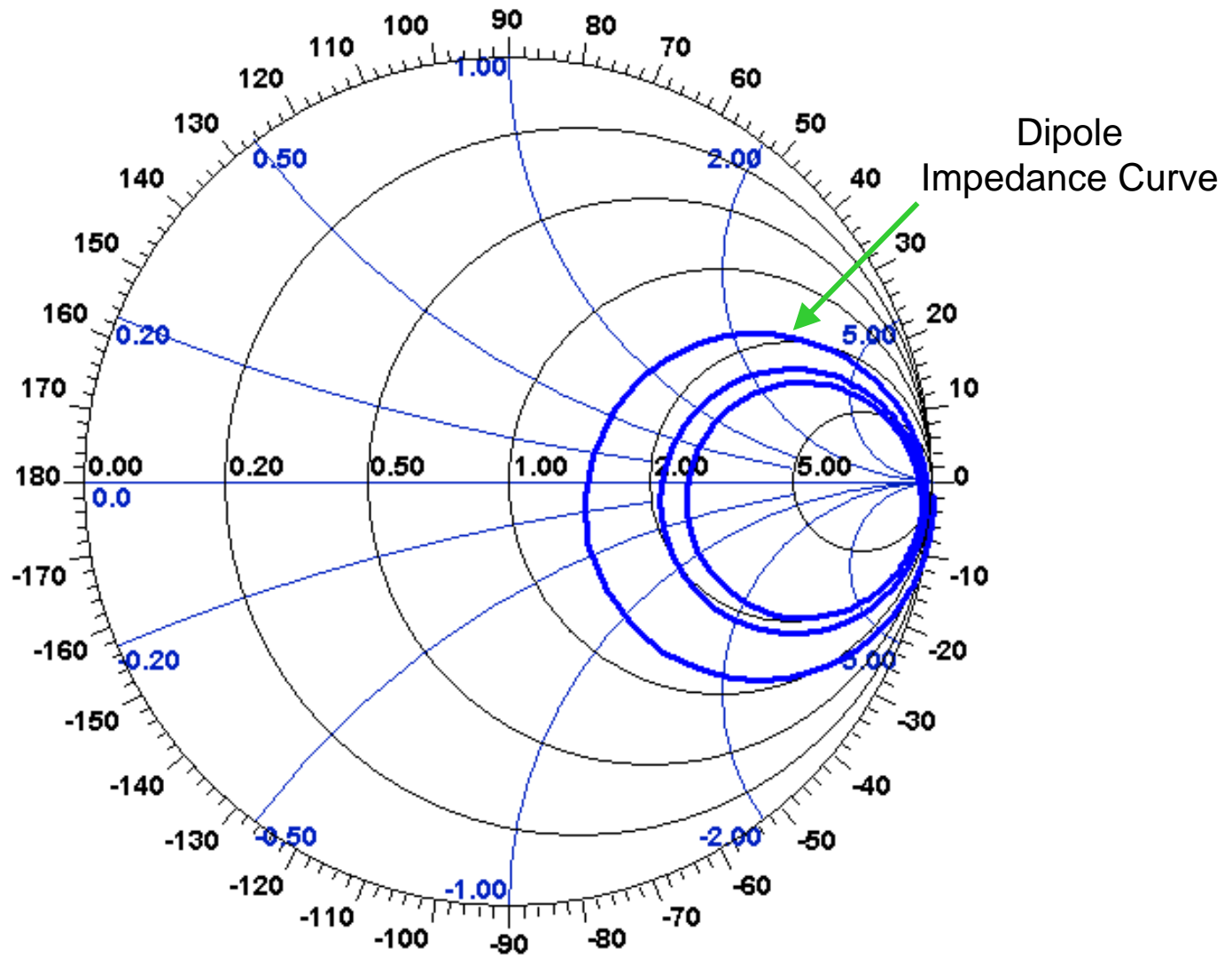

Smith Chart + Data + Match Goal

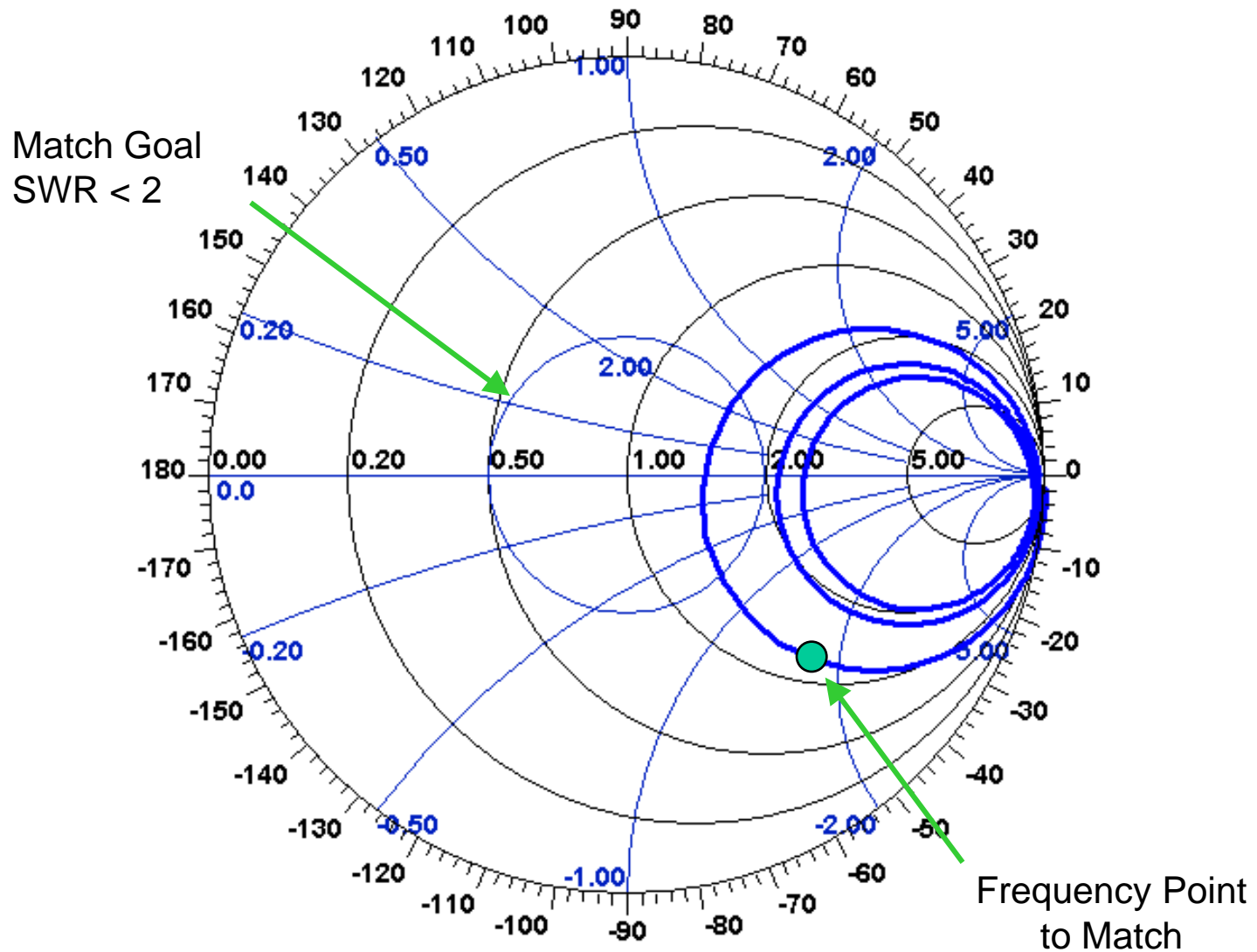

Smith Chart + Data + Filter Goals

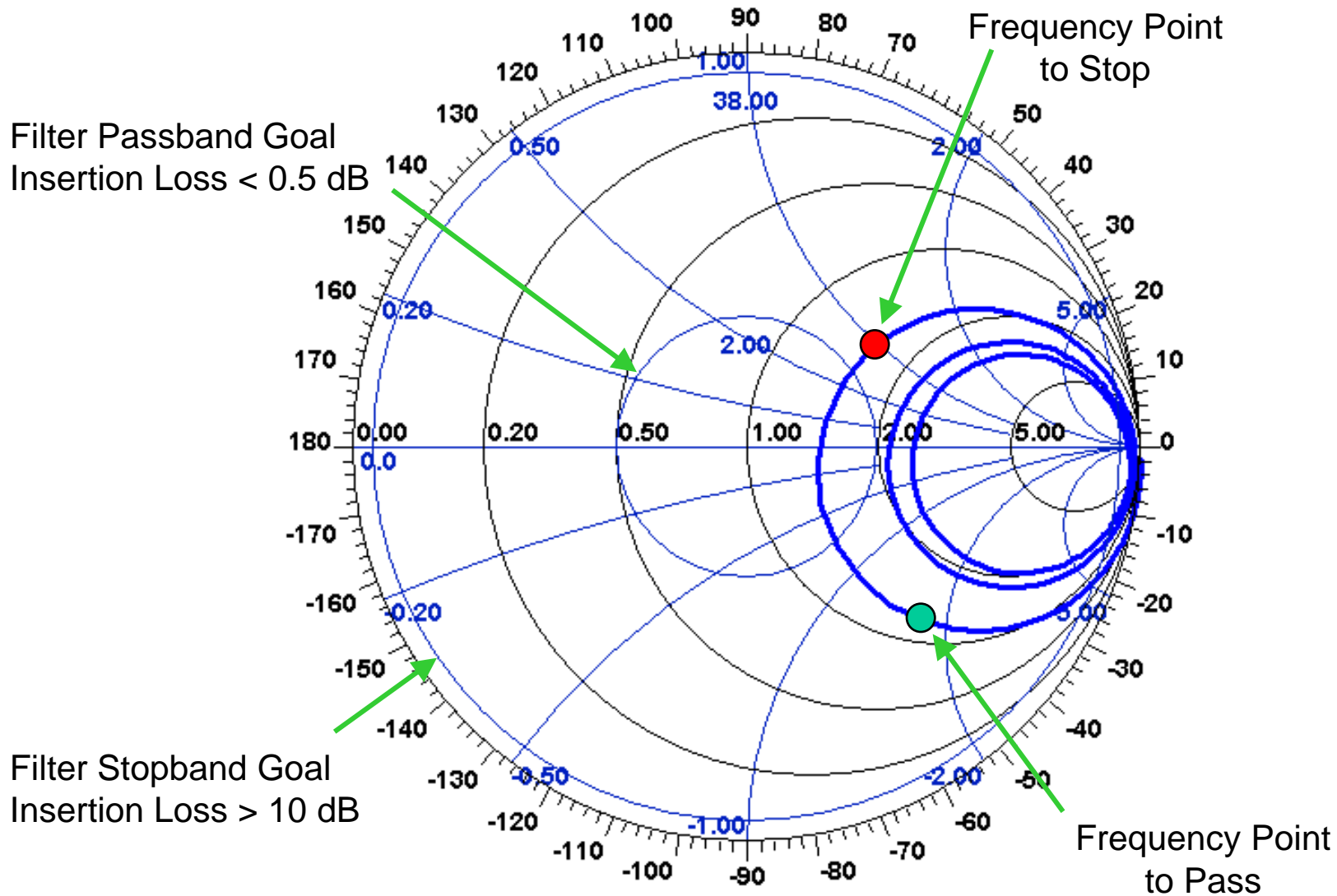

Some Transmission Line Properties

Characteristic Impedance

- **Transmission line characteristic impedance is a useful design variable**
- **For high-frequency applications (UHF), microstrip and stripline can be fabricated for a continuous range of impedances depending on trace width**
- **Coax can be obtained with discrete values of characteristic impedance from 12.5 to 190 ohms**
- **Additional values of characteristic impedance can be obtained by series or parallel combinations**
 - Lines can be series-connected to sum their characteristic impedances
 - Lines can be parallel-connected to sum their characteristic admittances

Non-50/75 Ohm Coaxial Transmission Lines

Impedance	Types
12.5 Ω	RG192, RG193, RG194
25 Ω	RG73, RG191, RG230, RG328 M17/124
35/37 Ω	RG83, RG100, RG264
93/95 Ω	RG7, RG22, RG43, RG57, RG62, RG71, RG111, RG130, RG131, RG133, RG180, RG294, RG317 M17/15, M17/30, M17/56, M17/90, M17/95, M17/100, M17/137, M17/139, M17/177, M17/178, M17/182, M17/185, M17/195,
100 Ω	RG285, RG287, RG383
125 Ω	RG23, RG24, RG63, RG79, RG89, RG160 M17/16, M17/31, M17/218
140 Ω	RG102
150 Ω	RG72, RG125
185 Ω	RG114 M17/47, M17/208
190 Ω	RG146

Small Diameter Coax Types

0.18 to 0.25 inch O.D. for BNC Connectors

Z_0	Line Types	v.f.	150 MHz dB/100'	150 MHz dB/ λ
35 Ω	RG100			
50 Ω	ETS1-50T	0.82	2.20	0.118
	LMR 300	0.85	2.40	0.134
	LMR 240	0.84	3.01	0.166
	9258-RG8/X	0.82	3.85	0.207
	LMR 200	0.83	3.98	0.217
	LMR 195	0.80	4.44	0.233
	9210-RG58/U	0.66	4.67	0.202
	9211-RG58A/U	0.75	4.92	0.242
	M17/28-RG58	0.66	5.63	0.243
93 Ω	6539Y8-RG62/U	0.84	3.30	0.182
	9269-RG62A/U	0.84	3.30	0.182
	M17/30-RG62	0.81	3.50	0.186
	M17/90-RG71	0.81	3.50	0.186
	M17/97-RG210	0.85	3.50	0.195
	M17/185	0.81	3.50	0.186
	M17/195	0.85	3.50	0.195
	8255-RG62B/U	0.84	3.60	0.198
95 Ω	M17/177	0.695	7.71	0.351

Larger Diameter Coax Types

0.40 to 0.42 inch O.D. for UHF Connectors

Z_0	Line Types	v.f.	150 MHz dB/100'	150 MHz dB/ λ
35 Ω	RG83	0.66	3.46	0.150
50 Ω	LDF2-50	0.88	1.28	0.074
	LMR 400	0.85	1.54	0.086
	9913-RG8/U	0.84	1.57	0.087
	9913F7-RG8/U	0.83	1.78	0.097
	9914-RG8	0.82	1.78	0.096
	M17/74-RG213	0.66	2.52	0.109
95 Ω	M17/100-RG133	0.66	2.74	0.118
	M17/15-RG22	0.66	2.81	0.122
	M17/182	0.66	2.81	0.122
125 Ω	9857-RG63/U	0.84	1.92	0.106
	M17/31-RG63	0.86	2.35	0.133
	M17/218	0.86	2.35	0.133
185 Ω	M17/47-RG114	0.85	4.29	0.239
	M17/208	0.83	4.29	0.233

Transmission Lines are 2-Port Devices

- **Transmission, Chain, or ABCD matrix**

$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh \gamma l & Z_0 \sinh \gamma l \\ \frac{1}{Z_0} \sinh \gamma l & \cosh \gamma l \end{bmatrix}$$

- **Open-circuit impedance matrix Z**


$$Z = \begin{bmatrix} \frac{A}{C} & \frac{1}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix} = Z_0 \begin{bmatrix} \coth \gamma l & \frac{1}{\sinh \gamma l} \\ \frac{1}{\sinh \gamma l} & \coth \gamma l \end{bmatrix}$$

- **Short-circuit admittance matrix Y**

$$Y = \begin{bmatrix} \frac{D}{B} & \frac{-1}{B} \\ \frac{-1}{B} & \frac{A}{B} \end{bmatrix} = Y_0 \begin{bmatrix} \coth \gamma l & \frac{-1}{\sinh \gamma l} \\ \frac{-1}{\sinh \gamma l} & \coth \gamma l \end{bmatrix}$$

2-Port Series Connection Sums Line Impedances
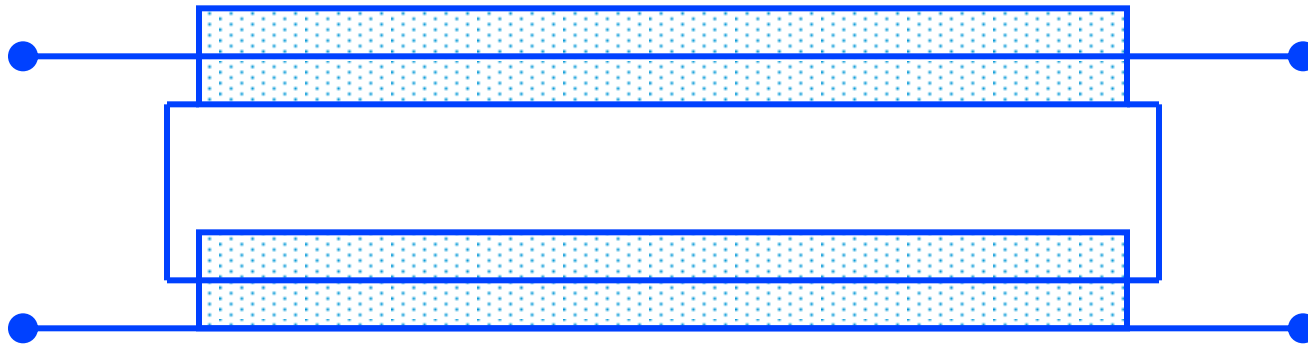
$$Z'_0 = Z_{01} + Z_{02} \quad \text{if} \quad \beta_1 l_1 = \beta_2 l_2$$



- **Make line electrical lengths equal, $\beta_1 l_1 = \beta_2 l_2$**
- **Unbalanced version shown**
 - Keep lines spaced several diameters apart
 - Build as a common-mode choke
 - Put ferrite beads along both shields or wind on a toroid
- **Balanced version is made by joining shields instead**
 - OK if shields touch

Proof

- When 2-ports are connected so ports are in series, their Z matrices sum


$$\begin{aligned} Z &= Z_{01} \begin{bmatrix} \coth \gamma_1 l_1 & \frac{1}{\sinh \gamma_1 l_1} \\ \frac{1}{\sinh \gamma_1 l_1} & \coth \gamma_1 l_1 \end{bmatrix} + Z_{02} \begin{bmatrix} \coth \gamma_2 l_2 & \frac{1}{\sinh \gamma_2 l_2} \\ \frac{1}{\sinh \gamma_2 l_2} & \coth \gamma_2 l_2 \end{bmatrix} \\ &= (Z_{01} + Z_{02}) \begin{bmatrix} \coth \gamma l & \frac{1}{\sinh \gamma l} \\ \frac{1}{\sinh \gamma l} & \coth \gamma l \end{bmatrix} \end{aligned}$$

- Characteristic impedances of series connected lines sum if $\beta_1 l_1 = \beta_2 l_2$

$$Z'_0 = Z_{01} + Z_{02}$$

2-Port Parallel Connection Sums Line Admittances
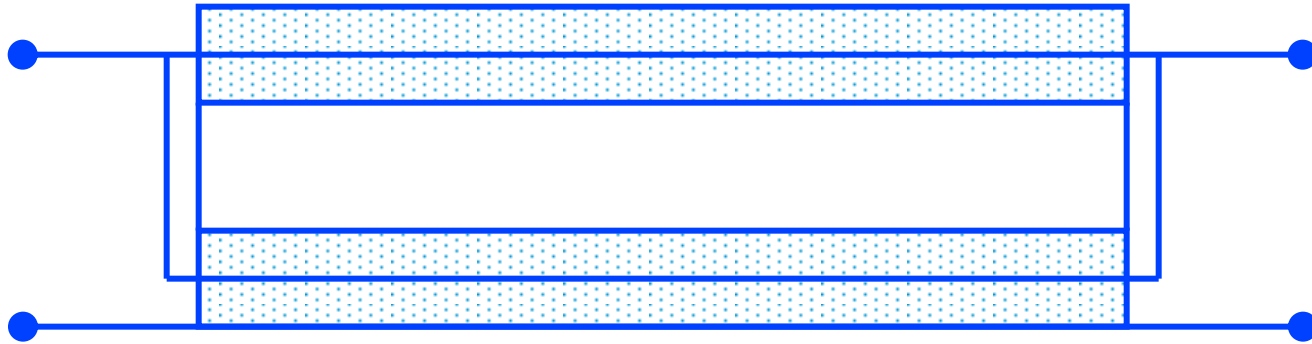
$$Z'_0 = \frac{1}{\frac{1}{Z_{01}} + \frac{1}{Z_{02}}} \quad \text{if} \quad \beta_1 l_1 = \beta_2 l_2$$



- **Make line electrical lengths equal, $\beta_1 l_1 = \beta_2 l_2$**
- **Unbalanced version shown**
 - OK if shields touch
- **Balanced version is made by joining each line's center to other line's shield instead**
 - Keep lines several diameters apart

Proof

- When 2-ports are connected so ports are in parallel, their Y matrices sum

$$Y = Y_{01} \begin{bmatrix} \coth \gamma_1 l_1 & \frac{-1}{\sinh \gamma_1 l_1} \\ \frac{-1}{\sinh \gamma_1 l_1} & \coth \gamma_1 l_1 \end{bmatrix} + Y_{02} \begin{bmatrix} \coth \gamma_2 l_2 & \frac{-1}{\sinh \gamma_2 l_2} \\ \frac{-1}{\sinh \gamma_2 l_2} & \coth \gamma_2 l_2 \end{bmatrix}$$
$$= (Y_{01} + Y_{02}) \begin{bmatrix} \coth \gamma l & \frac{-1}{\sinh \gamma l} \\ \frac{-1}{\sinh \gamma l} & \coth \gamma l \end{bmatrix}$$

- Characteristic admittances of parallel connected lines sum if $\beta_1 l_1 = \beta_2 l_2$

$$Z'_0 = \frac{1}{Y'_0} = \frac{1}{Y_{01} + Y_{02}} = \frac{1}{\frac{1}{Z_{01}} + \frac{1}{Z_{02}}}$$

Impedance of Transmission Line Stubs

- Terminated general transmission lines

$$Z_{in} = Z_0 \frac{Z_L \cosh \gamma l + Z_0 \sinh \gamma l}{Z_L \sinh \gamma l + Z_0 \cosh \gamma l}$$

- Terminated lossless lines with unity velocity factor

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \frac{2\pi fl}{c}}{Z_0 + jZ_L \tan \frac{2\pi fl}{c}}$$


- Short-circuited stub reactance and susceptance

$$Z_{in} = jZ_0 \tan \frac{2\pi fl}{c} \quad Y_{in} = -jY_0 \cot \frac{2\pi fl}{c}$$

- Open-circuited stub reactance and susceptance


$$Z_{in} = -jZ_0 \cot \frac{2\pi fl}{c} \quad Y_{in} = jY_0 \tan \frac{2\pi fl}{c}$$

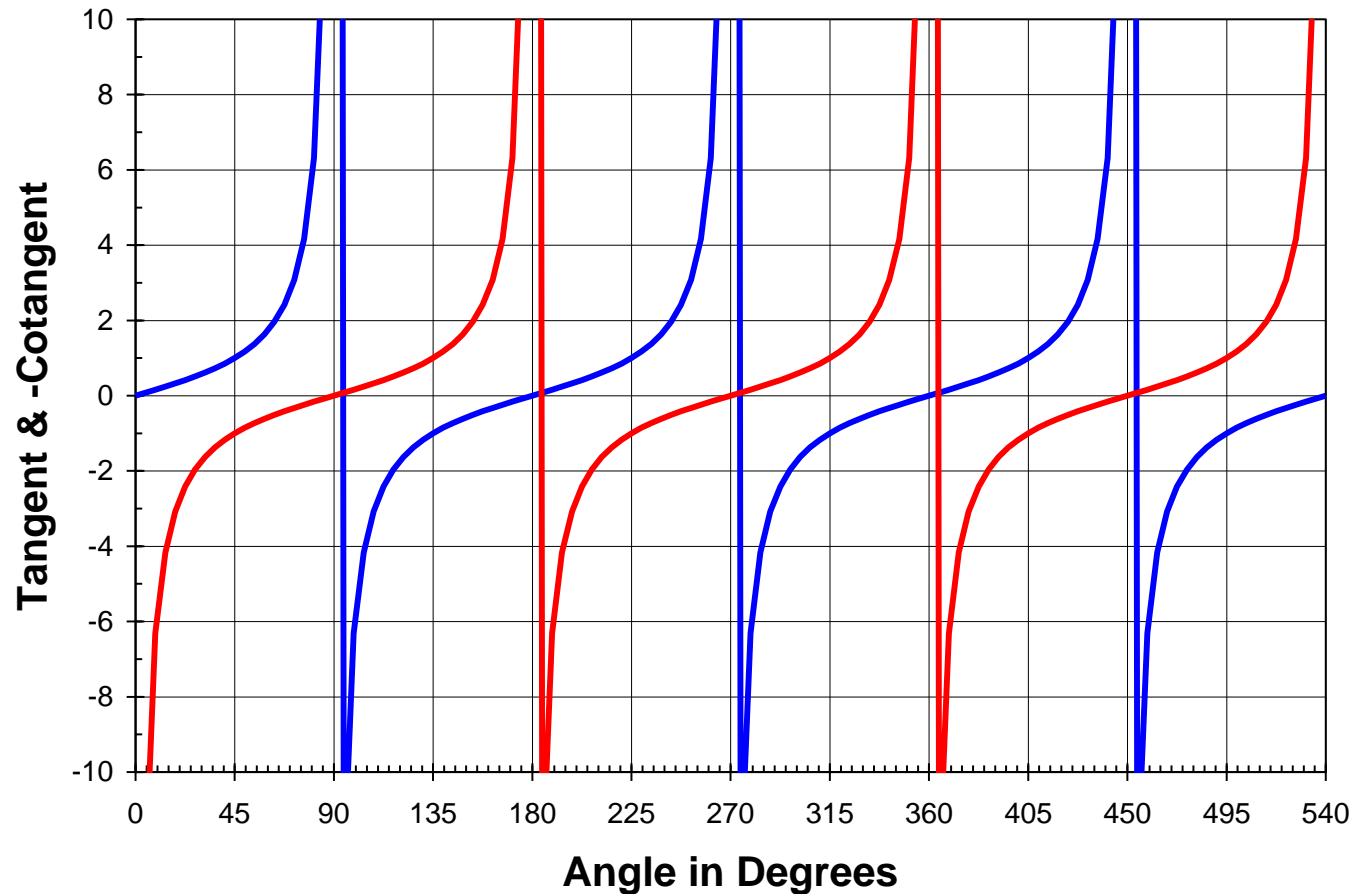Graph of Tangent and -Cotangent Functions



Foster's Reactance Theorem requires that reactance and susceptance of lossless devices and networks have positive slopes.

Smith Chart

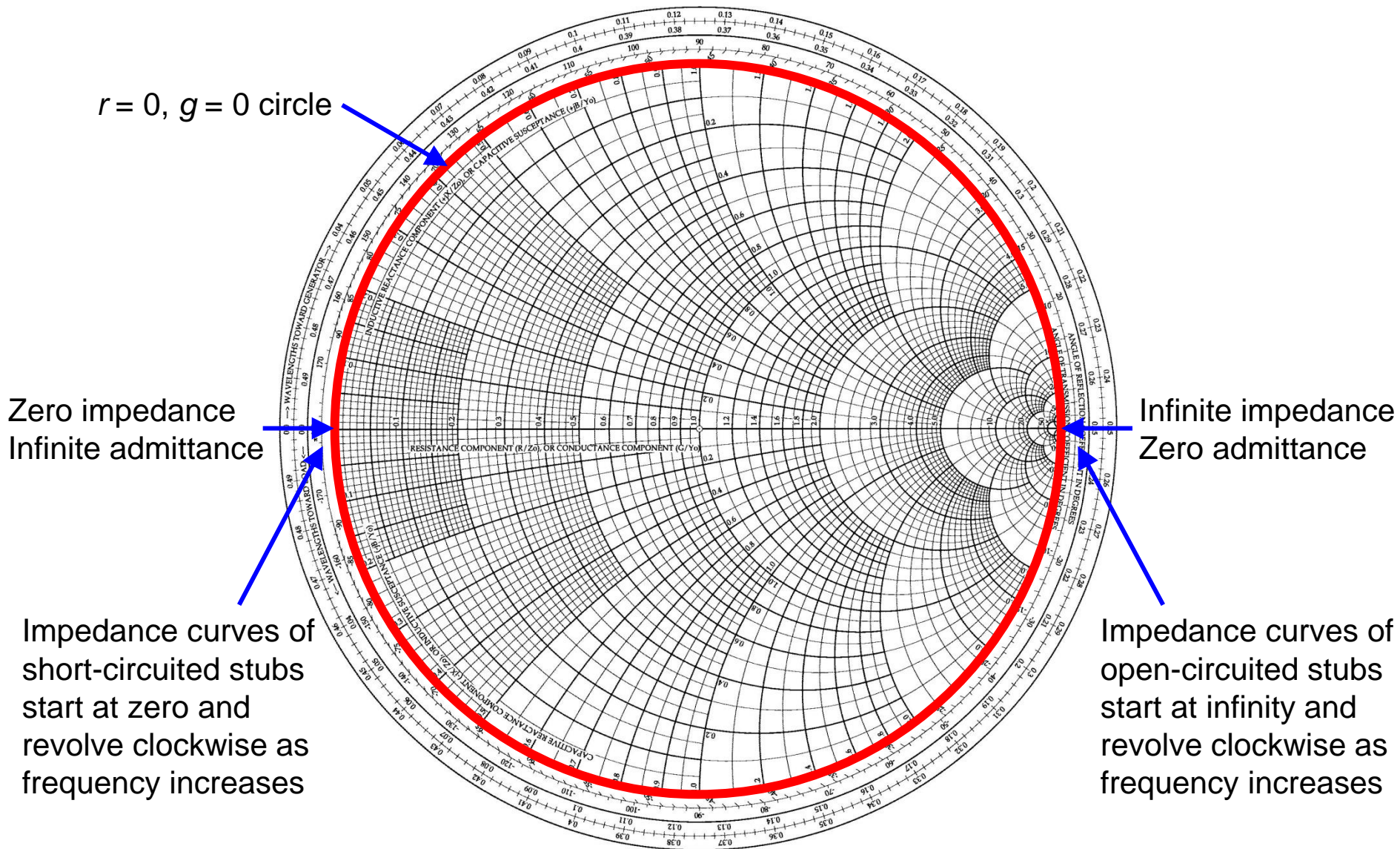

Electrically-Short Stubs As Capacitors and Inductors

- Open and shorted stubs that are electrically short act like lumped element capacitors and inductors
- Electrically-short short-circuited stubs act as inductors

$$Z_{in} = jZ_0 \tan \frac{2\pi fl}{c} \approx j2\pi f \frac{Z_0 l}{c} \Rightarrow L = \frac{Z_0 l}{c} = Z_0 \tau$$

- Electrically-short open-circuited stubs act as capacitors

$$Z_{in} = -jZ_0 \cot \frac{2\pi fl}{c} \approx \frac{1}{j2\pi f \frac{l}{Z_0 c}} \Rightarrow C = \frac{l}{Z_0 c} = \frac{\tau}{Z_0}$$

- Stubs may be used in place of capacitors and inductors to make filters

Capacitance and Inductance

- Set C and L by changing both Z_0 and l
- Set C and L by changing Z_0 with l fixed
- Set C and L by changing l with Z_0 fixed

Z_0	Short-Circuited Stubs nH per ft	Open-Circuited Stubs pF per ft
12.5	12.7	81.3
25	25.4	40.7
37.5	38.1	27.1
50	50.8	20.3
75	76.2	13.6
100	102	10.2
150	152	6.78
200	203	5.08

Quarter-Wave Stubs As Resonant Circuits

- Quarter-wave stubs act like resonant LC circuits
- Short-circuited stubs act like parallel resonant circuits

$$Z_{in} = jZ_0 \tan \frac{\pi}{2} \frac{f}{f_0} \quad \Rightarrow \quad L = \frac{2Z_0}{\pi^2 f_0} \quad C = \frac{1}{8Z_0 f_0}$$

- Open-circuited stubs act like series-resonant circuits

$$Z_{in} = -jZ_0 \cot \frac{\pi}{2} \frac{f}{f_0} \quad \Rightarrow \quad L = \frac{Z_0}{8 f_0} \quad C = \frac{2}{\pi^2 Z_0 f_0}$$

Exact 1-Port Equivalent Circuits of an Open Stub





$$Z_{in} = Z_0 \coth \gamma l = Z_0 \coth(\alpha l + j\beta l)$$

Constant, frequency-independent loss
 R, L, G, C are for total line length l

$$L = Z_0 \frac{l}{c} = Z_0 \tau$$

$$C = \frac{l}{Z_0 c} = \frac{\tau}{Z_0}$$

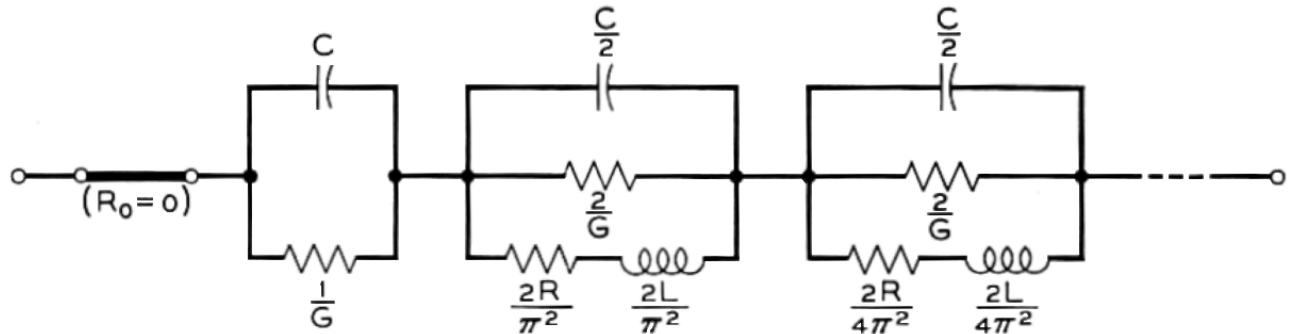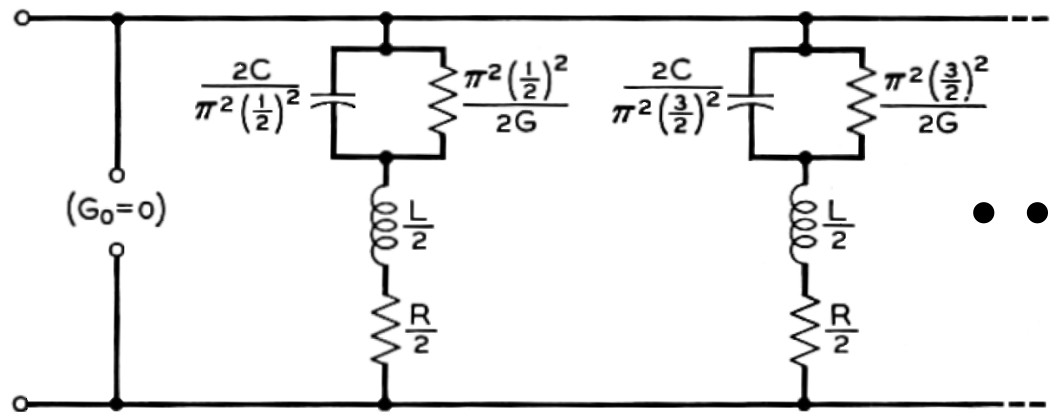

Exact 1-Port Equivalent Circuits of a Shorted Stub




$$Z_{in} = Z_0 \tanh \gamma l = Z_0 \tanh (\alpha l + j\beta l)$$

Constant, frequency-independent loss
 R, L, G, C are for total line length l

$$L = Z_0 \frac{l}{c} = Z_0 \tau$$
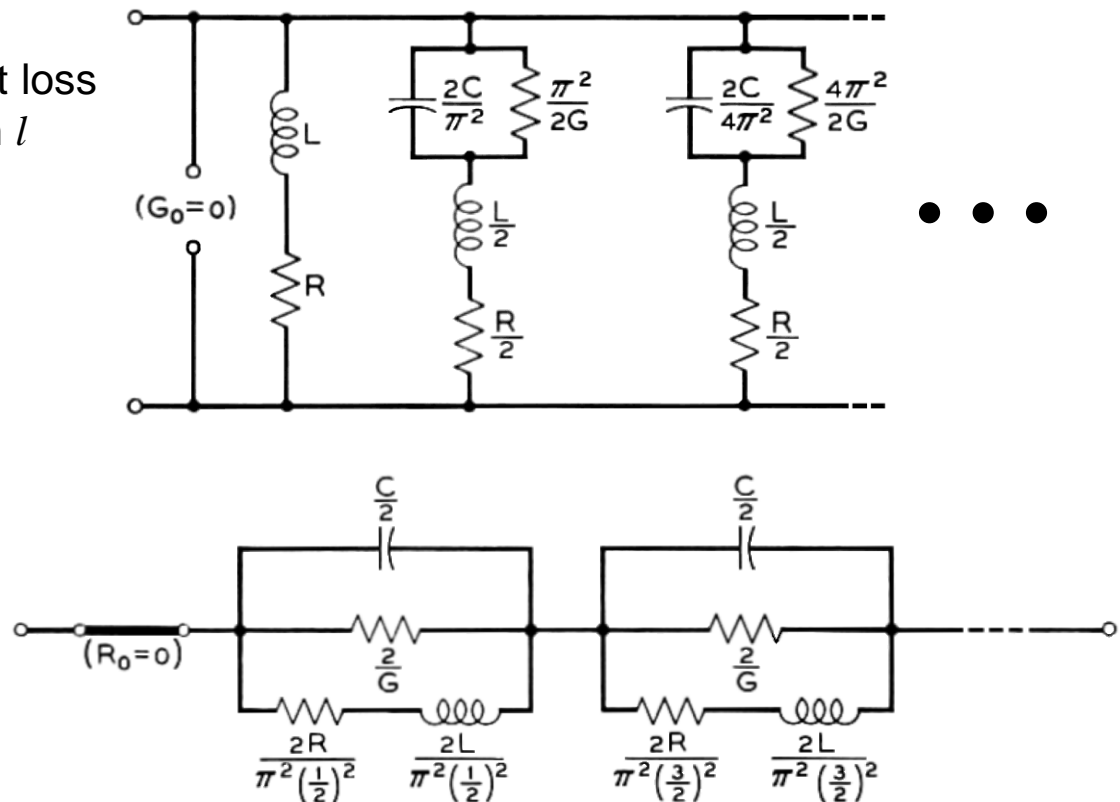
$$C = \frac{l}{Z_0 c} = \frac{\tau}{Z_0}$$



Evaluation of Broadband Open Stub Model in QUCS

Qucs 0.0.16 - Project: Open_Stub

File Edit Positioning Insert Project Tools Simulation View Help

Open-Stub.sch Open-Stub.dpl

transmission lines

Transmission Line 4-Terminal Transmission Line

Coupled Transmission Line Twisted-Pair

Coaxial Line Rectangular Waveguide

RLCG Substrate

Transmission Line

Microstrip Line Coupled Microstrip Line

Microstrip Corner Microstrip Mitered Bend

P1 Num=1 Z=50 Ohm

C1 C=C1 L1 L=L1

C2 C=C2 L2 L=L1

C3 C=C3 L3 L=L1

C4 C=C4 L4 L=L1

C5 C=C5 L5 L=L1

C6 C=C6 L6 L=L1

C7 C=C7 L7 L=L1

C8 C=C8 L8 L=L1

C9 C=C9 L9 L=L1

C10 C=C10 L10 L=L1

Cinfinity C=Cinf

P2 Num=2 Z=50 Ohm

Line6 Z=50 Ohm L=75

R1 R=1E08 Ohm

S parameter simulation

SP1
Type=lin
Start=10 kHz
Stop=30 MHz
Points=3000

Equation


Eqn1
L=12.50886E-06
L1=L/2
C=5003.4E-12
C1=8*C/(pi*1)^2
C2=8*C/(pi*3)^2
C3=8*C/(pi*5)^2
C4=8*C/(pi*7)^2
C5=8*C/(pi*9)^2
C6=8*C/(pi*11)^2
C7=8*C/(pi*13)^2
C8=8*C/(pi*15)^2
C9=8*C/(pi*17)^2
C10=8*C/(pi*19)^2
Cinf=120E-12

Equation

Eqn2
Z=stoz(S,50)
reactance1=imag(Z[1,1])
reactance2=imag(Z[2,2])

no warnings 0:0

Broadband Open Stub Model for 0 – 19 MHz

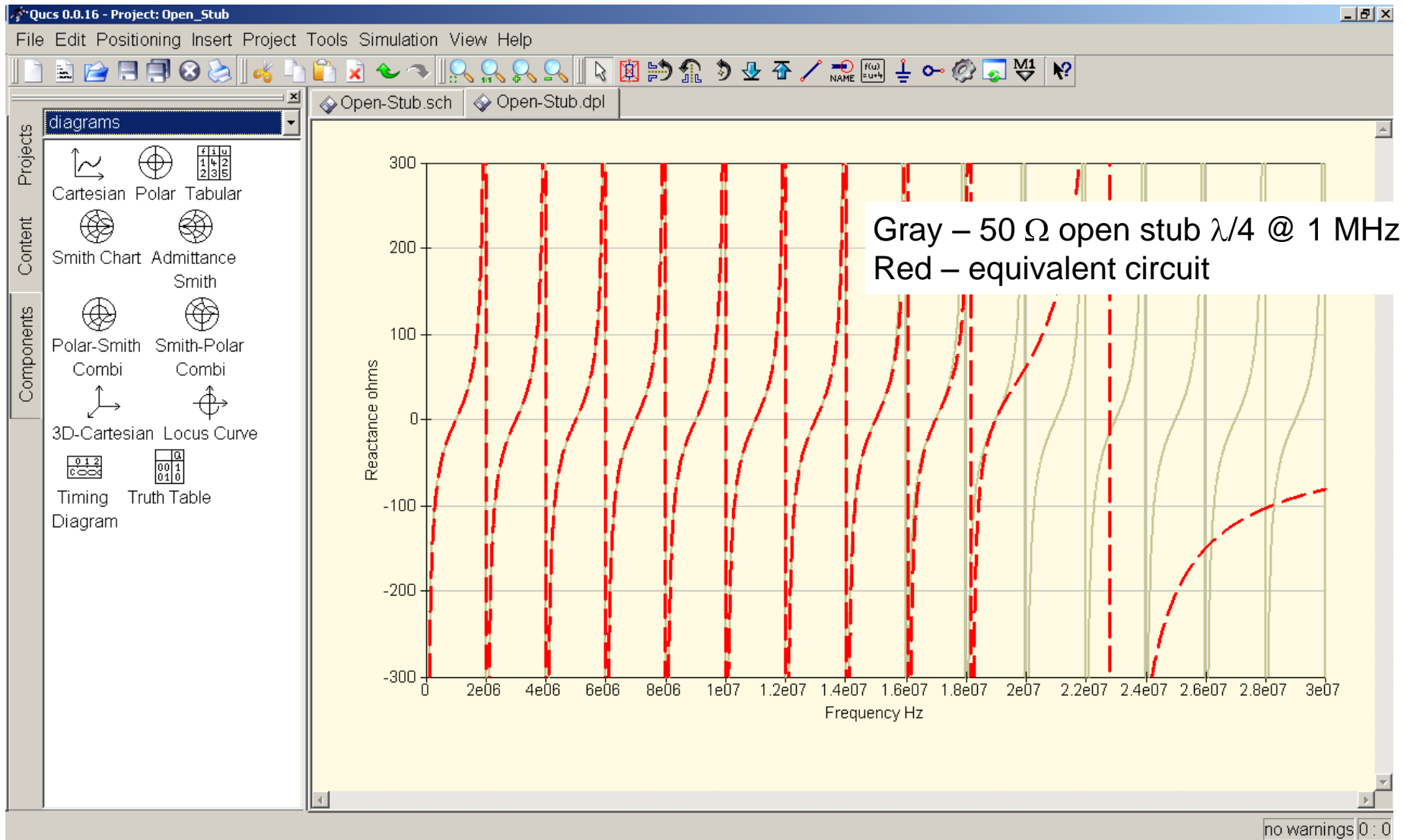

Floating Stubs


- Some stubs may need to float, e.g. series stubs
- Floating stubs require common mode chokes

K9YC Chokes (Improvements on W1JR, W2DU Designs)




Transmission Line Filters

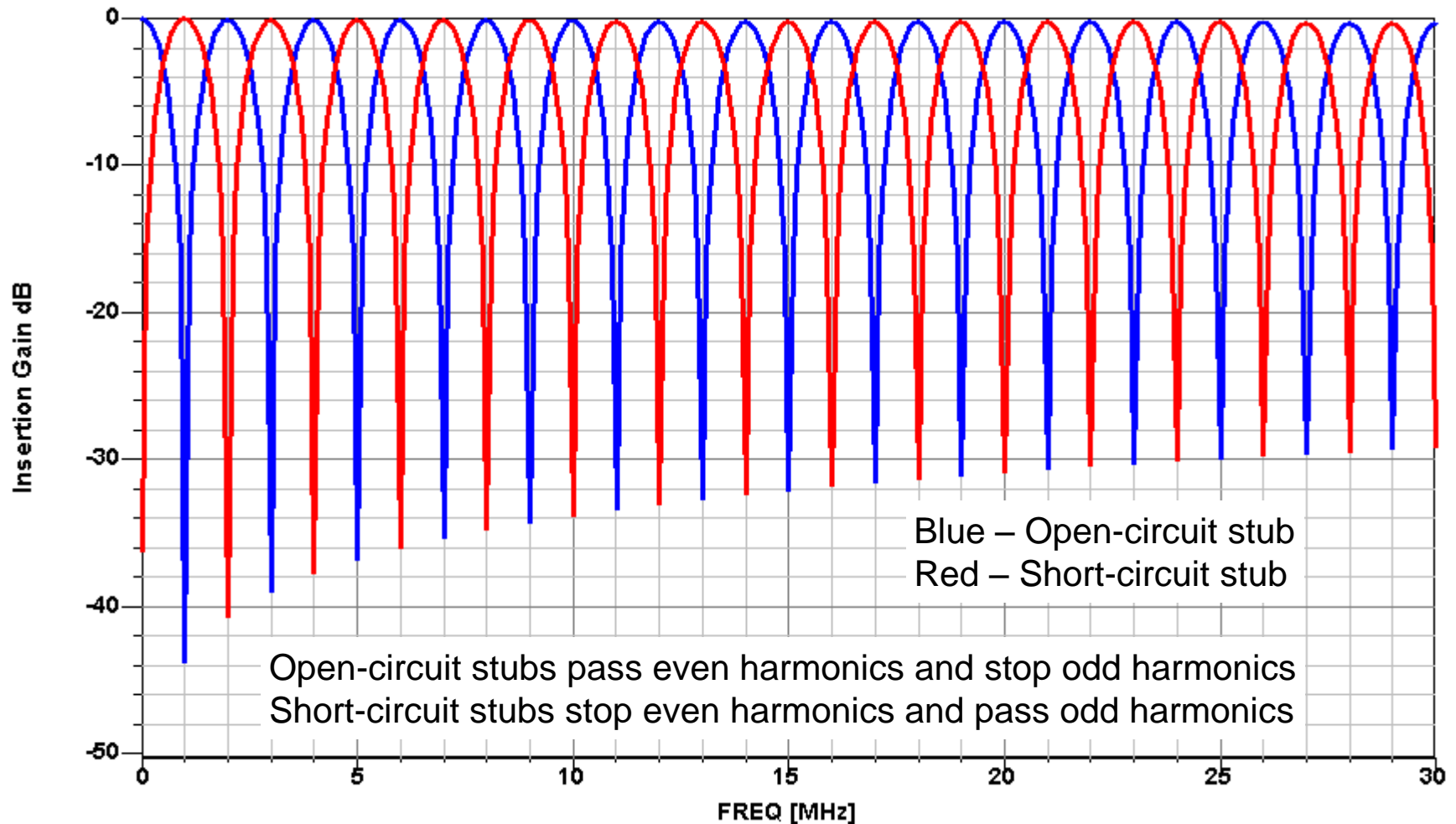
Single Shunt Stub Filter, Quarter-Wave at 1 MHz



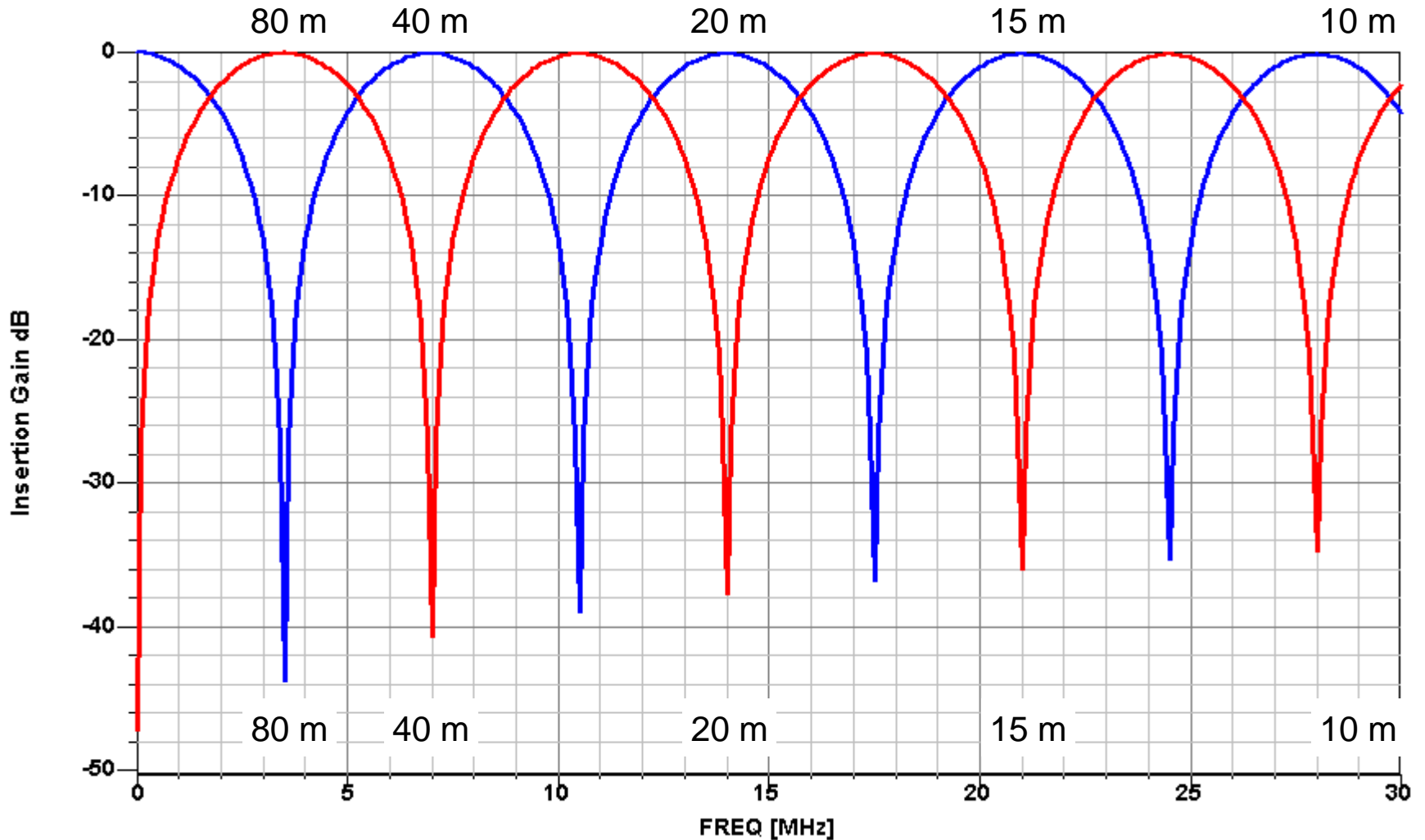
Many Amateur HF Bands are Harmonically Related



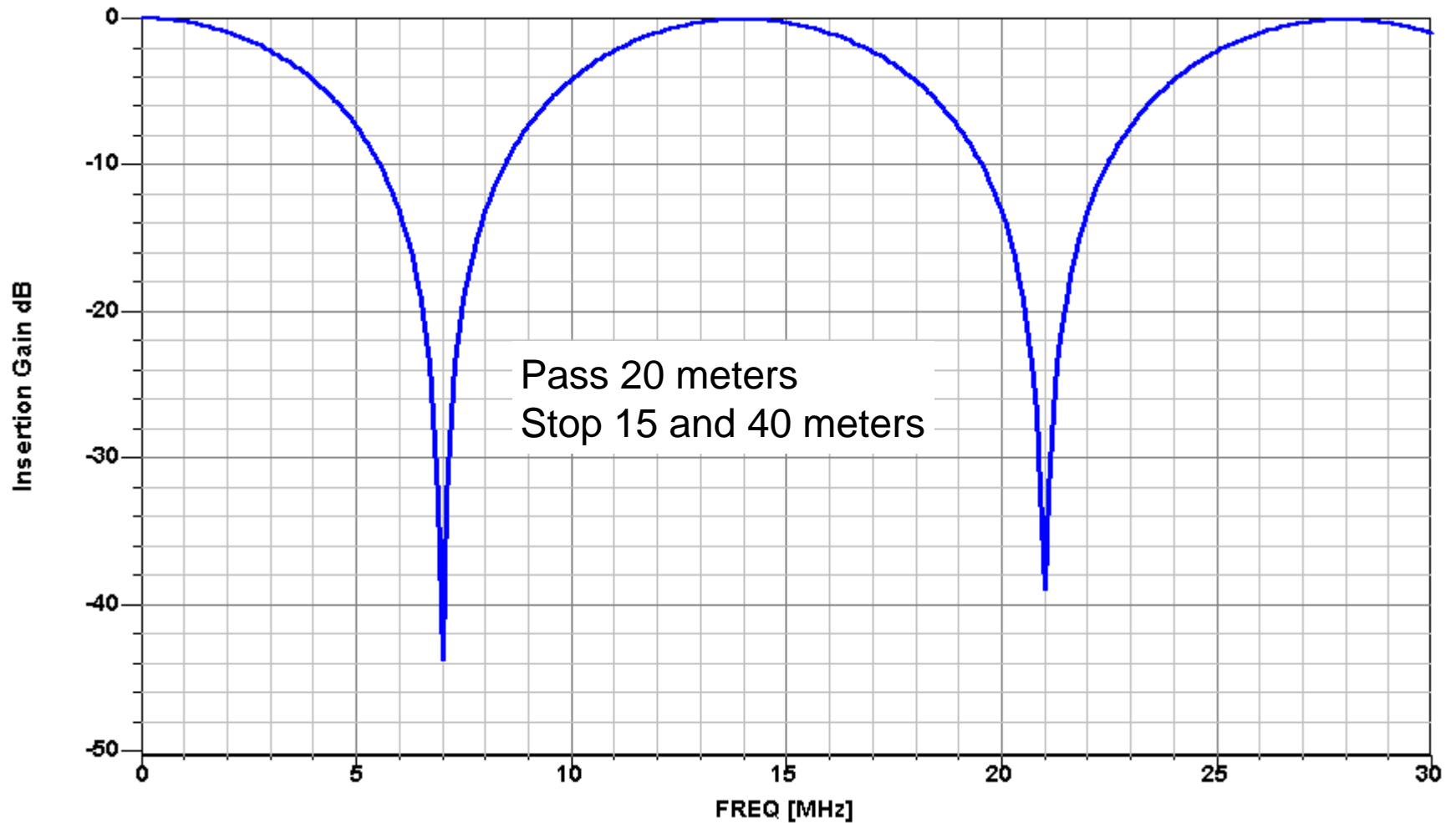Example 1 of Single Open-Circuited Stub Filter



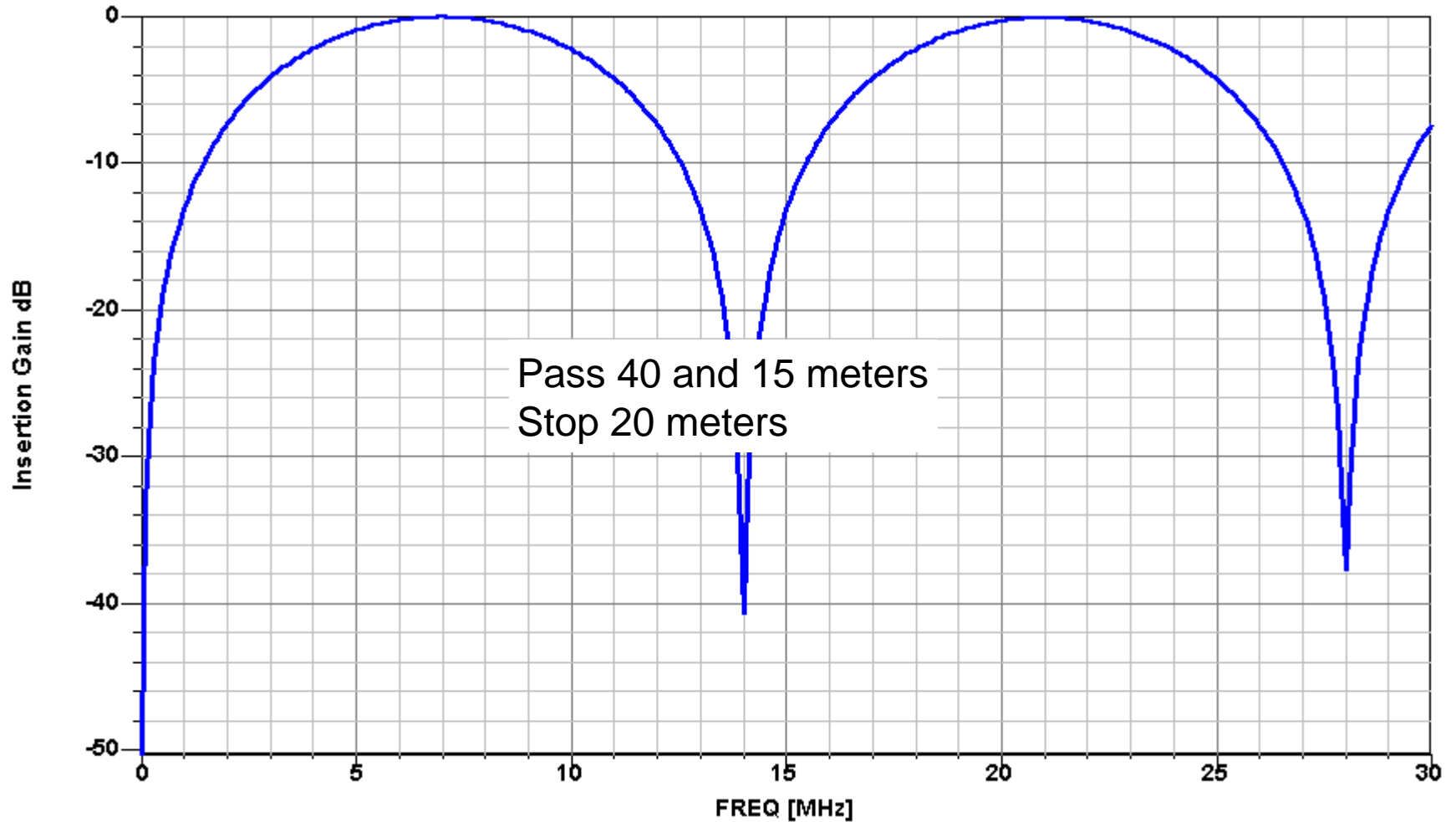Example 2 of Single Short-Circuited Stub Filter



Simple Transmission Line Filters

FILTER NO.	STRUCTURE	CHARACTERISTIC ATTENUATION	CHARACTERISTIC IMPEDANCE
1			
2			

3			
4			

5			
6			

W.P. Mason and R.A. Sykes, *Bell Syst. Tech. J.*, July 1937

Warren Perry Mason, 1900-1986



Courtesy of AT&T Archives and History Center

Filters with Multiple Pass and Stop Frequencies

- Suppose we are given a set of discrete frequencies in ascending order

$$f_1 < f_2 < \dots < f_{N-1} < f_N$$

- Each frequency is designated as either pass or stop
- Consider the case of three frequencies
- We focus on the non-trivial cases
 - 2 pass and 1 stop frequency
 - 2 stop and 1 pass frequency

f_1	f_2	f_3
Pass	Pass	Pass
Pass	Pass	Stop
Pass	Stop	Pass
Pass	Stop	Stop
Stop	Pass	Pass
Stop	Pass	Stop
Stop	Stop	Pass
Stop	Stop	Stop

Design Synthesis Procedure for Reflection Stub Filter


- **Decide 1 or 2 pass frequencies and 1 or 2 stop frequencies**
- **Decide port impedances – antenna or 50 ohms**
- **Synthesis procedure for ladder network:**
- **Step 1**
 - Insert quarter wave open stubs or half-wave shorted stubs for each stop frequency, stubs all in shunt
- **Step 2 (on Smith chart)**
 - For 1 pass frequency, insert transmission line section and adjust Z_0 and length to revolve the impedance point of the pass frequency to center
 - For 2 pass frequencies, insert transmission line section and adjust Z_0 and length to revolve the impedance points of both pass frequencies to the unit conductance circle, i.e. $g = 0$
- **Step 3 (for 2 pass frequencies)**
 - If the upper pass frequency point is above (counter-clockwise) from the lower pass frequency point, insert a shunt open stub and adjust length to bring both points to center
 - If the upper pass frequency point is below (clockwise) from the lower pass frequency point, insert a shunt shorted stub and adjust length to bring both points to center
- **Final step – fine tune design**
 - Run optimizer on all adjustable parameters to dial in design goals (bandwidths, insertion loss, SWR) and satisfy design constraints (allowed Z_0 values)

Pager Rejection Filter


K6OIK

ARRL Pacificon 2002

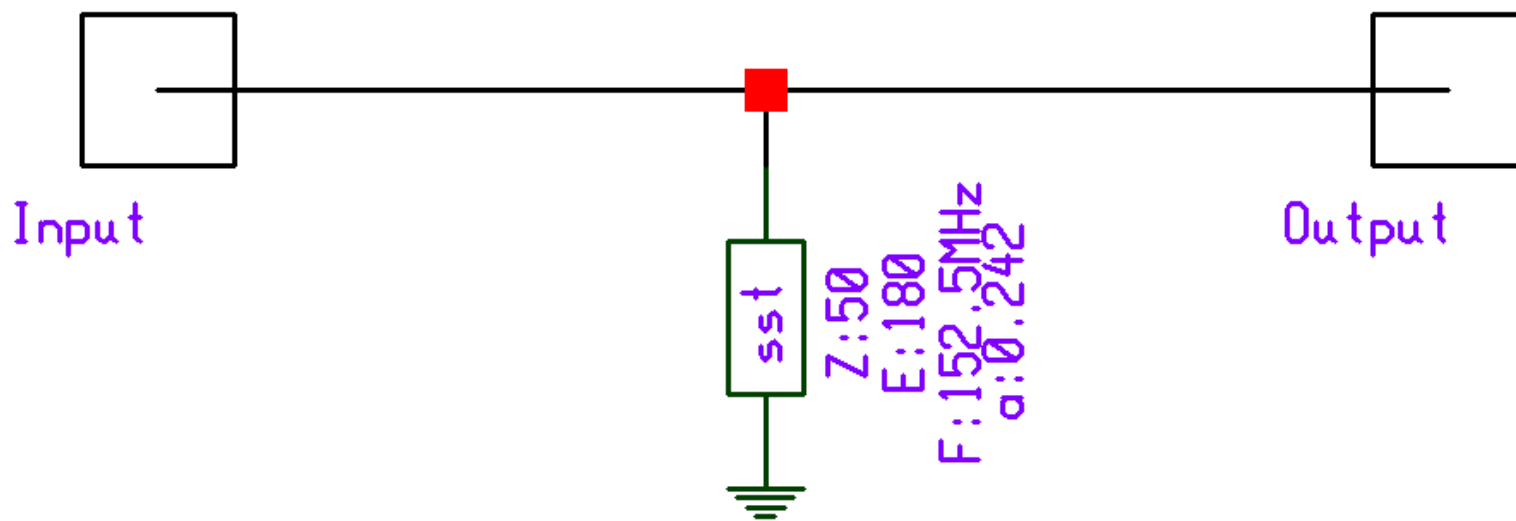First Attempt: The Classic Trap Filter Half-Wavelength Shorted Stub in Shunt




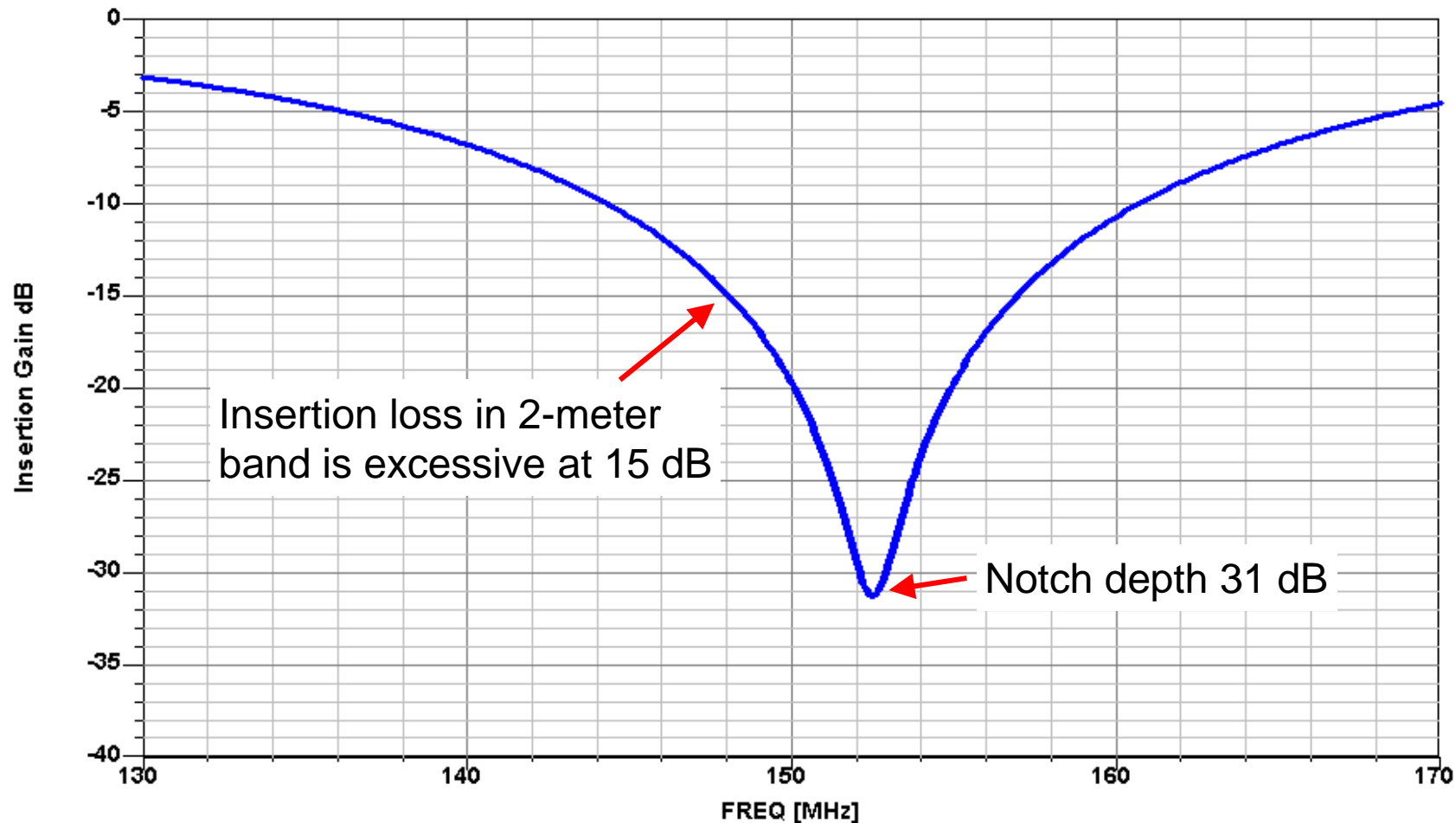Good Notch Depth But High Insertion Loss in 2-Meter Band!




First Modification

Change Stub to RG62 High-Impedance Coax

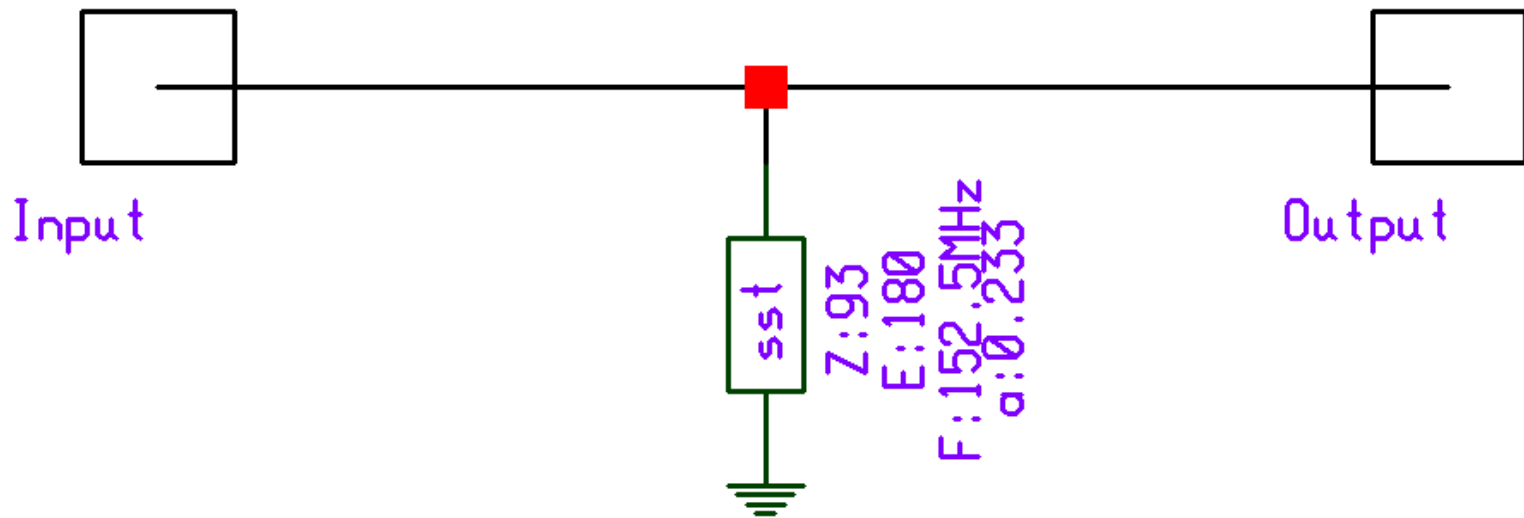


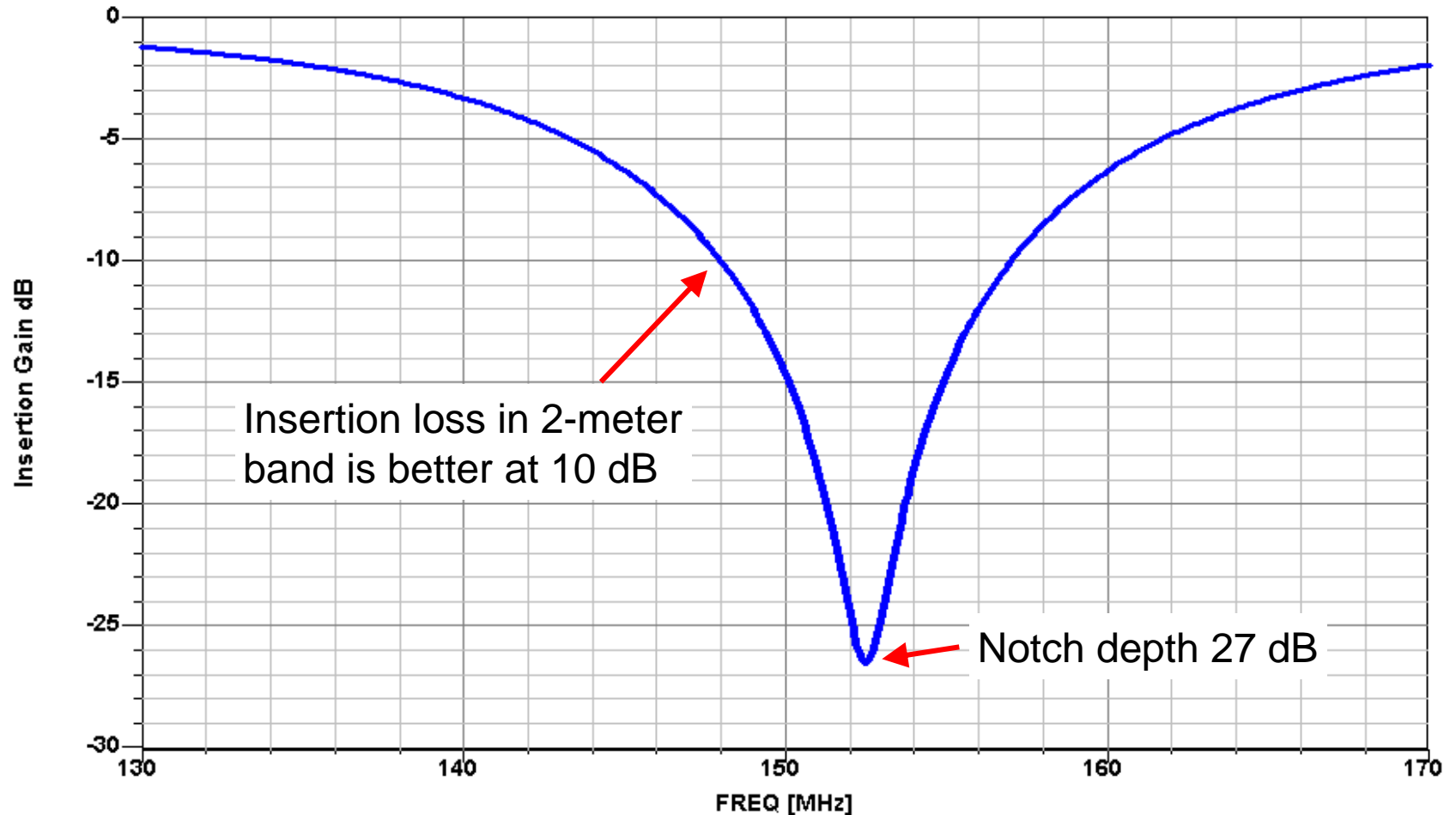Reduced Insertion Loss in 2-Meter Band But More Improvement Needed!



Second Modification

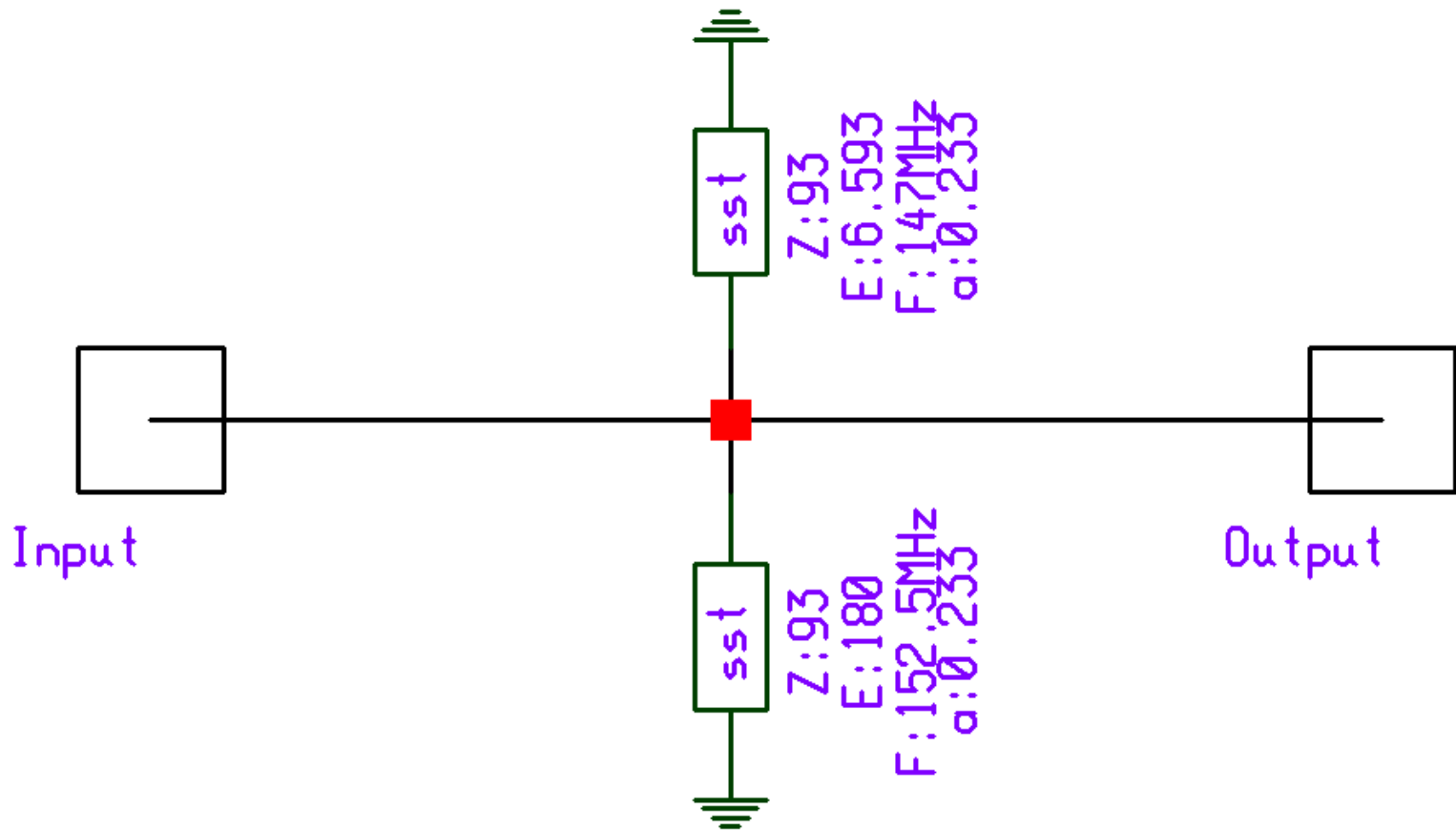
Second Stub Peaks 2-Meter Response via Inductance




How It Works

- **Notch frequency is above pass frequency**
- **Primary rejection stub acts like**
 - Series resonant circuit at the notch frequency
 - Shunt capacitor at the pass frequency
- **Second stub in parallel with primary stub acts like**
 - Inductor at the pass frequency
- **Together the stubs act like a parallel resonant circuit at the pass frequency, i.e. high shunt impedance**
- **Notch depth and insertion loss at pass frequency are limited only by line losses of stubs**
- **Use of low-loss line gives:**
 - Deeper null at notch frequency
 - Smaller insertion loss at pass frequency


Frequency Response of Two-Stub Filter

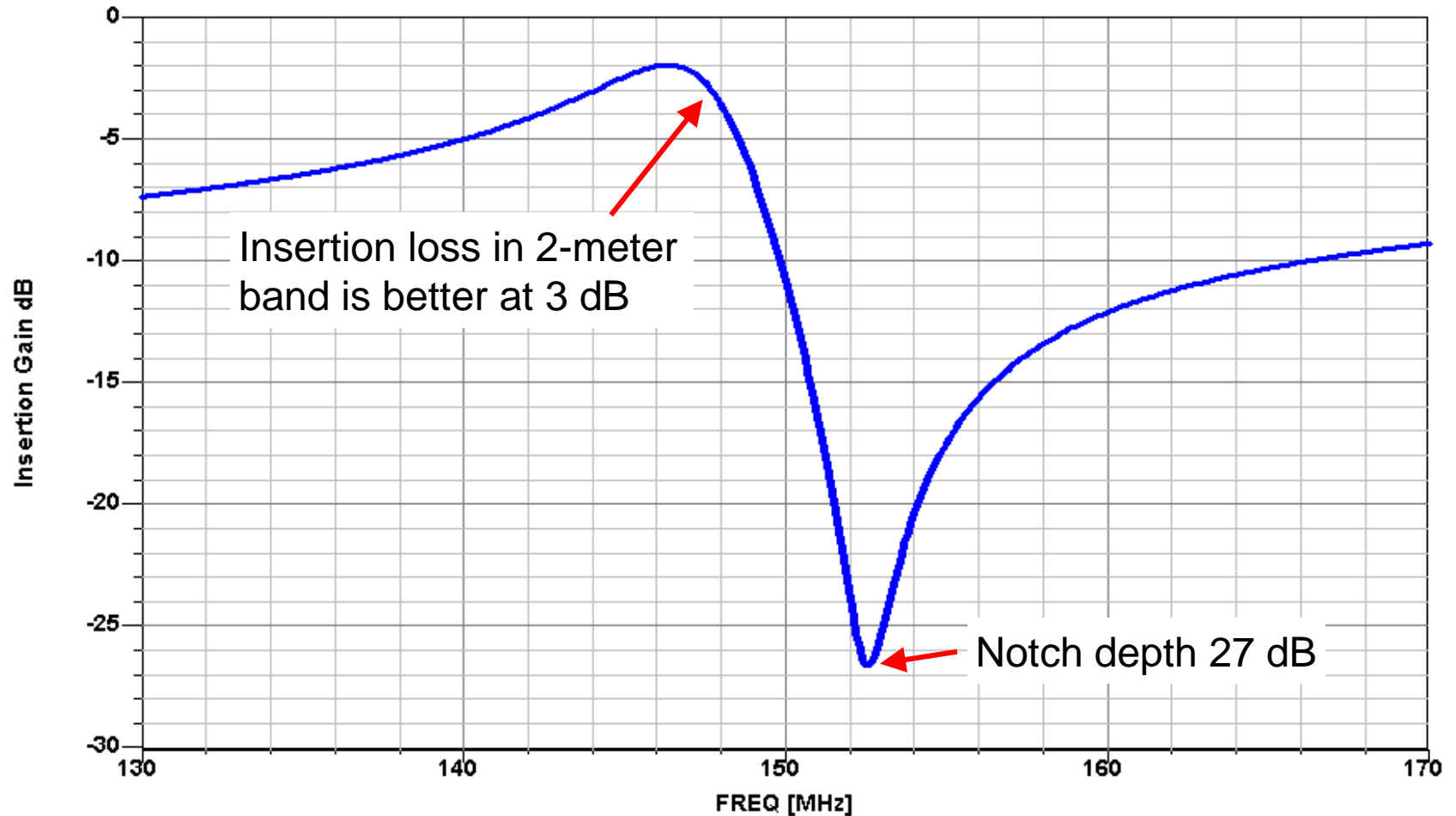


Input SWR of Two-Stub Filter

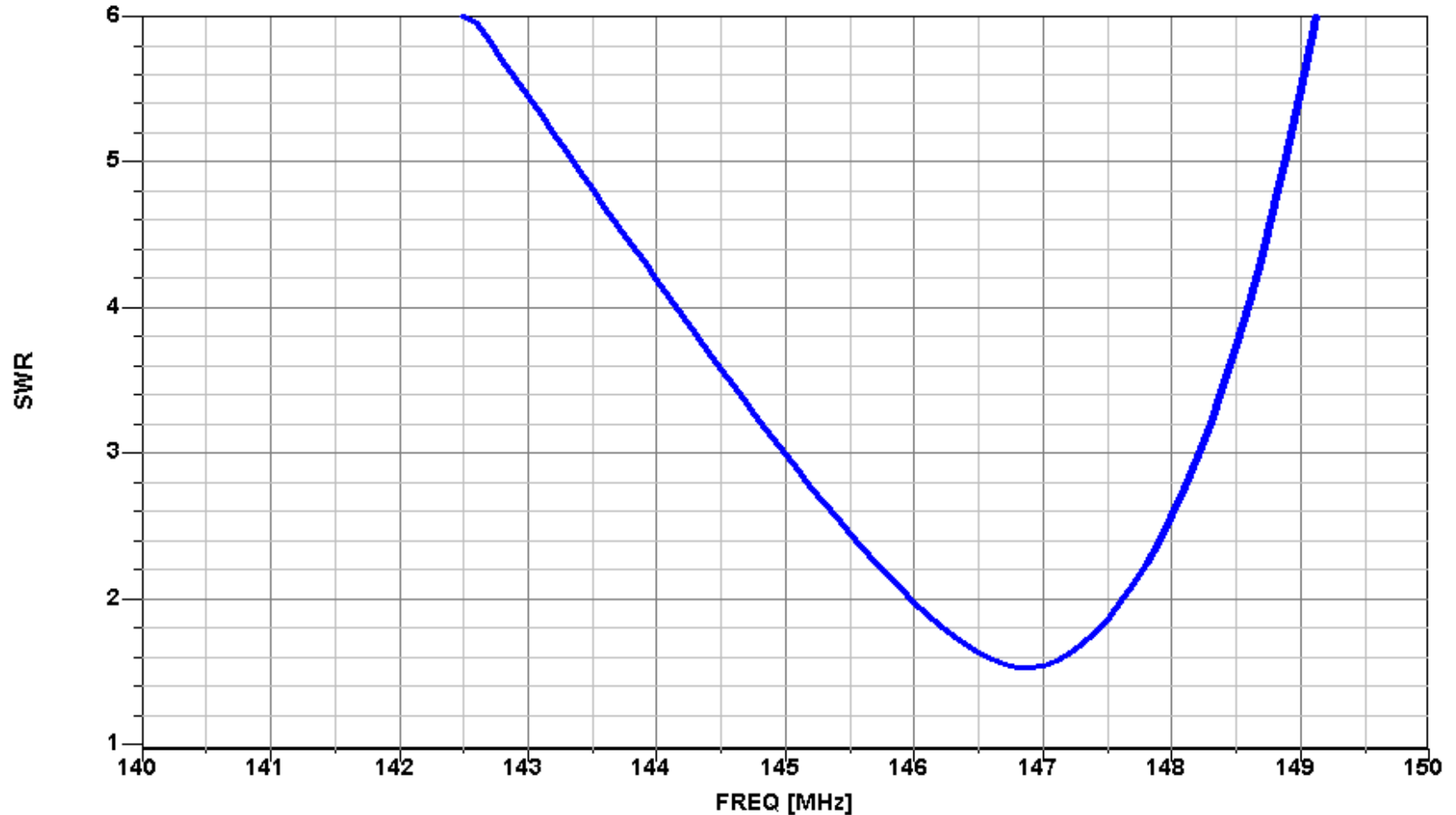

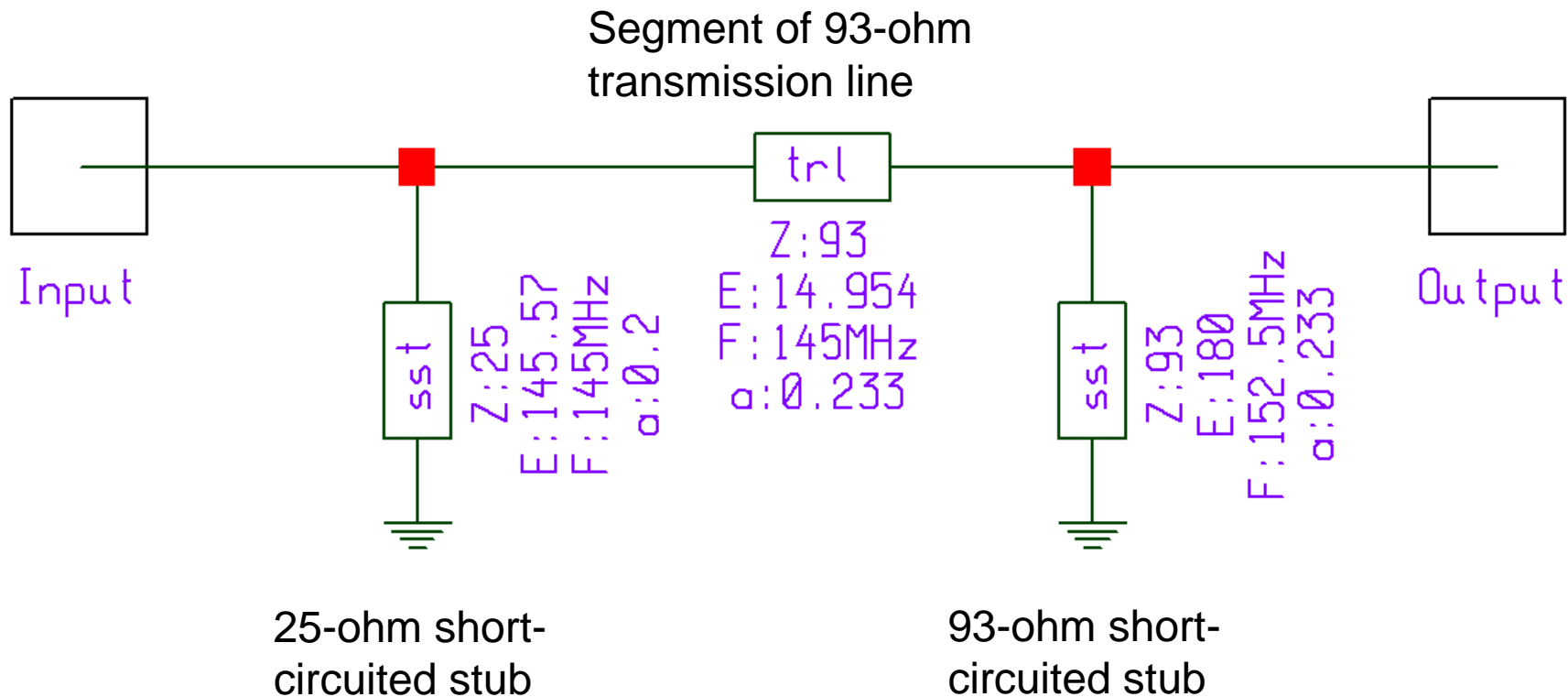
Third Modification – Transmission Line between Stubs Gives LPF Response



Low-Pass Filter with a Rejection Notch

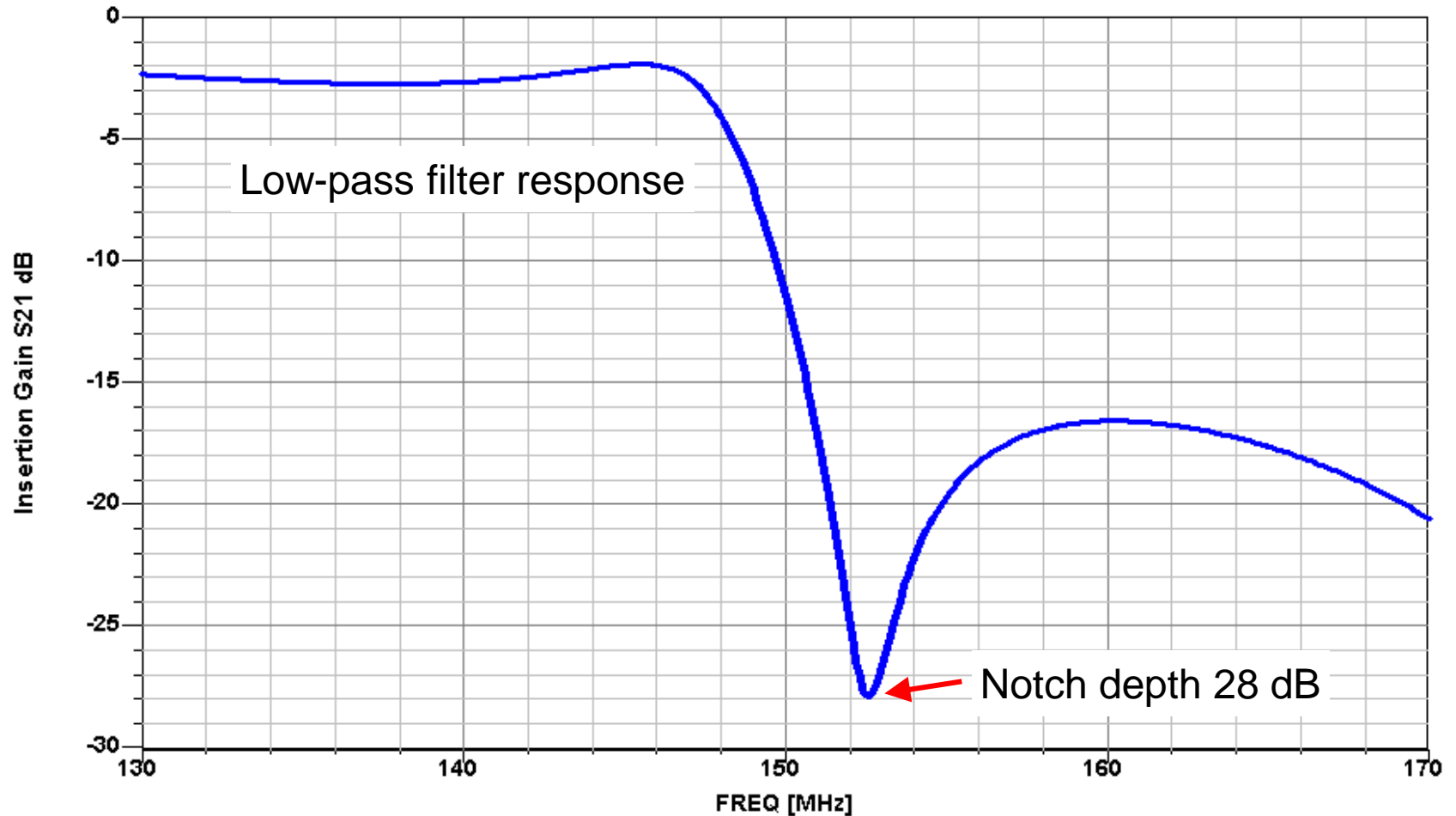


Input SWR of Improved 2-Stub Filter

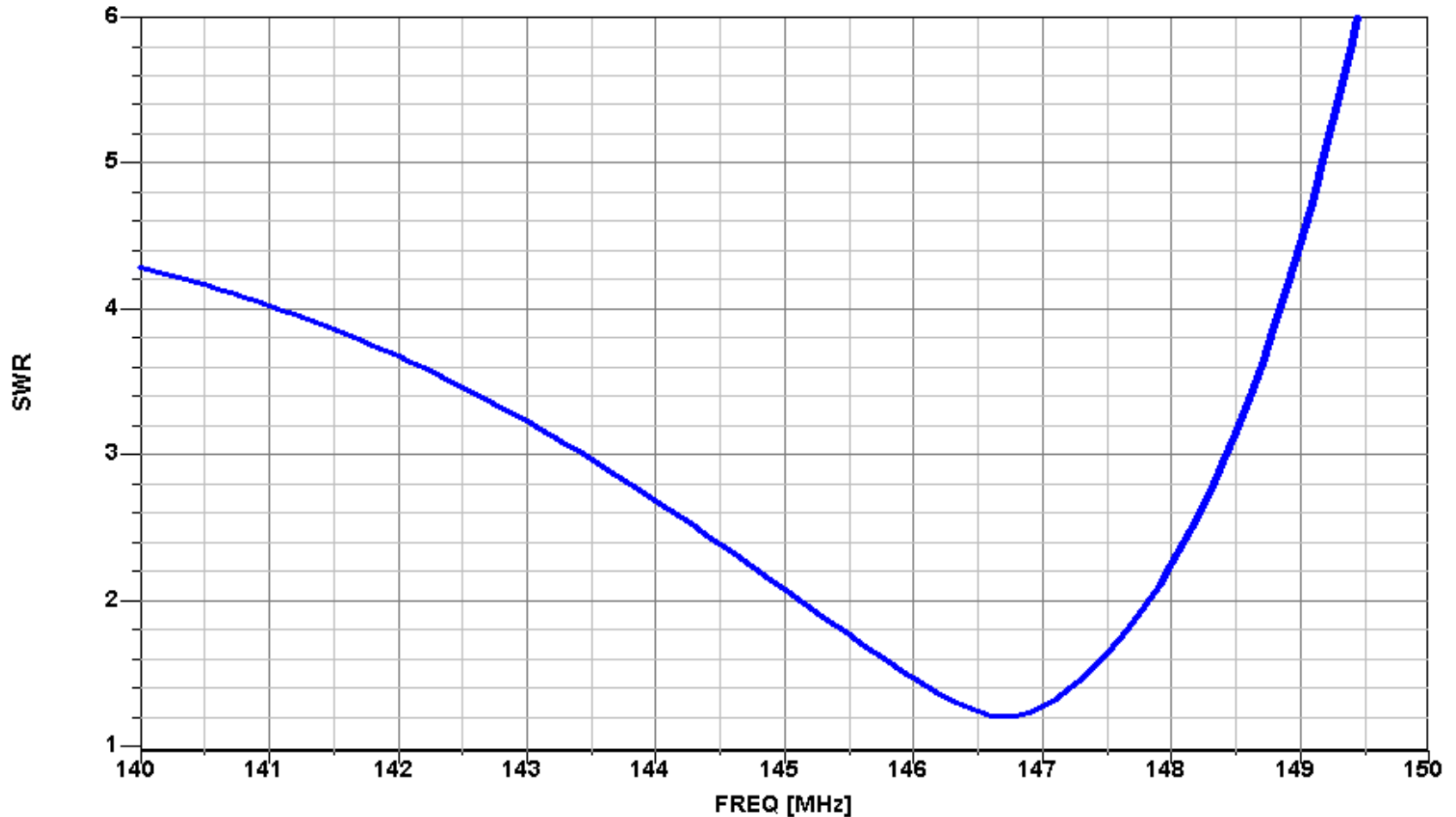

Hybrid Filters Using Lumped Elements and Stubs


DL1GBH 2-Meter Harmonic Filter

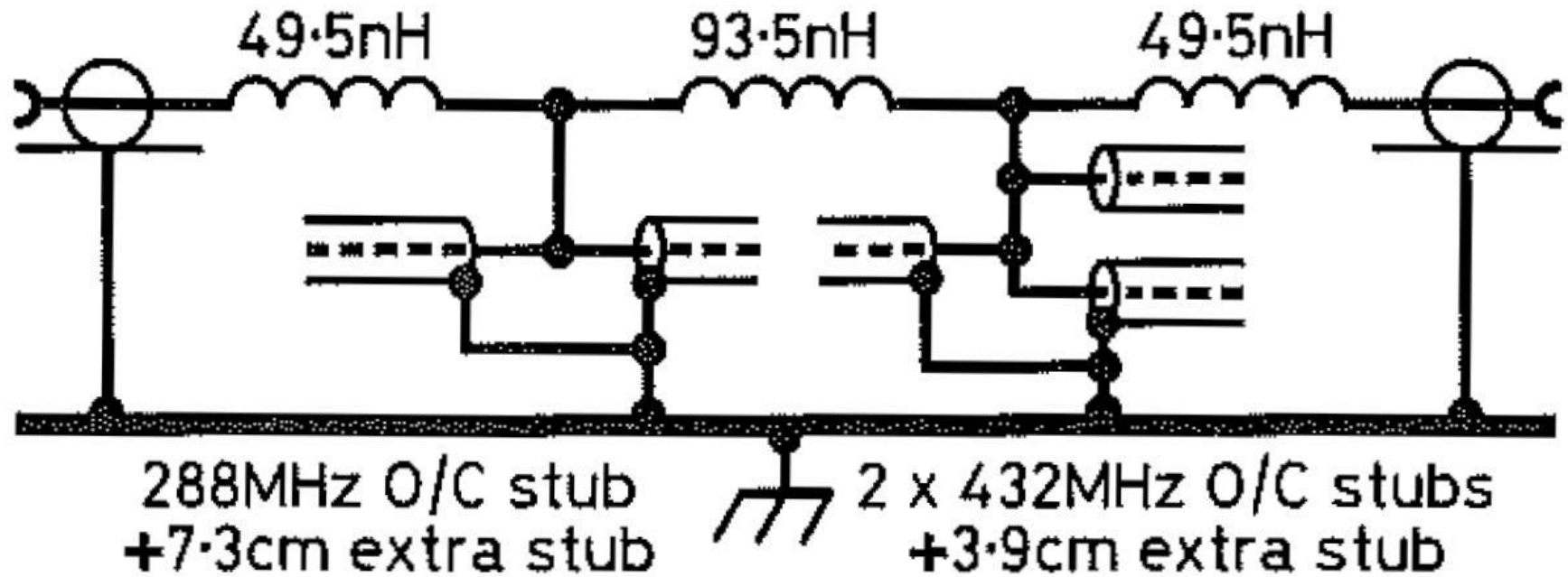

© RSGB RC337

J. Regnault, G4SWX, *RadCom* (RSGB), Nov. 1994

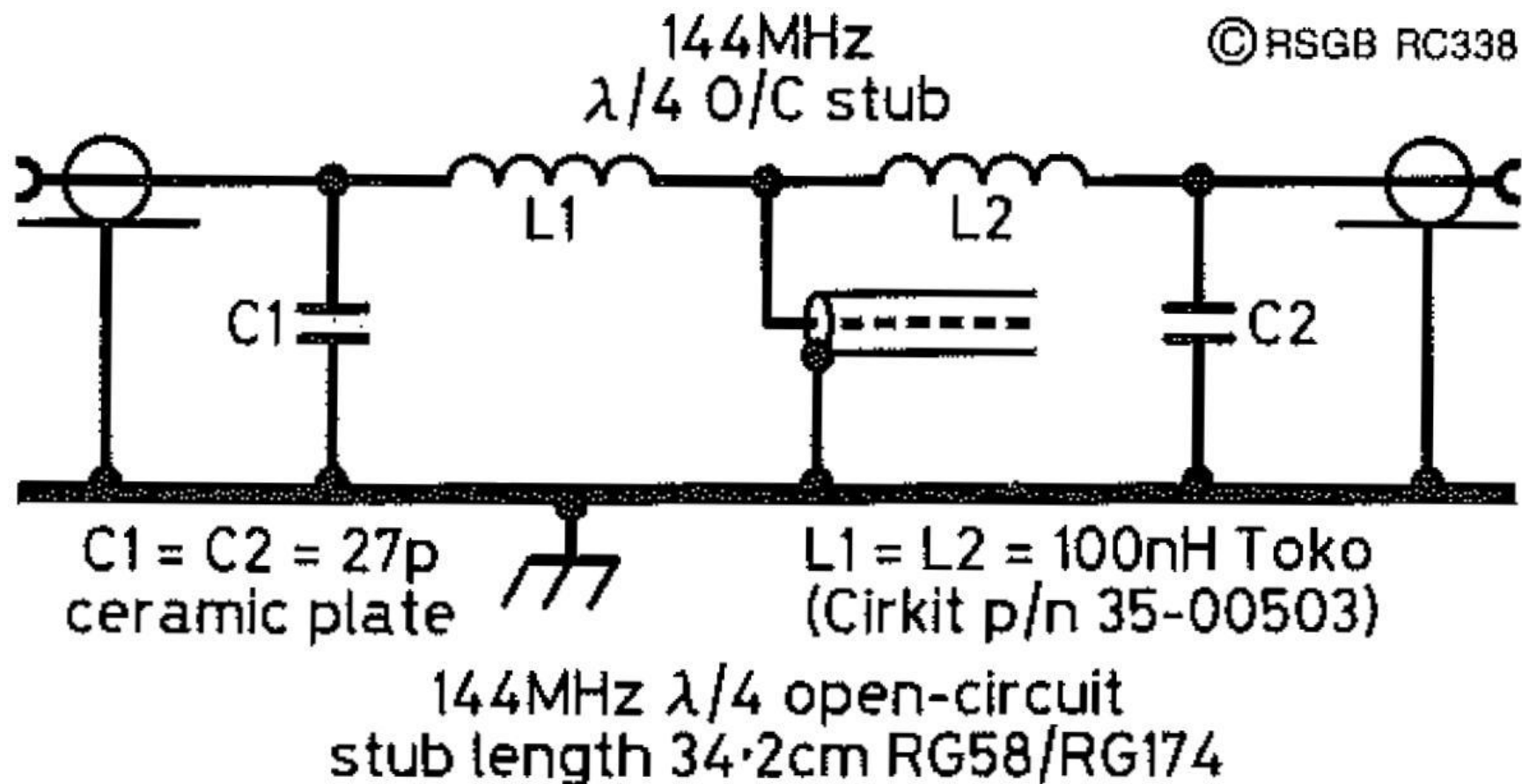
G4SWX FM Broadcast Pass, 2-Meter Reject Filter




J. Regnault, G4SWX, *RadCom* (RSGB), Nov. 1994

FM Broadcast, 2-Meter Reject Filter Performance

© RSGB RC339

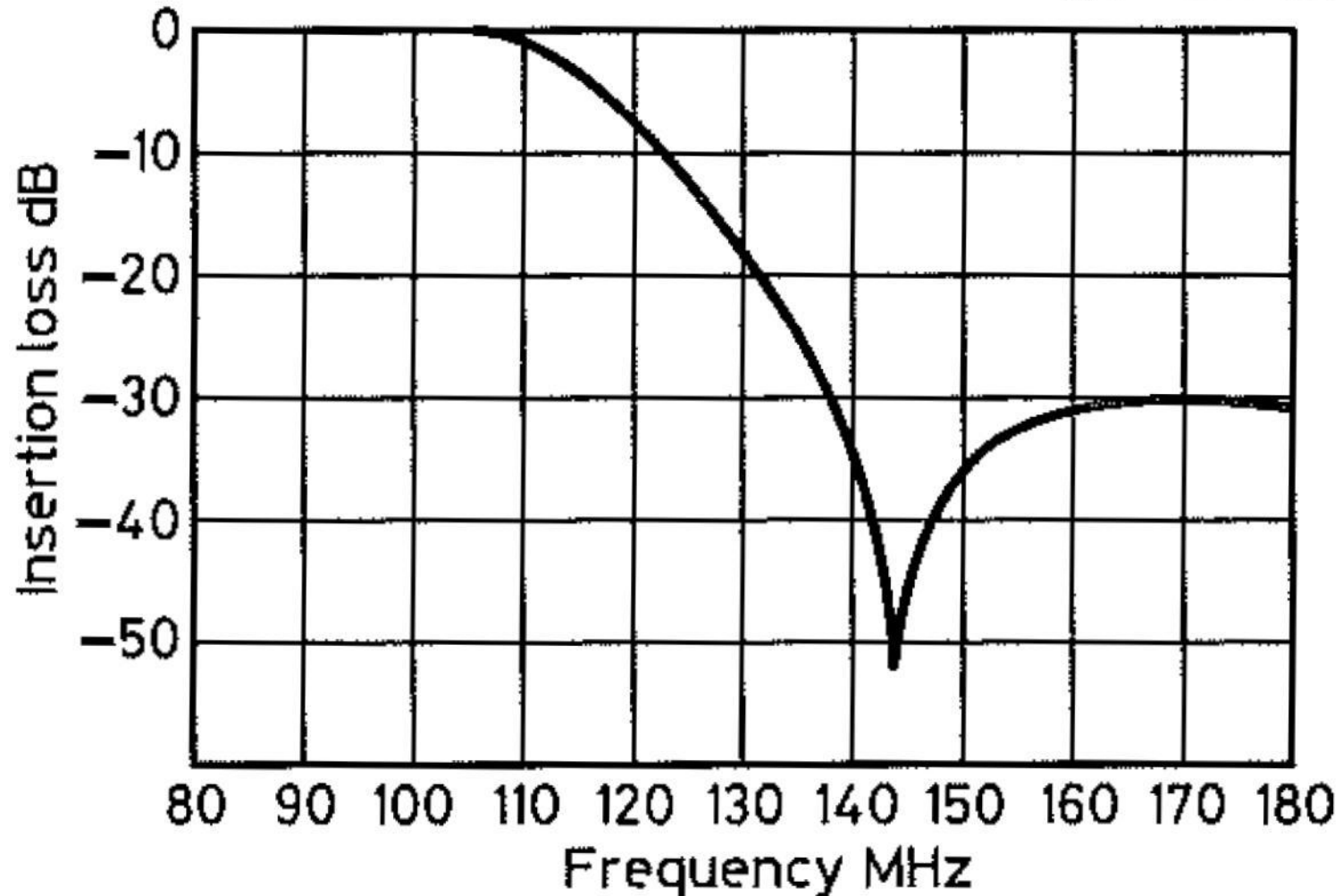

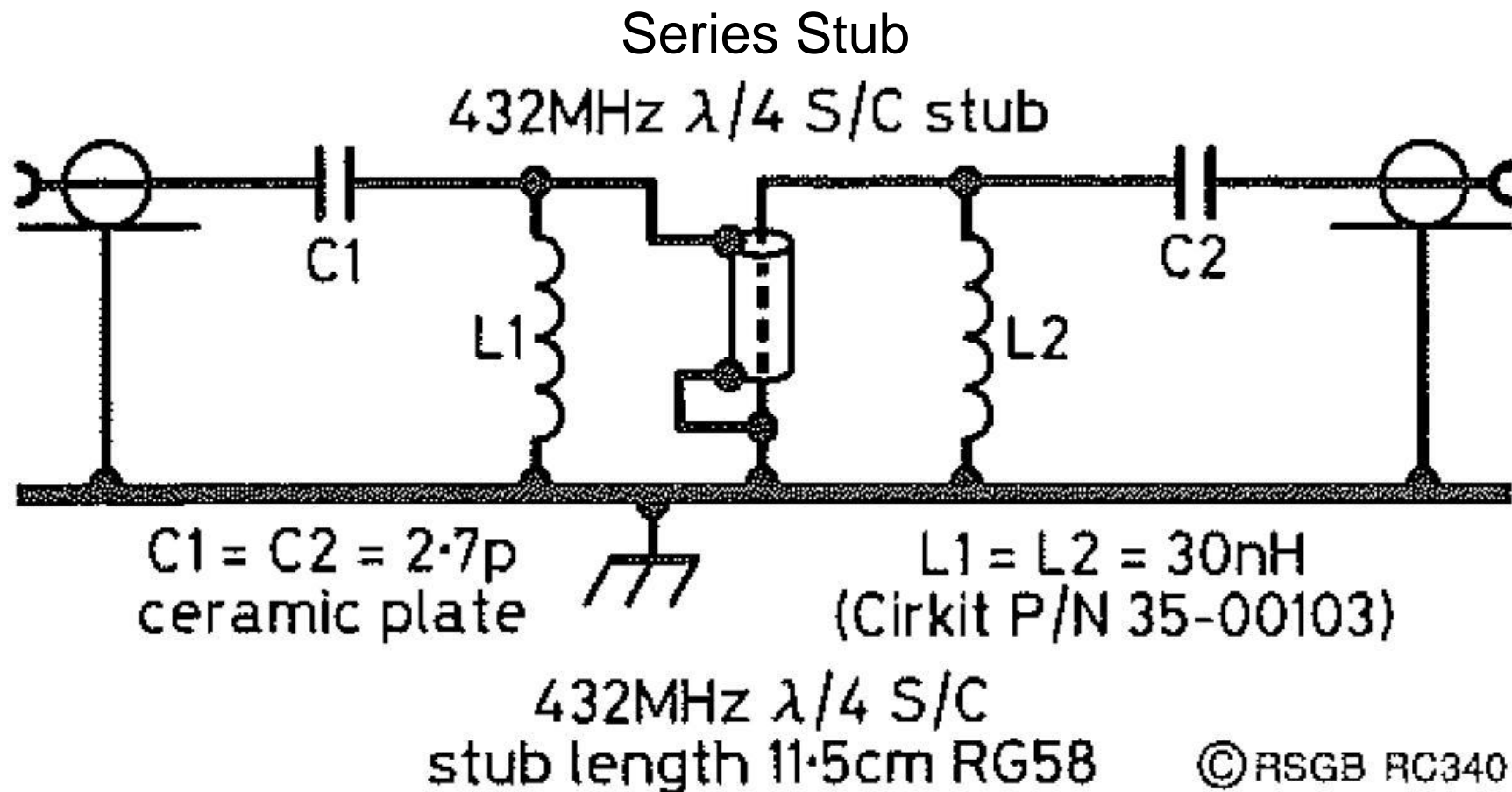
G4SWX UHF TV Pass, 432 and 1296 MHz Reject Filter




J. Regnault, G4SWX, *RadCom* (RSGB), Nov. 1994

UHF TV Filter Performance

© RSGB RC341

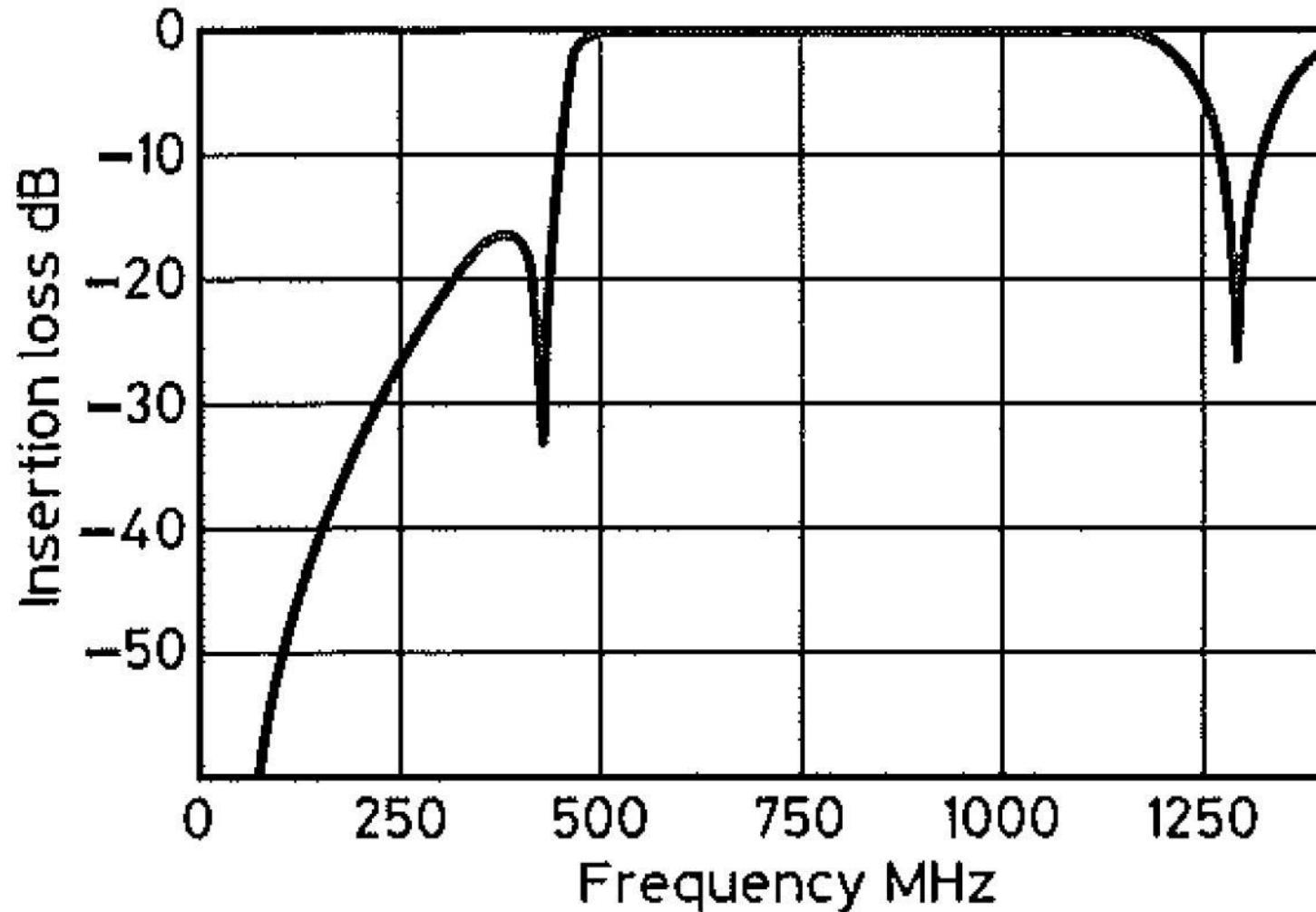

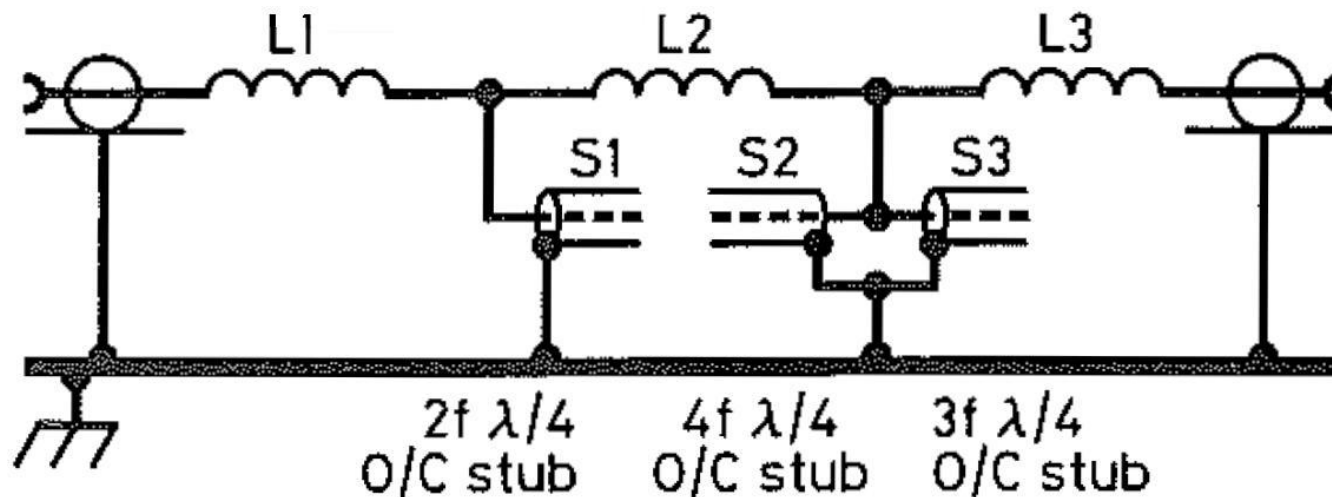G4SWX Tx Low Pass Filters for 50 & 144 MHz Bands




	50MHz	144MHz	
L1 = L3	175nH	60nH	
L2	340nH	115nH	
S1	48.9cm	17.2cm	all stubs
S2	24.7cm	8.6cm	UR43/
S3	32.7cm	11.5cm	RG58 coax

©RSGB RC342

J. Regnault, G4SWX, *RadCom* (RSGB), Nov. 1994


50 MHz Tx Low Pass Filter Performance

© RSGB RC343

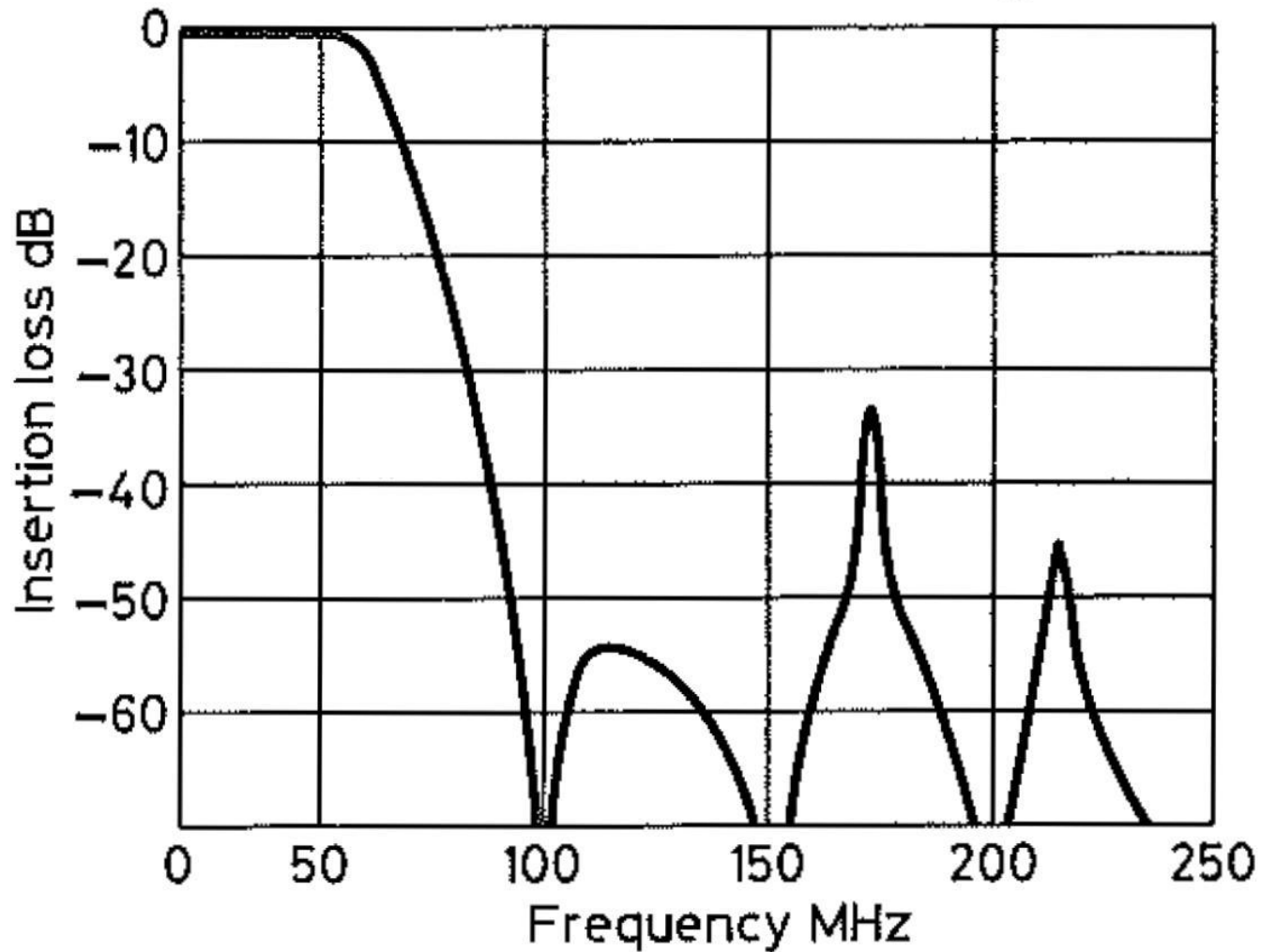


Sub-Band Filters for Field Day


Sub-Bands to be Isolated by Filtering

Band (meters)	CW / Digital Sub-band	Phone Sub-band	Transition Skirt Width
10	28.000 – 28.150	28.300 – 28.500	0.53%
15	21.000 – 21.100	21.200 – 21.450	0.47%
 20	14.000 – 14.150	14.200 – 14.350	1.06%
40	7.000 – 7.100	7.150 – 7.300	0.70%
80	3.000 – 3.600	3.700 – 4.000	2.74%

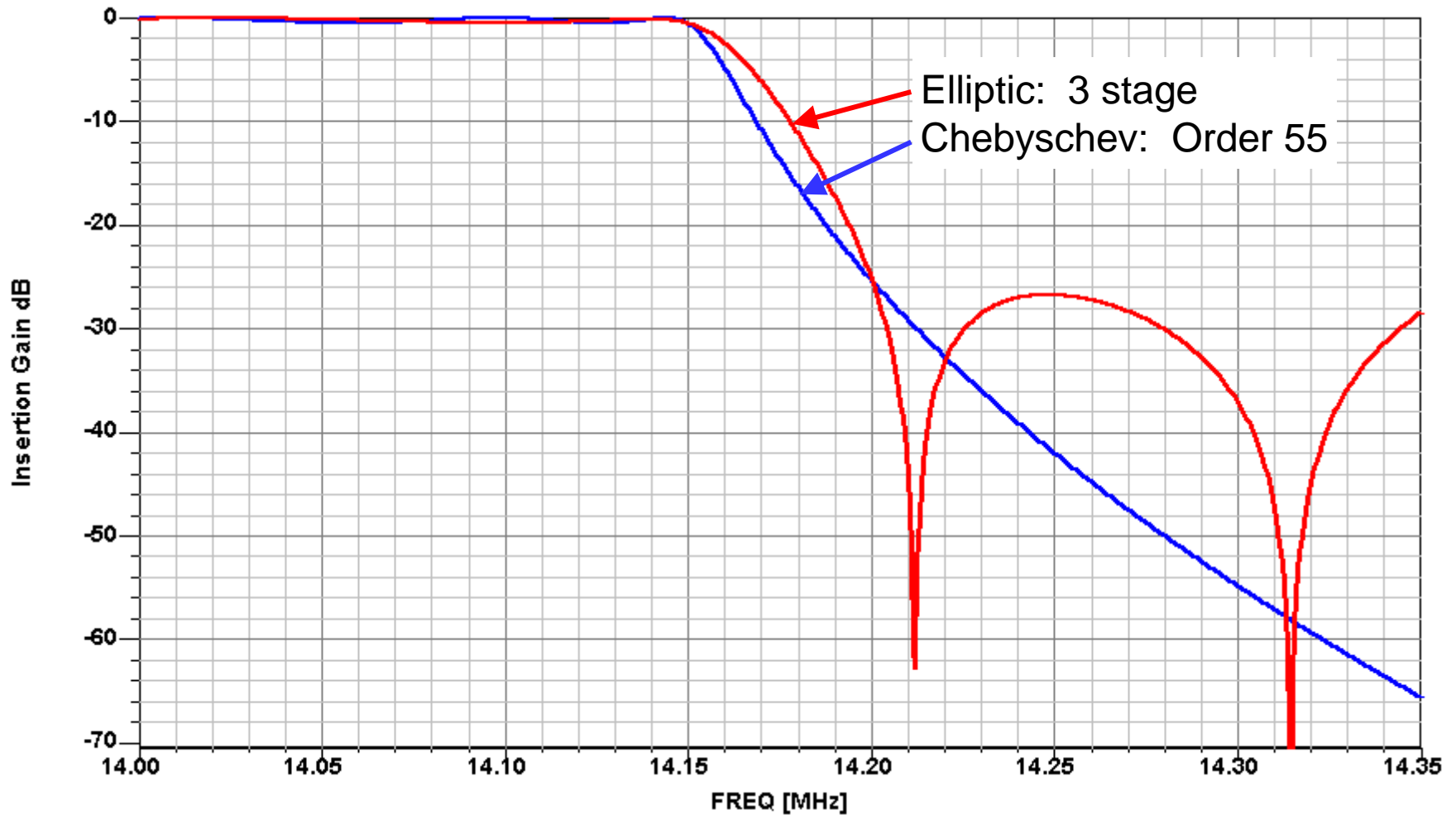
Comparison of Lumped-Element Prototype Filters



Input SWR


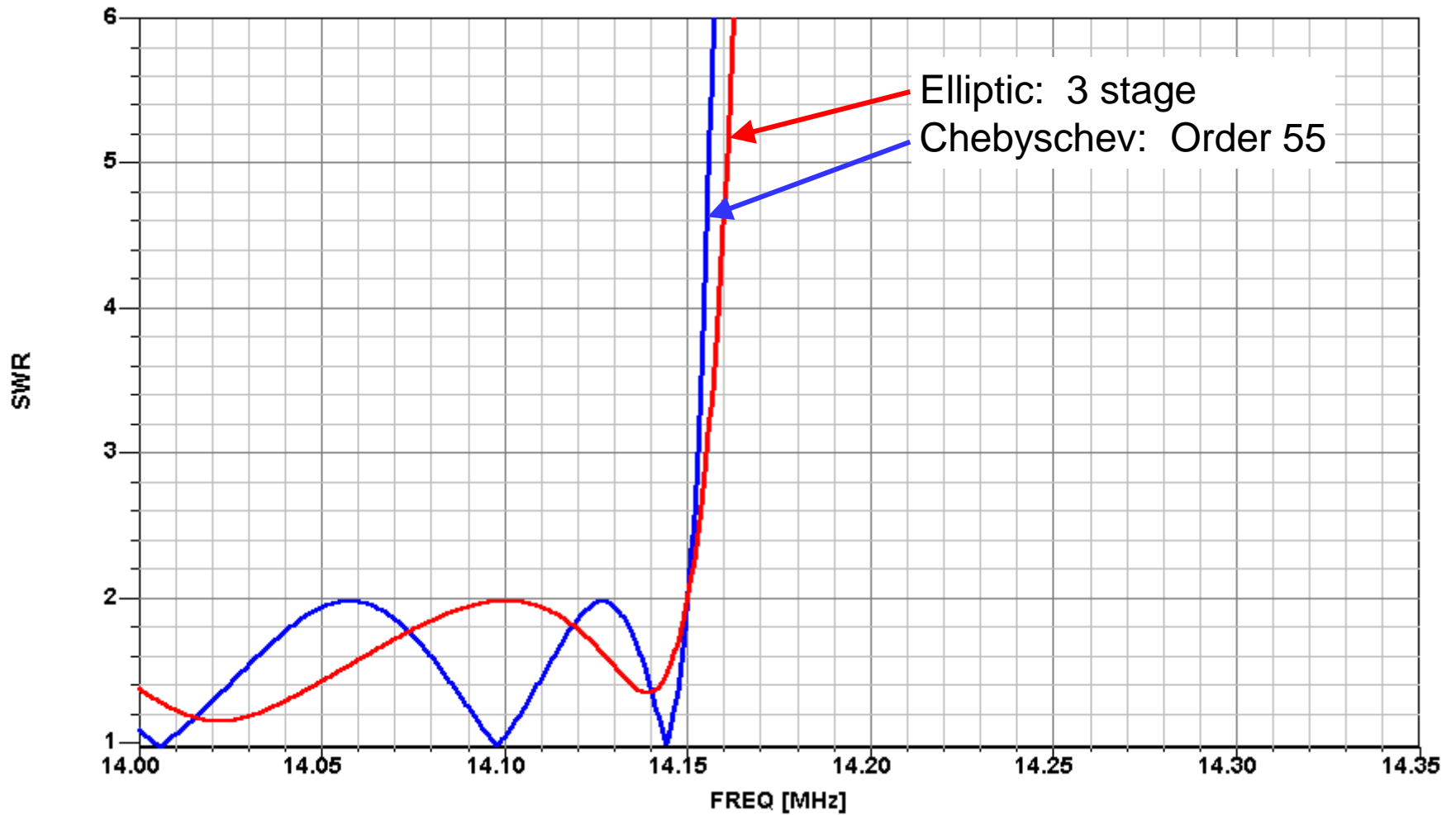


Filter Input Impedance on Smith Chart

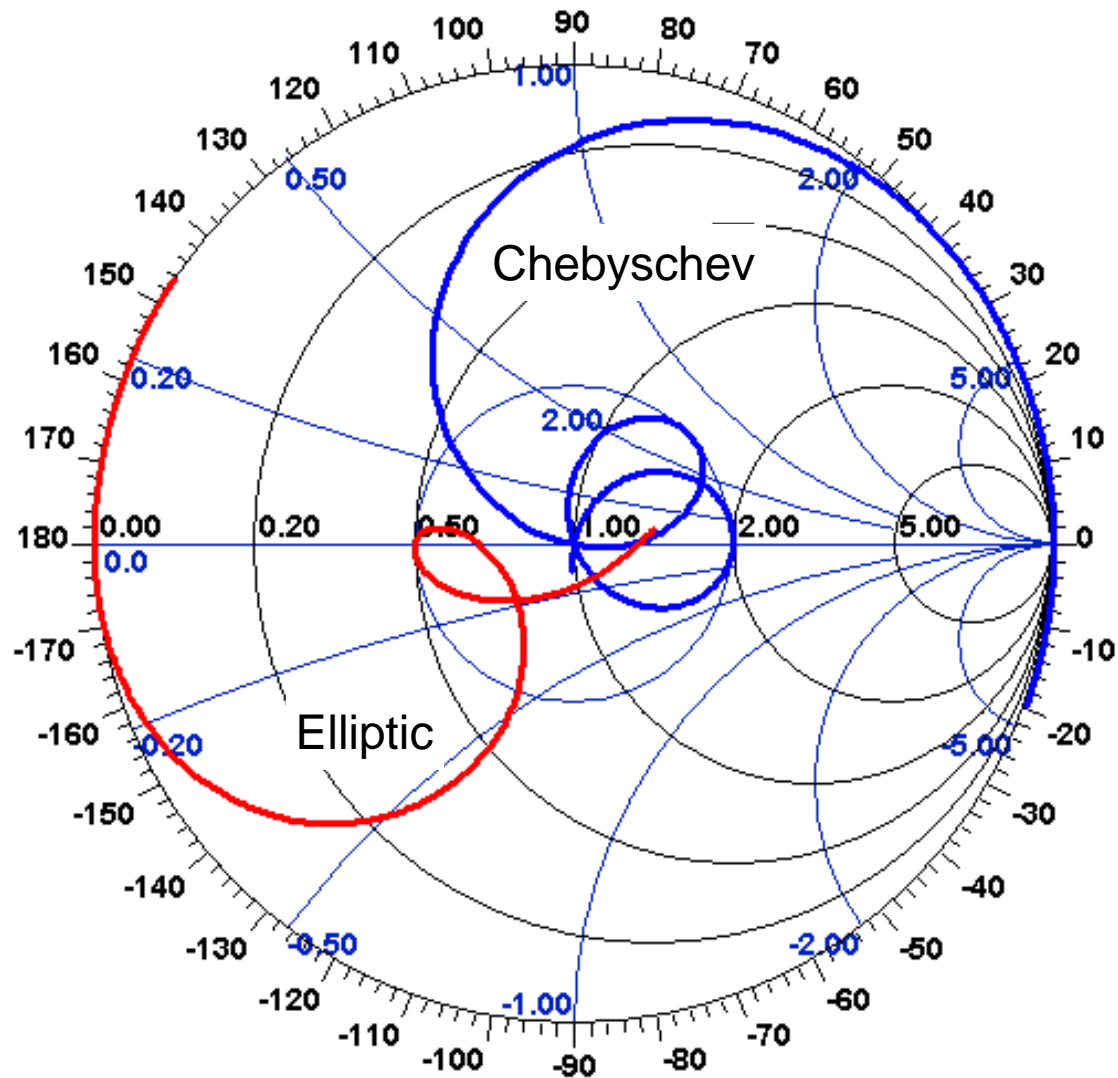


Example 1: 2-Stub Filter Optimized by Serenade SV

20 meters Pass CW, Stop phone

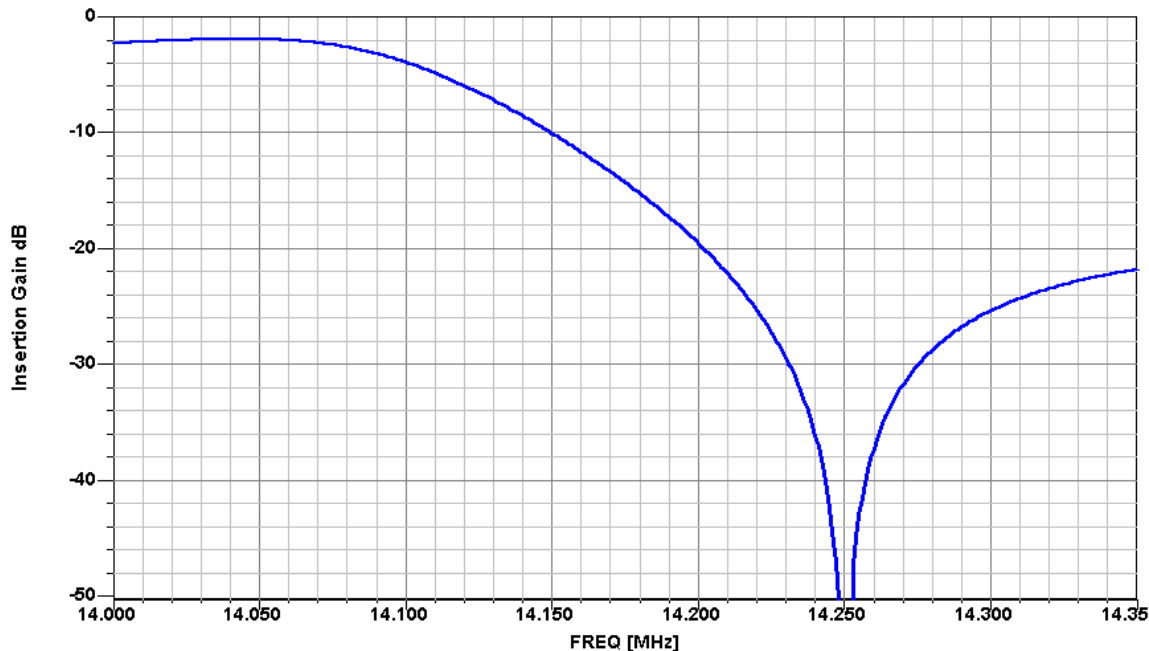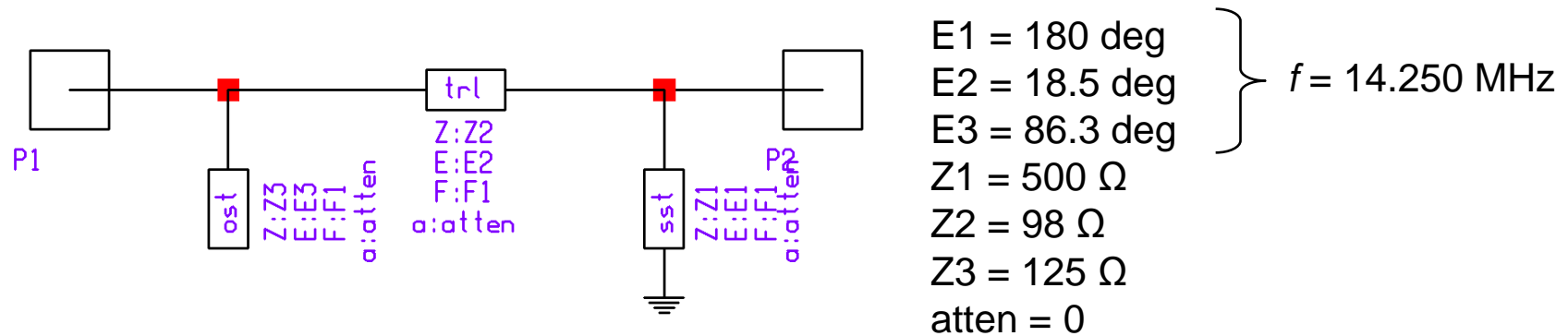

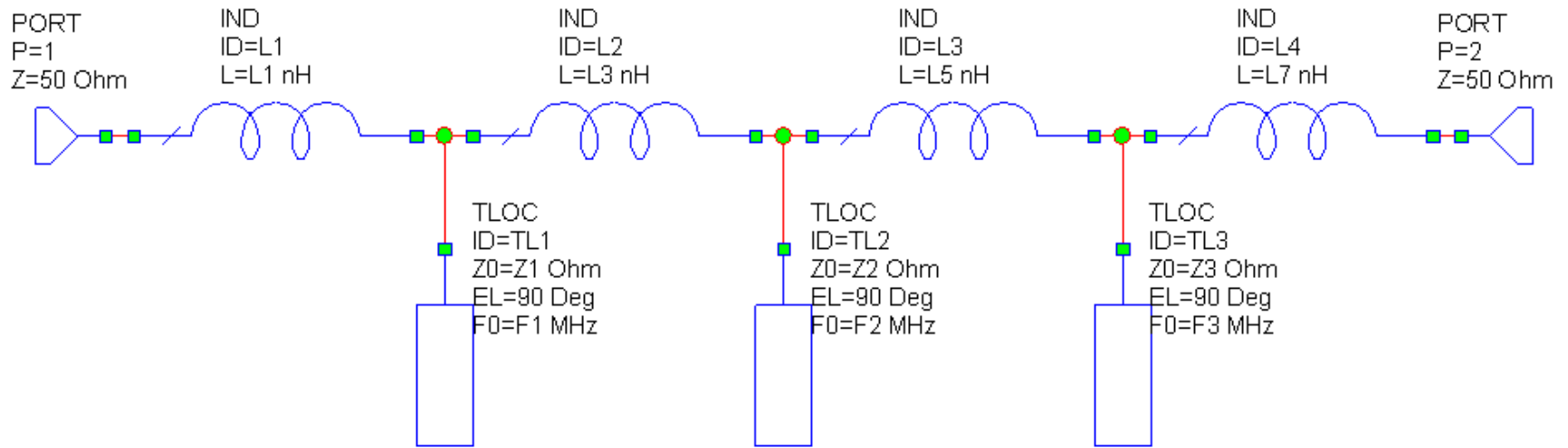Example 2: 3-Stub Filter Found by Microwave Office




F1 = 14.6 MHz
Z1 = 199.6 Ω

F2 = 14.21 MHz
Z2 = 199.2 Ω


F3 = 15.24 MHz
Z3 = 79.21 Ω

L1 = 7.895 nH
L3 = 1130.3 nH
L5 = 126.9 nH
L7 = 163.0 nH

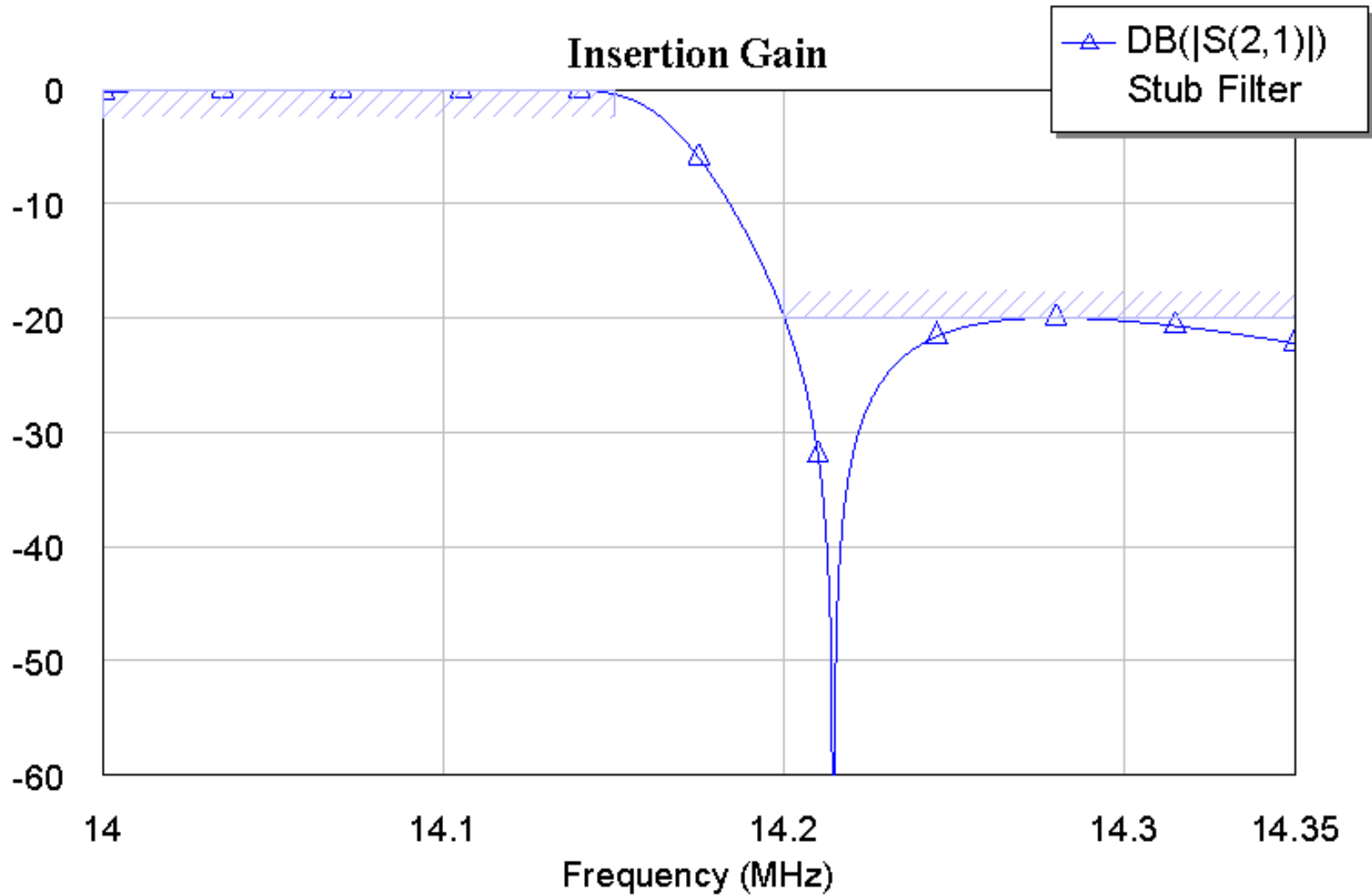
20-Meter CW Pass, Phone Reject Performance




Input SWR

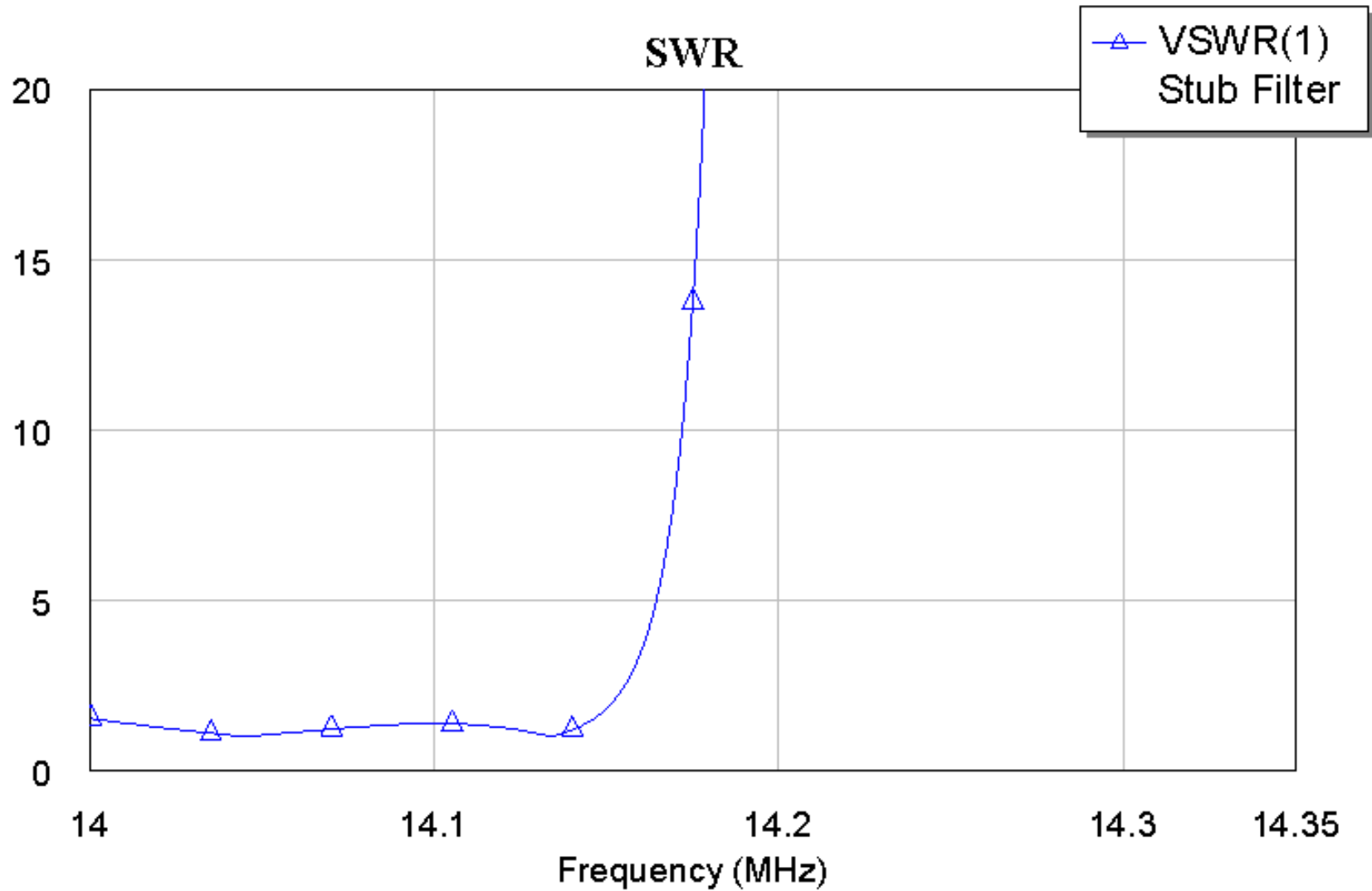

Input Impedance on Smith Chart

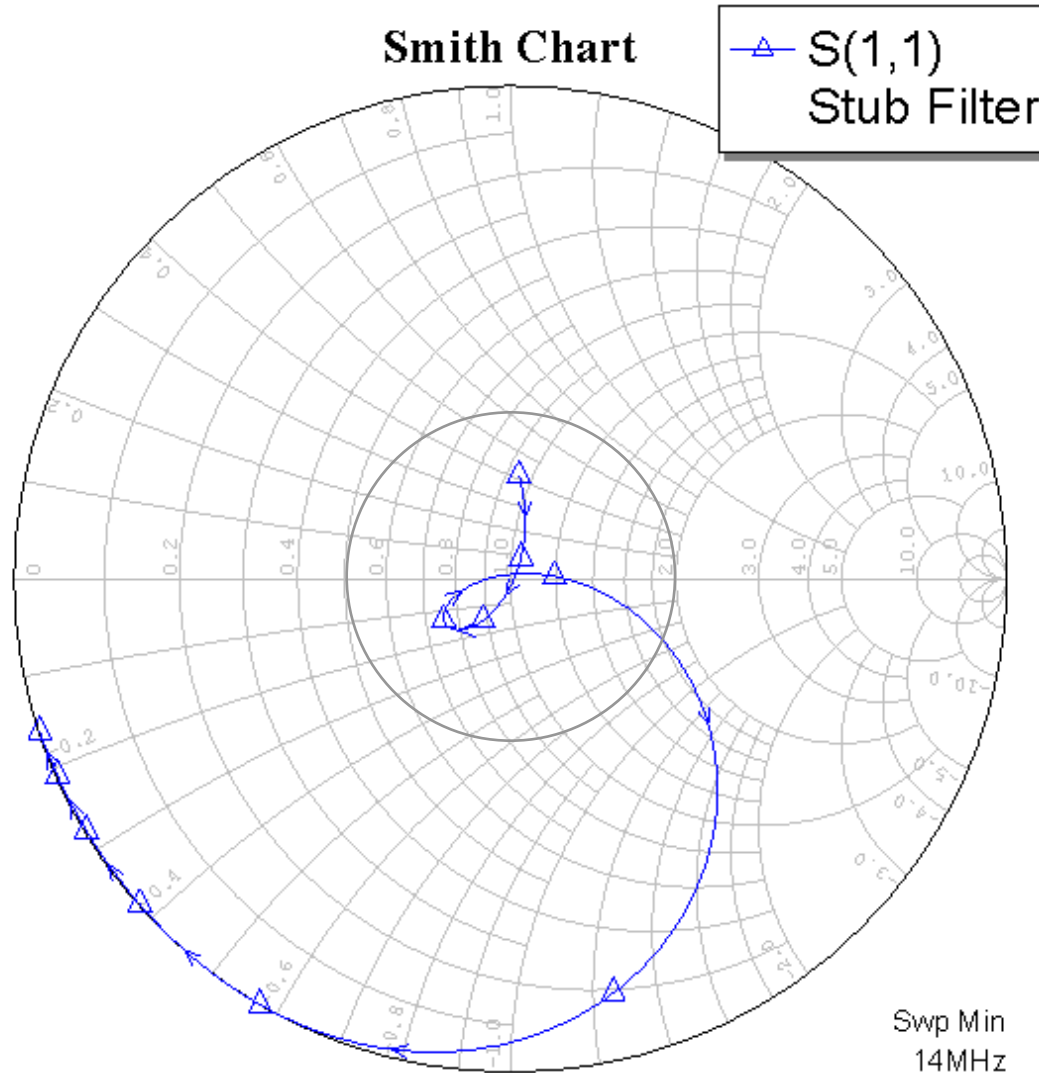

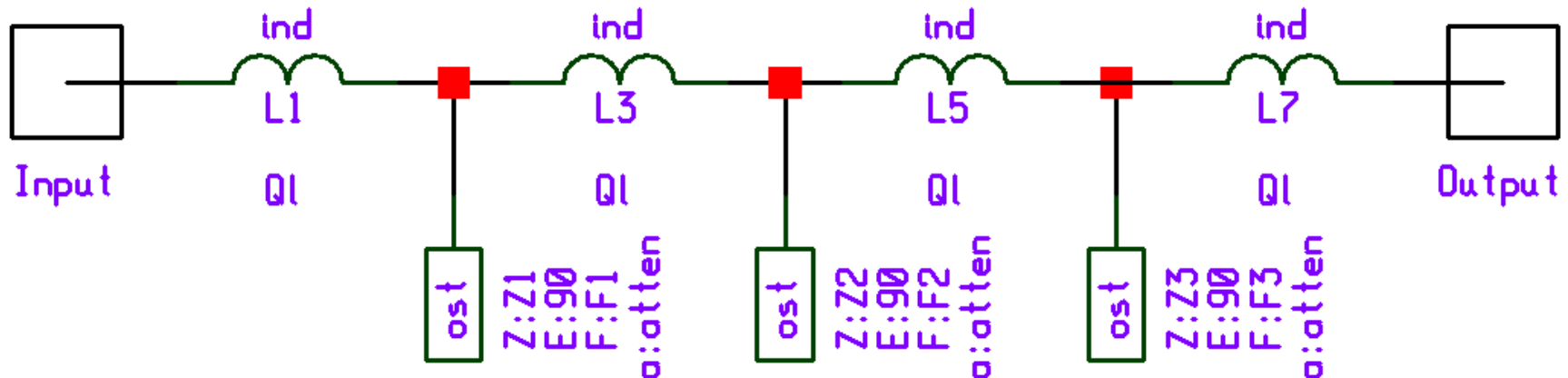
Example 3: 3-Stub Filter w/ Losses, Optimized by ARD




$F1 = 14.537 \text{ MHz}$ $F2 = 14.211 \text{ MHz}$ $F3 = 14.686 \text{ MHz}$
 $Z1 = 200 \ \Omega$ $Z2 = 200 \ \Omega$ $Z3 = 122 \ \Omega$
 $\text{atten} = 0.03 \text{ dB}/\lambda$ $\text{atten} = 0.03 \text{ dB}/\lambda$ $\text{atten} = 0.03 \text{ dB}/\lambda$

$L1 = 5.354 \text{ nH}$
 $L3 = 116.3 \text{ nH}$
 $L5 = 99.21 \text{ nH}$
 $L7 = 4.897 \text{ nH}$
 $Q_L = 200$

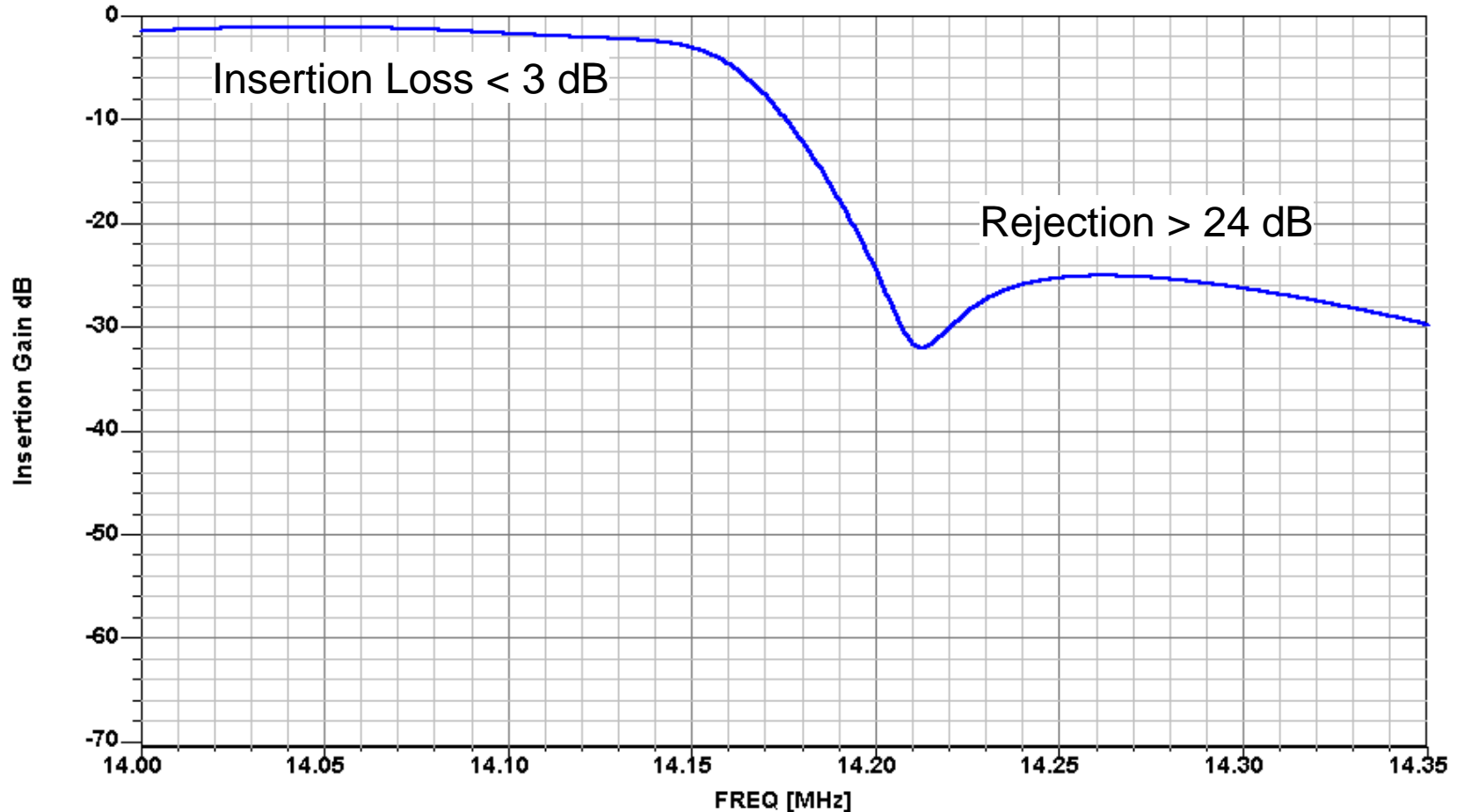
20-Meter CW Pass, Phone Reject Performance



Input SWR

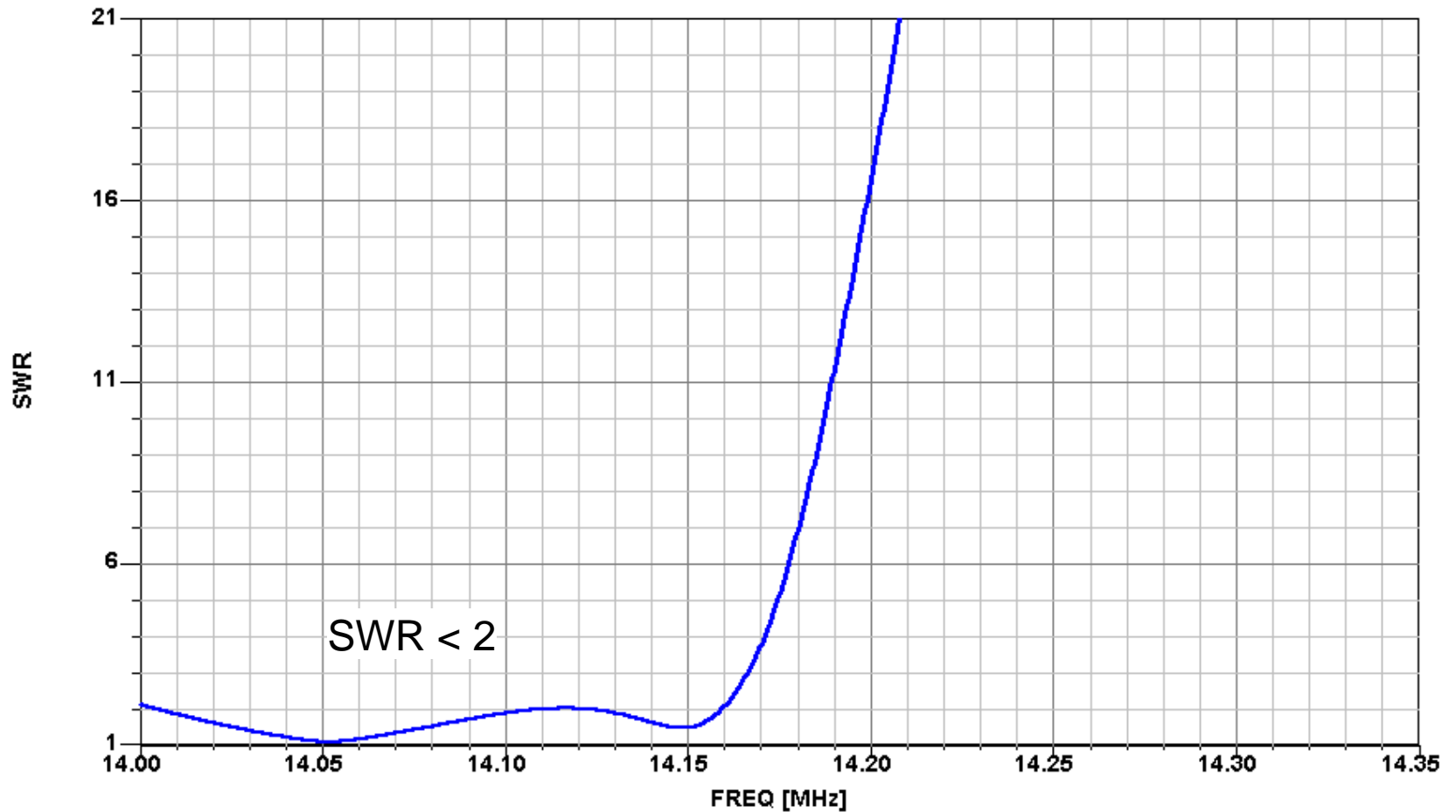

Input Impedance on Smith Chart

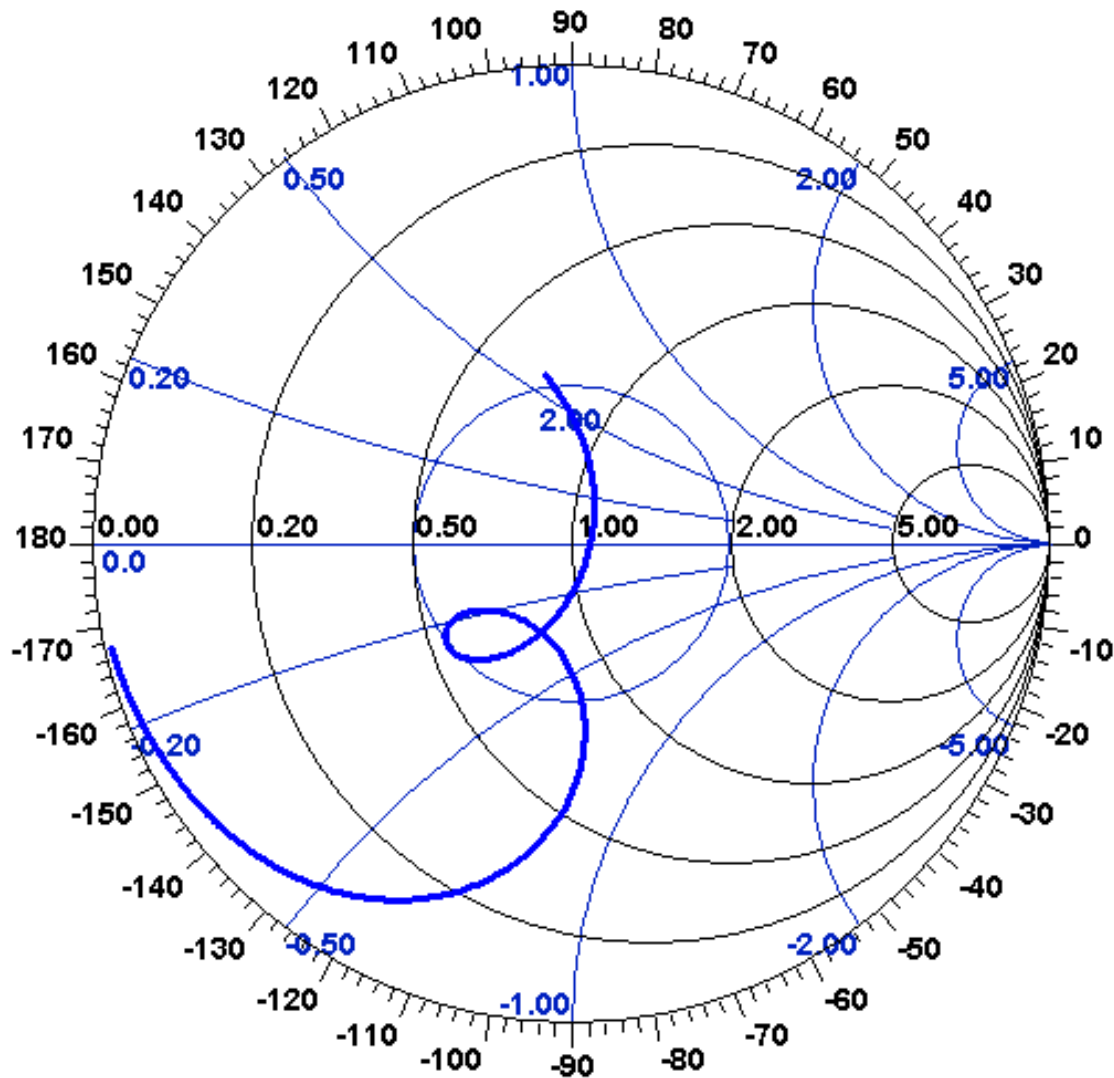

Summary

- Field Day 20-meter sub-band filters were studied
- Neither 1-stub nor 2-stub filters were found that met the performance objectives
- Determined that 3rd order elliptic lumped element filter would work
- A similar 3-stub filter was found that has acceptable performance
 - SWR < 2 in the “pass” sub-band
 - Insertion loss < 3 dB in the “pass” sub-band
 - Rejection > 24 dB in the “stop” sub-band
- Stubs require ~ $50.3 \times v.f.$ feet of line in two characteristic impedances

Determined by losses



Determined by filter order

Sub-Harmonic Stub Filters

Sub-Harmonic Stub Filters

- **Pass and stop frequencies can be placed arbitrarily close together by using electrically-long stubs**
- **Set the stub's fundamental frequency low enough such that the pass and stop frequencies are even-odd or odd-even harmonics of the fundamental**
- **The method can be extended to three frequencies, where each is a pass or stop, provided the frequencies are rationally related and relatively prime**
- **This technique requires long line lengths and so is best suited to UHF frequencies**
- **The following example shows a sub-harmonic stub for the 20-meter sub-band filter problem**
- **Long stub length makes the solution impractical for HF, but method is educational**

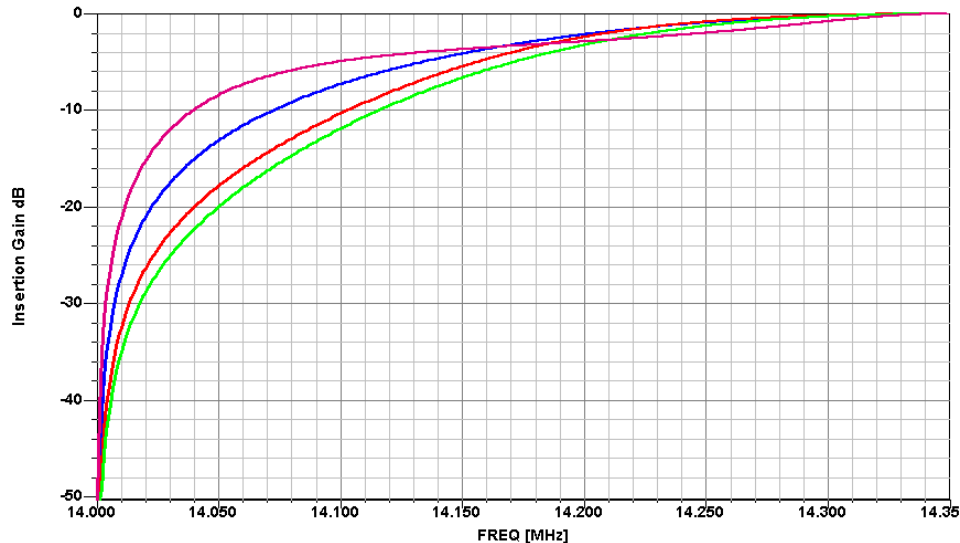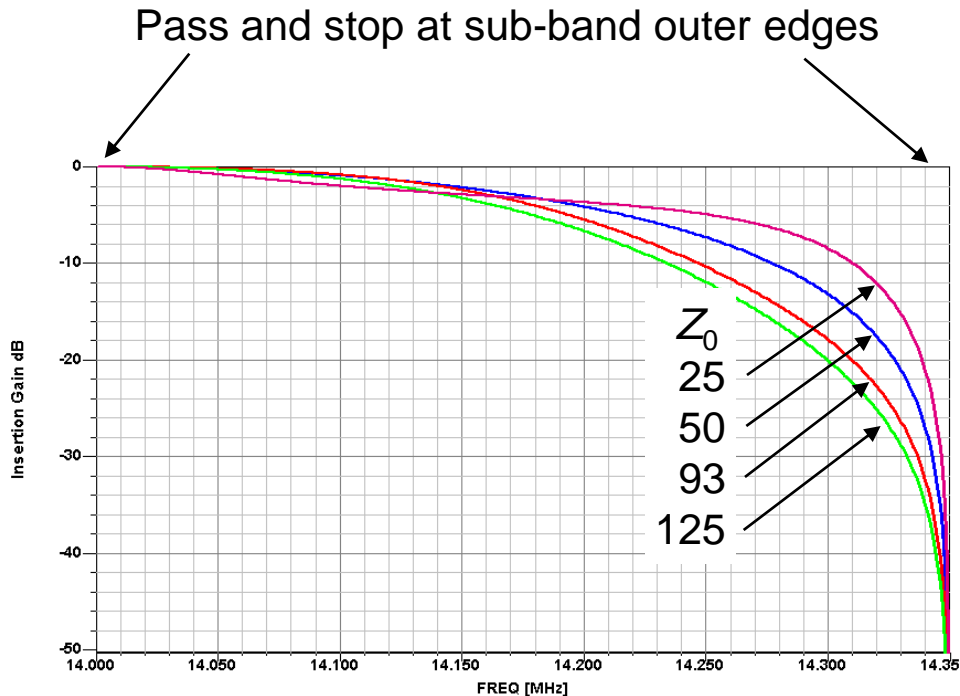Example 4: Sub-Band Filters via a Sub-Harmonic Stub



Open-circuit stubs pass even harmonics

Fundamental frequency 350 kHz

$$l = \lambda / 4 = 703 \text{ ft.} \times \text{v.f.}$$

Pass CW sub-band (harmonic 40)

Stop phone sub-band (harmonic 41)

Short-circuit stubs pass odd harmonics



Fundamental frequency 350 kHz

$$l = \lambda / 4 = 703 \text{ ft.} \times \text{v.f.}$$

Pass phone sub-band (harmonic 40)

Stop CW sub-band (harmonic 41)

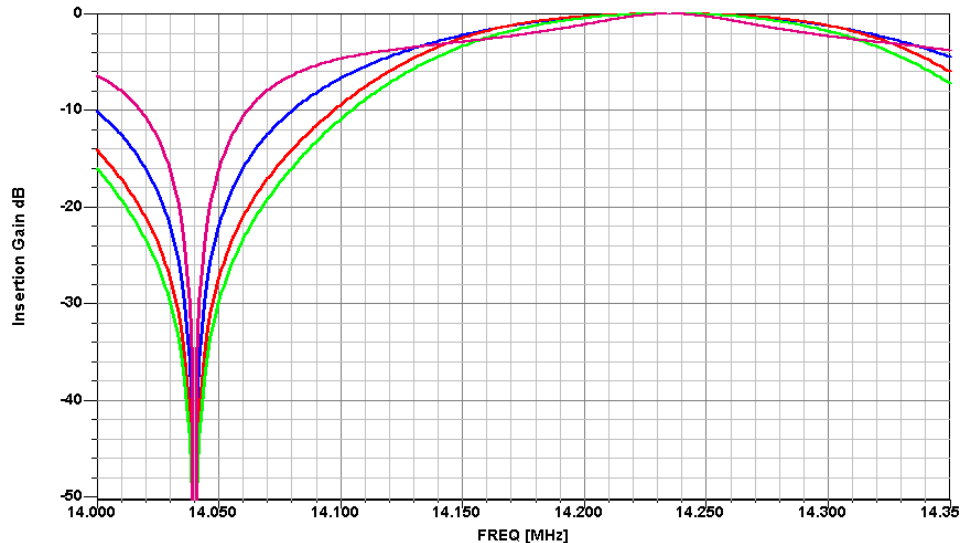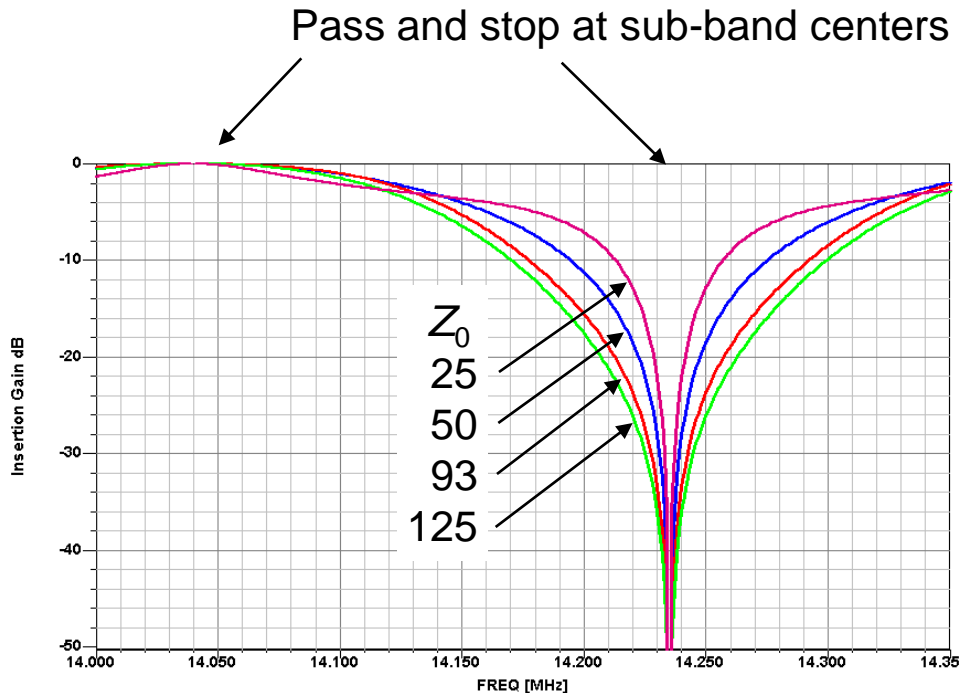Example 5: Decreasing Pass-to-Stop by a Longer Stub



Open-circuit stubs pass even harmonics

Fundamental frequency 195 kHz

$$l = \lambda / 4 = 1,262 \text{ ft.} \times \text{v.f.}$$

Pass CW sub-band (harmonic 72)

Stop phone sub-band (harmonic 73)

Short-circuit stubs pass odd harmonics

Fundamental frequency 195 kHz

$$l = \lambda / 4 = 1,262 \text{ ft.} \times \text{v.f.}$$

Pass phone sub-band (harmonic 72)


Stop CW sub-band (harmonic 73)

Reflectionless Stub Filters

Reflectionless Filters

- **Filter by absorption instead of reflection**
- **Can be viewed as a lossless 3-port or lossy 2-port network**
- **2-port implementation requires internal resistor**
- **3-port implementation gives diplexer function**
 - Even harmonic bands couple to one port
 - Odd harmonic bands couple to the other port
 - Ports must be terminated with matched impedances
- **Applications**
 - Connect a multiband transmitter to two antennas on different bands without using an antenna switch
 - Connect two transceivers to a single antenna on different bands

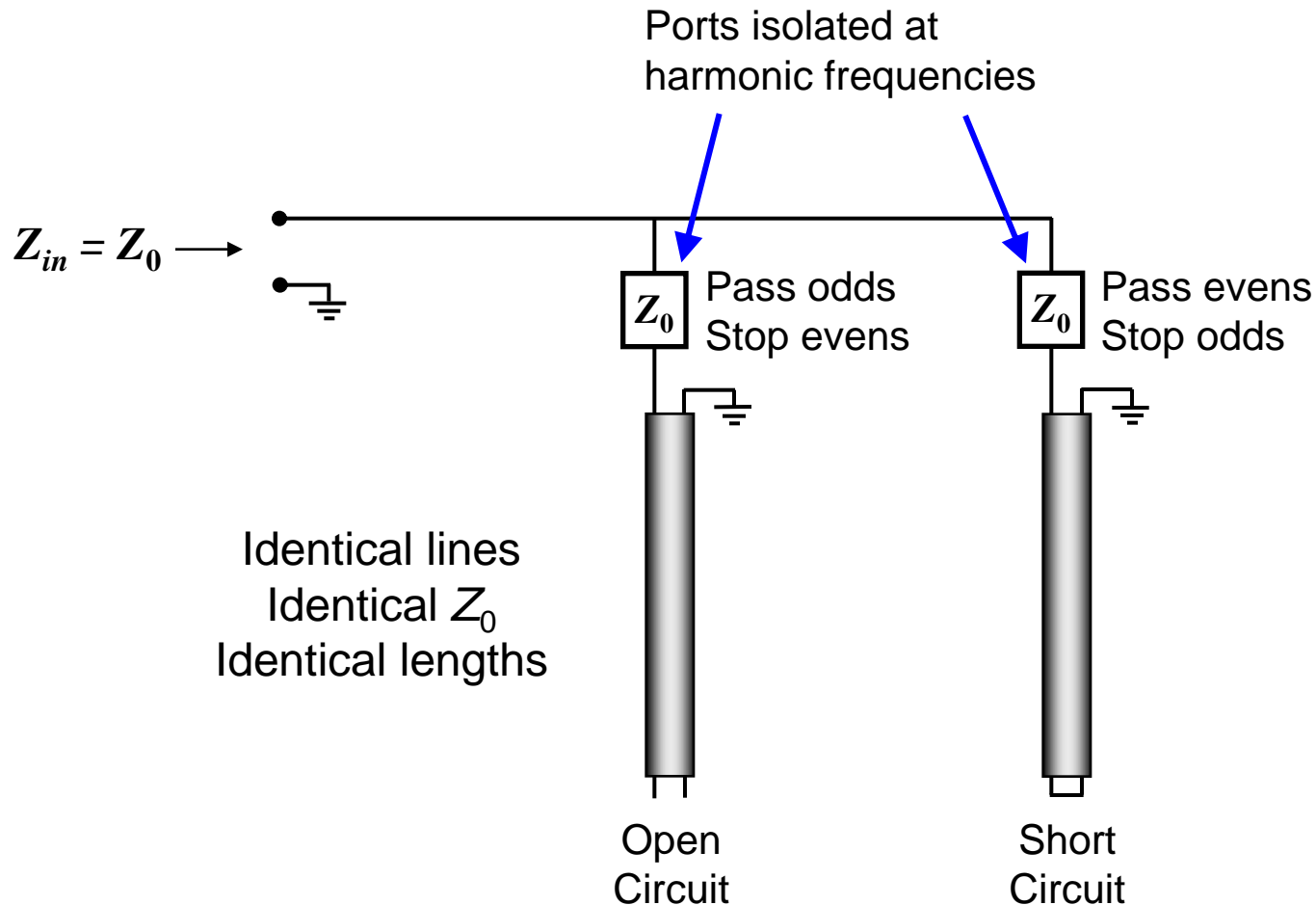
Reflectionless Filter Using Complementary Stubs




Complementary stubs provide constant input resistance and output port isolation at multiple pass and stop frequencies.

A 50-Ω Reflectionless Stub Filter


Pass even harmonics
Stop odd harmonics

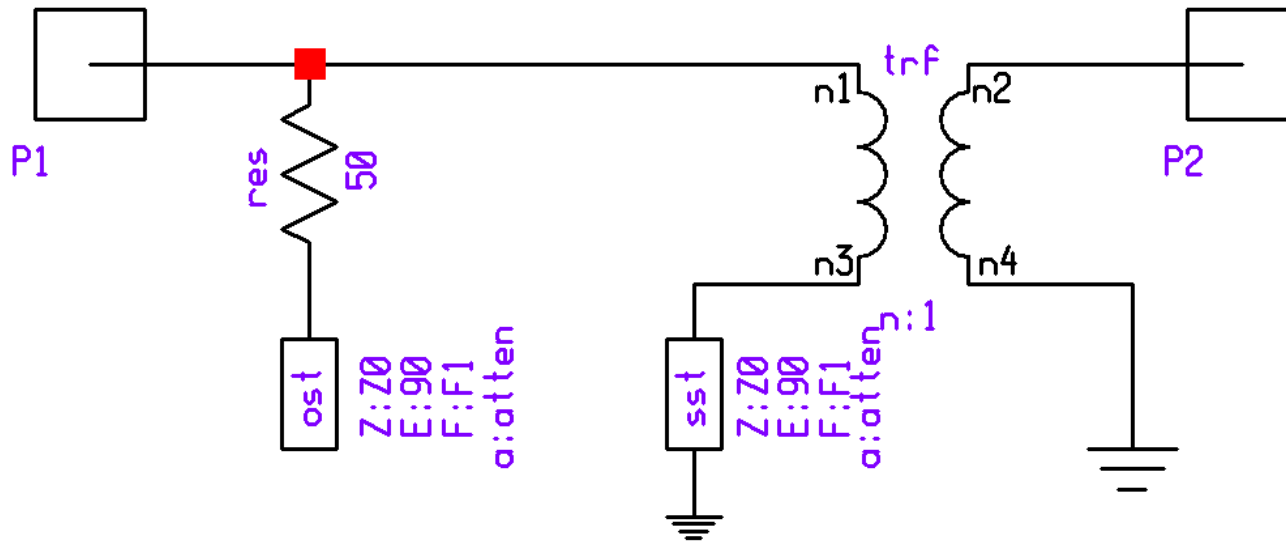

Insertion Gain from Input to Output Port

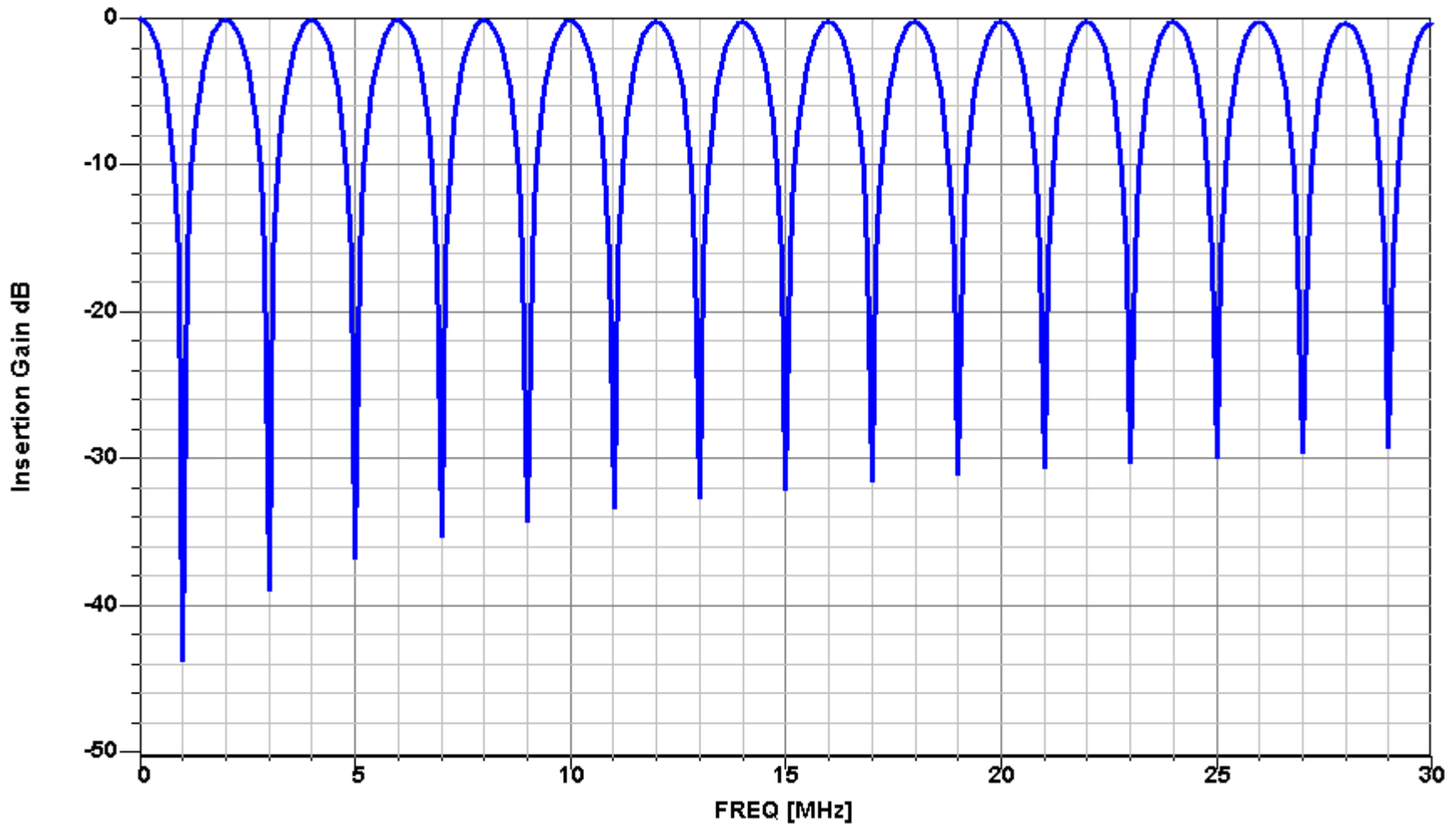

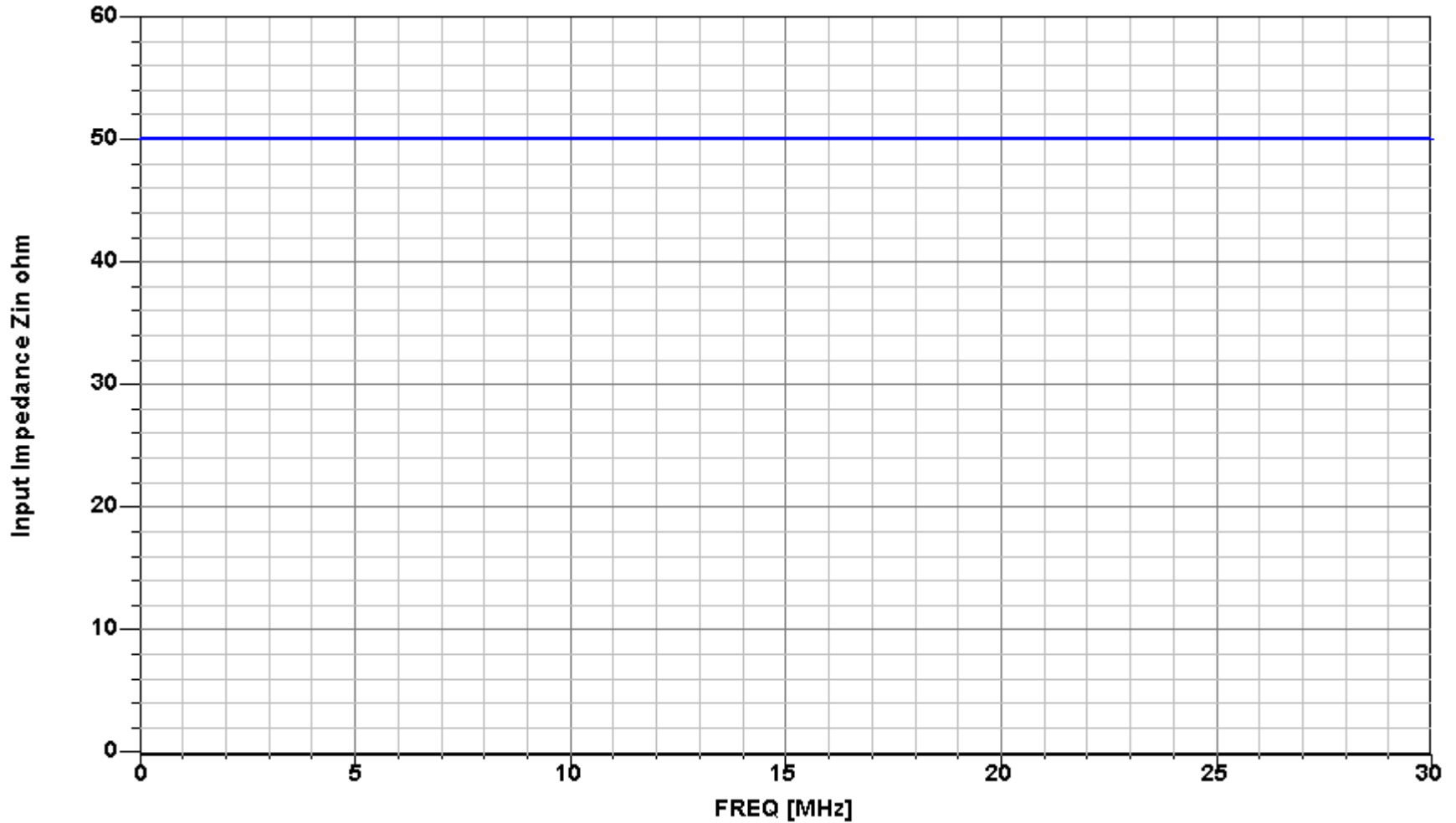Input Impedance of 50-Ω Terminated Filter



Commensurate Filters

Paul Irving Richards, 1923-1978



Courtesy of Harvard University

Commensurate Filters

- **Commensurate filters:** all transmission line sections have lengths that are integer multiples of a unit length l
- **Commensurate stub filters** use transmission line stubs in place of capacitors and inductors
- **Starting from a lumped-element prototype, replace all inductors and capacitors with short stubs, setting inductance L and capacitance C by the choice of integer n and Z_0 for each stub**
- **For inductors, use short-circuited stubs of length nl**

$$L = \frac{Z_0 n l}{c} = Z_0 \tau$$

- **For capacitors, use open-circuited stubs of length nl**

$$C = \frac{n l}{Z_0 c} = \frac{\tau}{Z_0}$$

Facts about Commensurate Stub-Resistor Networks

- **P.I. Richards's (1948) transformation extended lumped-element network theories of realizability, synthesis, and filtering to a class of transmission line networks**
 - Stub-resistor networks: no capacitors or inductors
 - Synthesis: Brune, Bott-Duffin, Darlington, etc.
 - Filters: Butterworth, Chebyshev, Elliptic, etc.
- **Commensurate filters act like lumped-element filters from *d-c* up to a given frequency, above which the frequency response repeats periodically**

Re-Entrant Transmission Line Filters


Andrew Alford, 1904-1992



Courtesy of IEEE


Re-Entrant Filter – Type 1

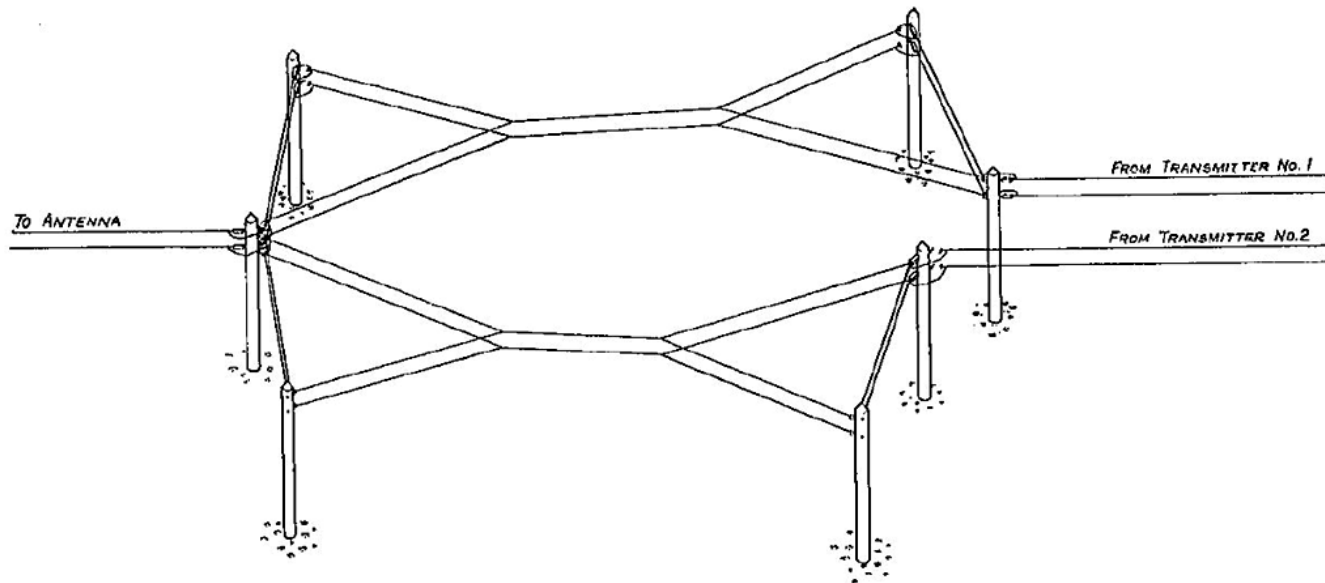- Introduced by A. Alford in 1939
- Transmission lines function as 2-port devices with both ends of the line connected into the network




Re-entrant diplexer, Mackay Radio and Telegraph Co., circa 1939

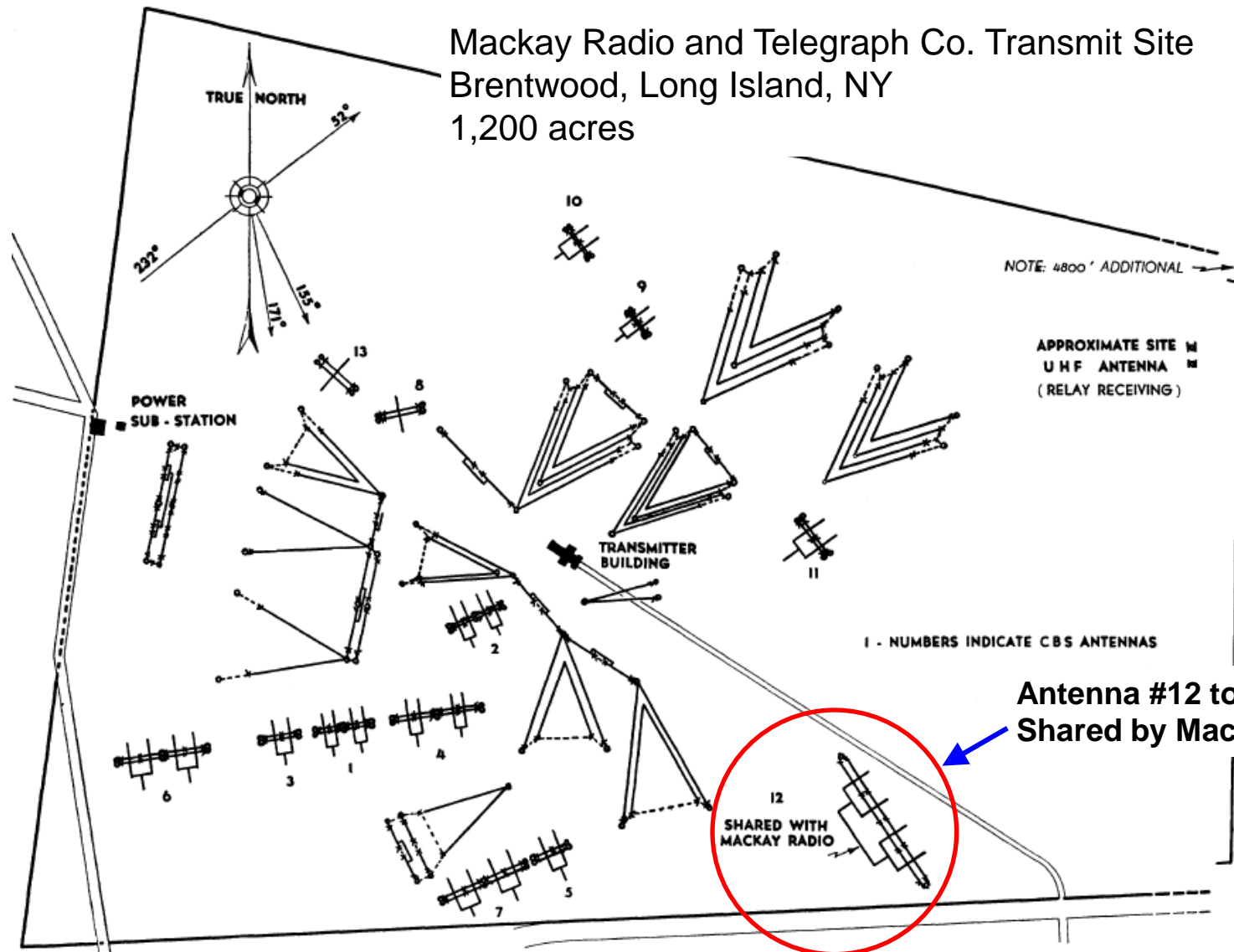CBS WCBX & WCRC Antennas, Brentwood, Long Island




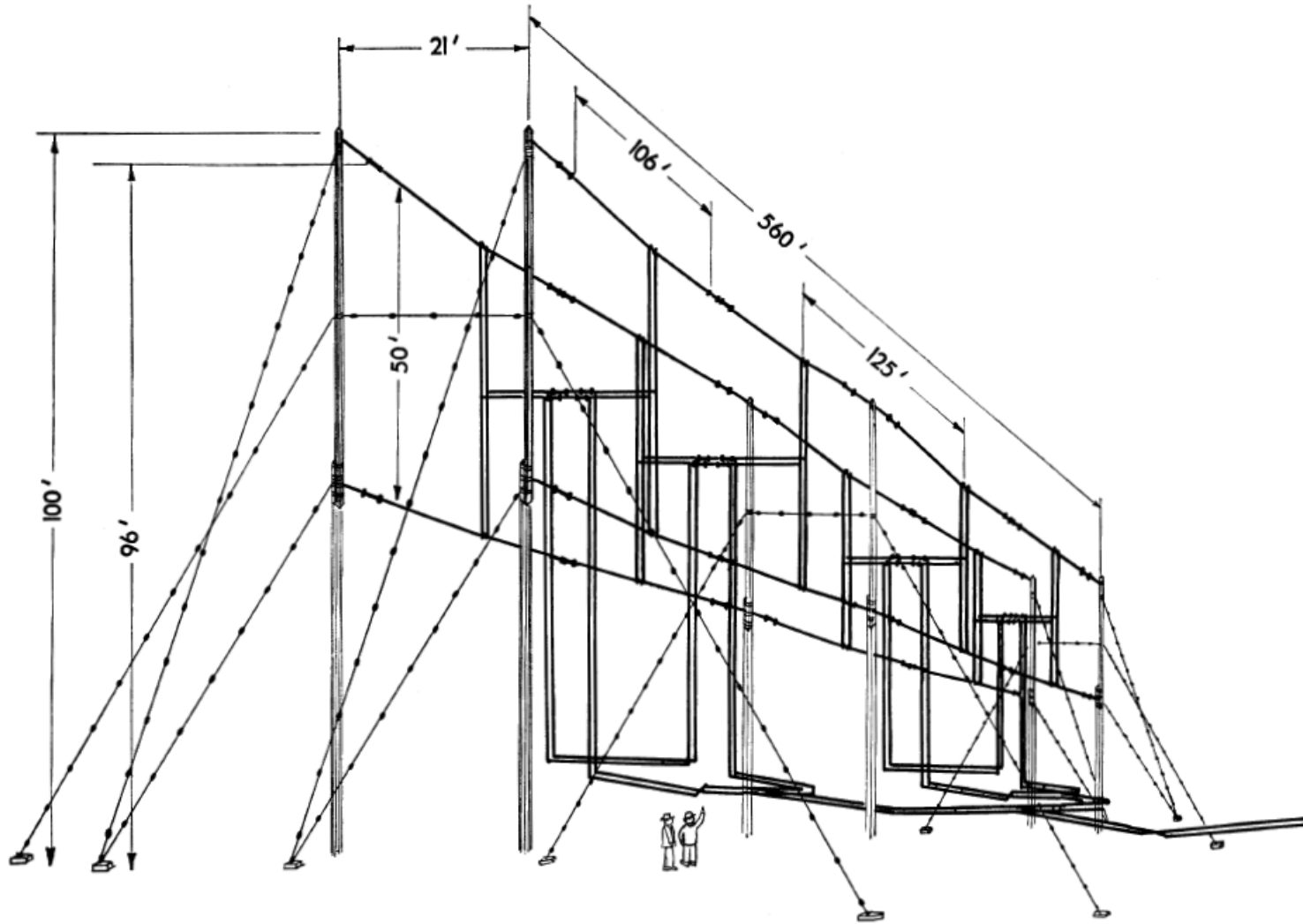Antenna No. 7 – Antenna No. 12's Little Brother





A.B. Chamberlain, "CBS International Broadcast Facilities," *Proc. IRE*, March 1942

Technical Specifications of Mackay/CBS Diplexer

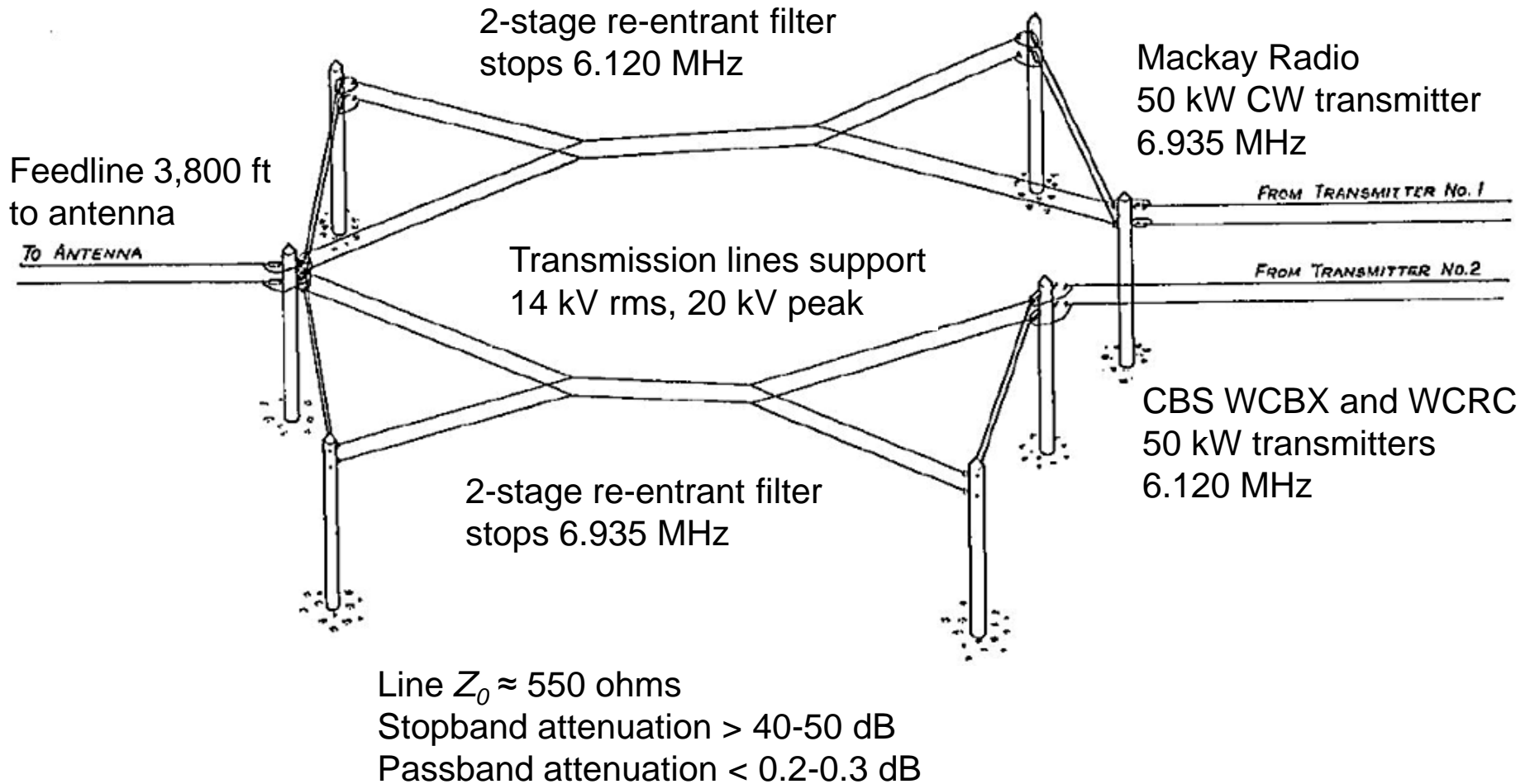


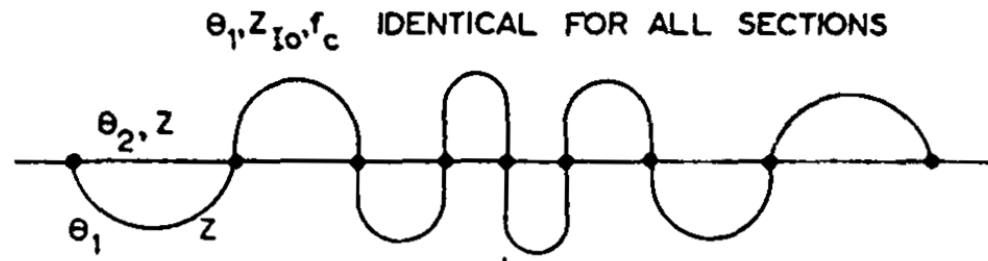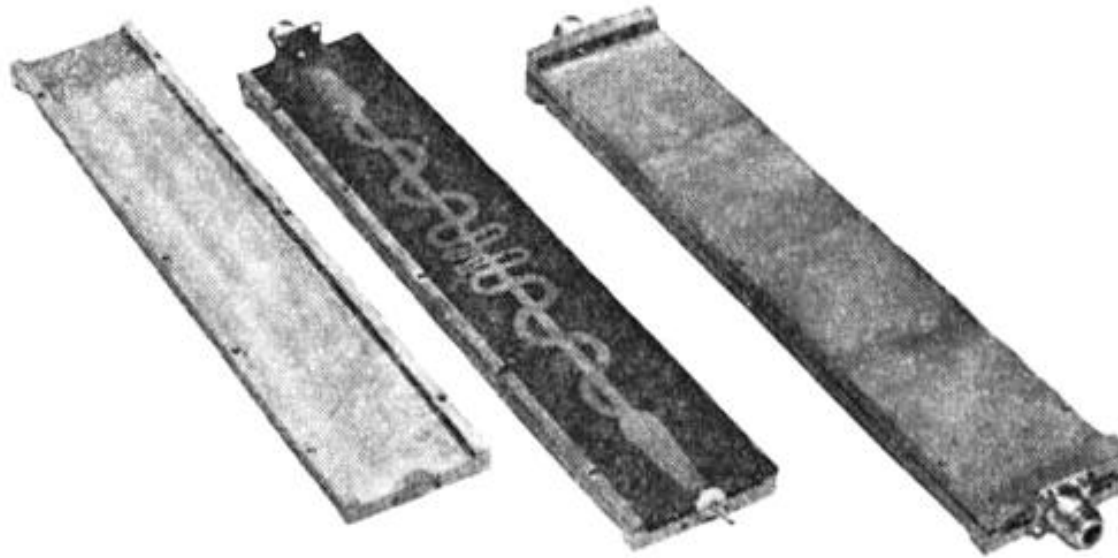Example 2: 6-Section Tapered Re-Entrant LPF




J.M.C. Dukes, "Re-entrant Transmission Line Filter Using Printed Conductors," *Proc. IEE*, Nov. 1957

Example 3: The Q3Q-PS Balun

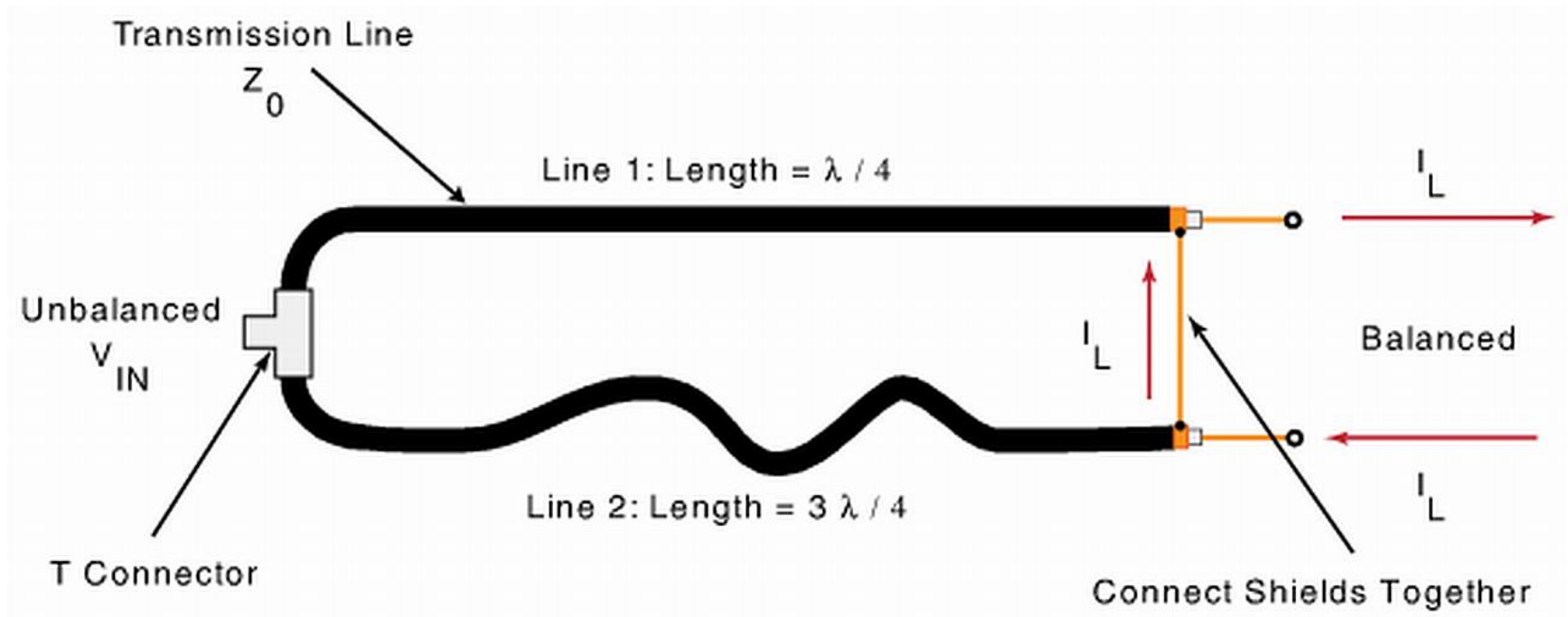


H.W. Silver, N0AX, "Experiment 116: The Quarter-Three-Quarter Wave Balun," QST, Sept. 2012


The Q3Q-PS Balun Schematic in Serenade

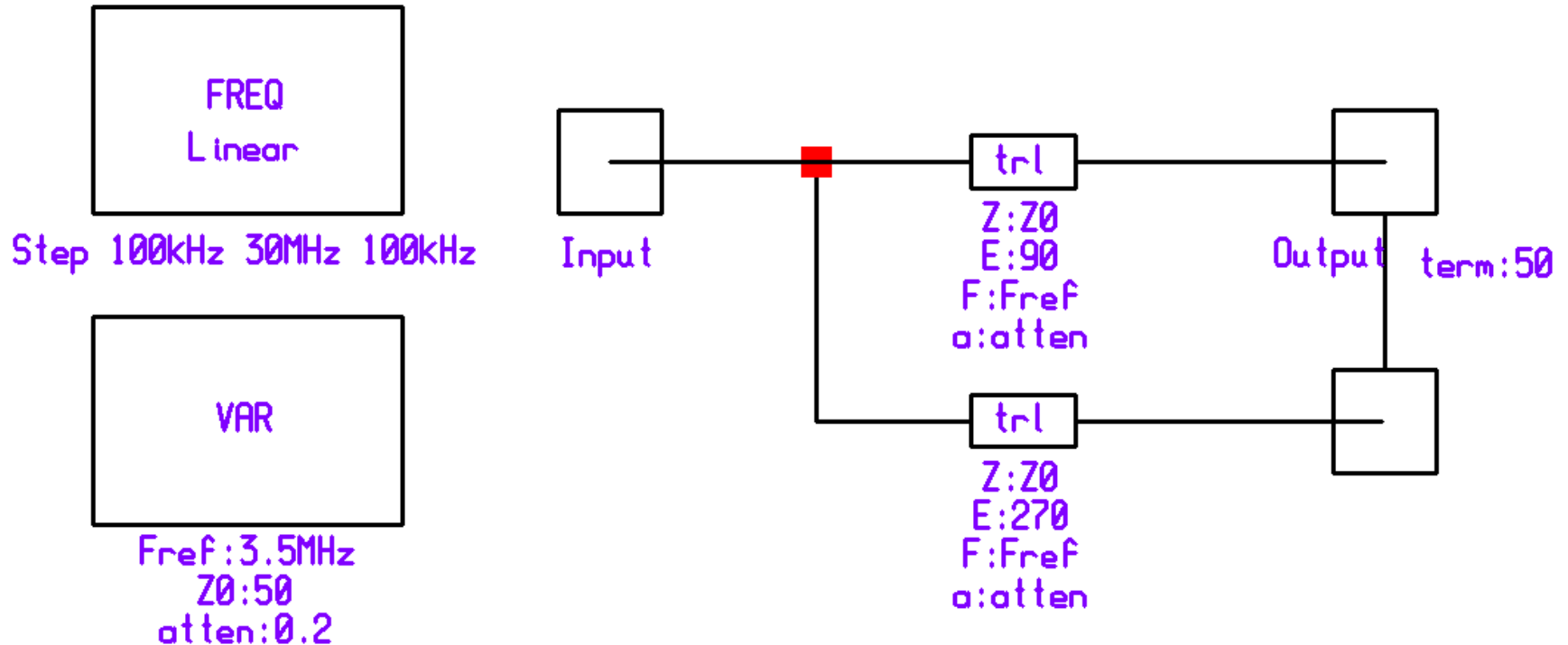

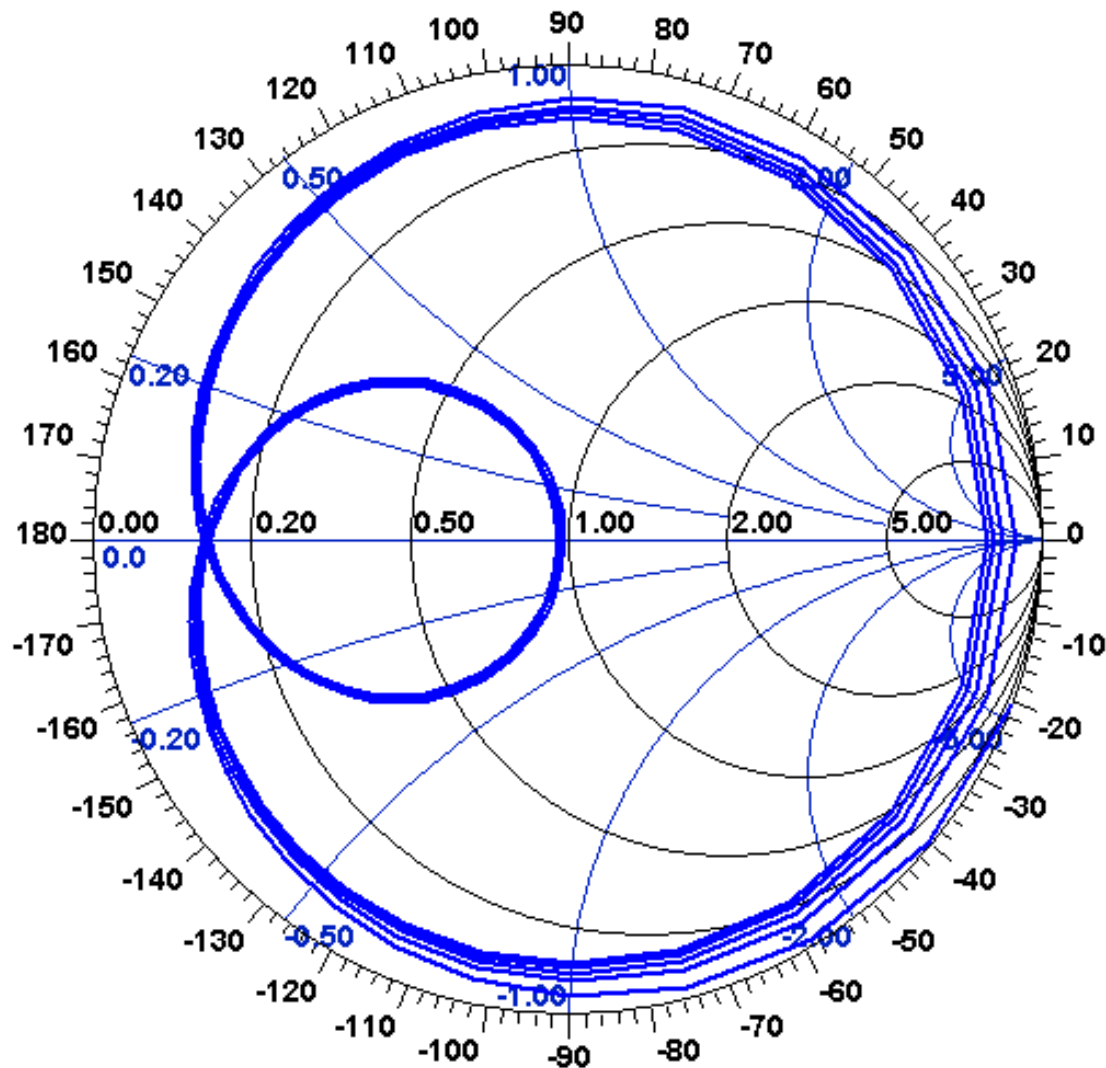
Q3Q-PS Balun Input Impedance on Smith Chart




Q3Q-PS Balun Input SWR vs Frequency

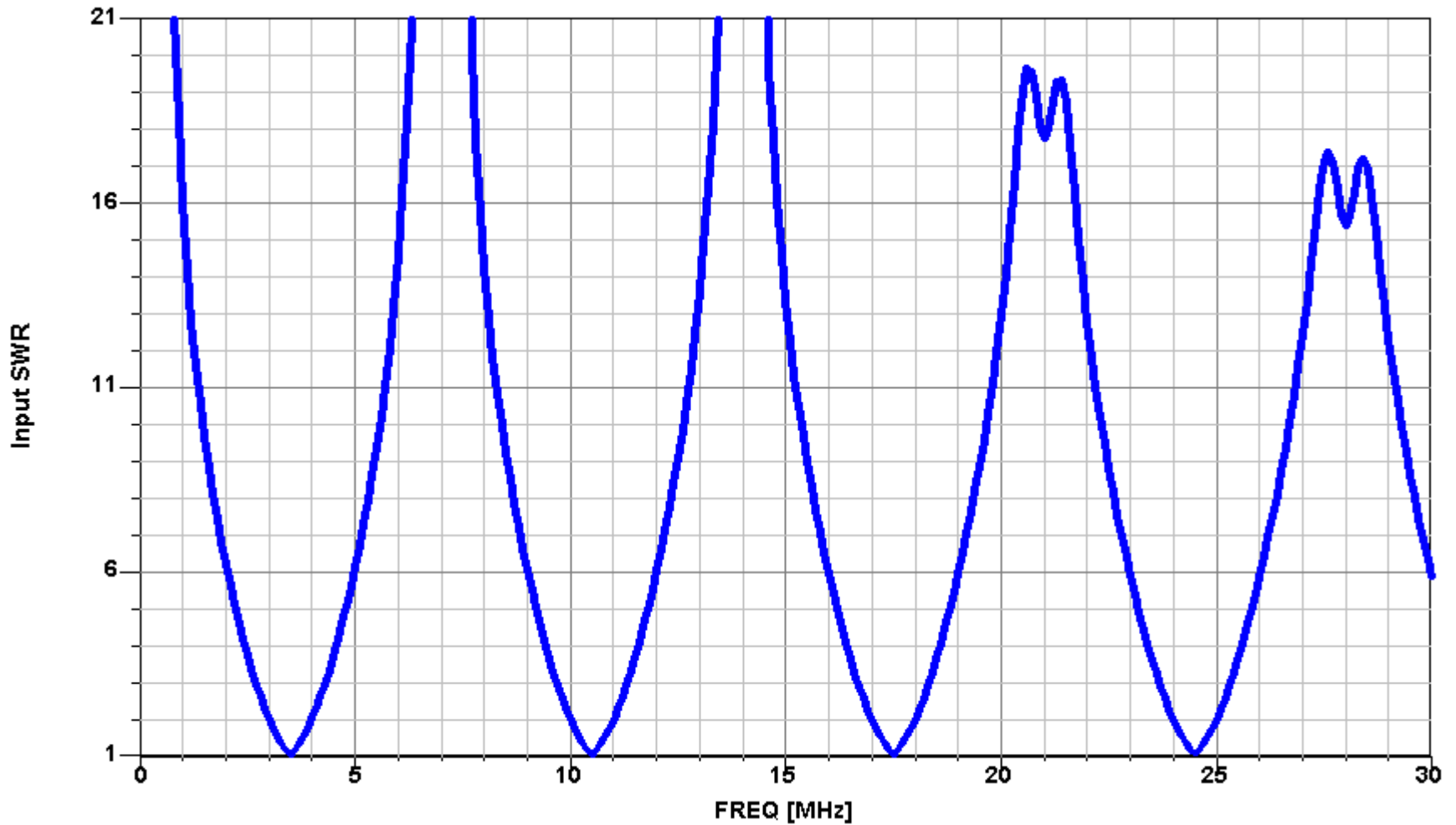


Q3Q Balun Insertion Gain vs Frequency

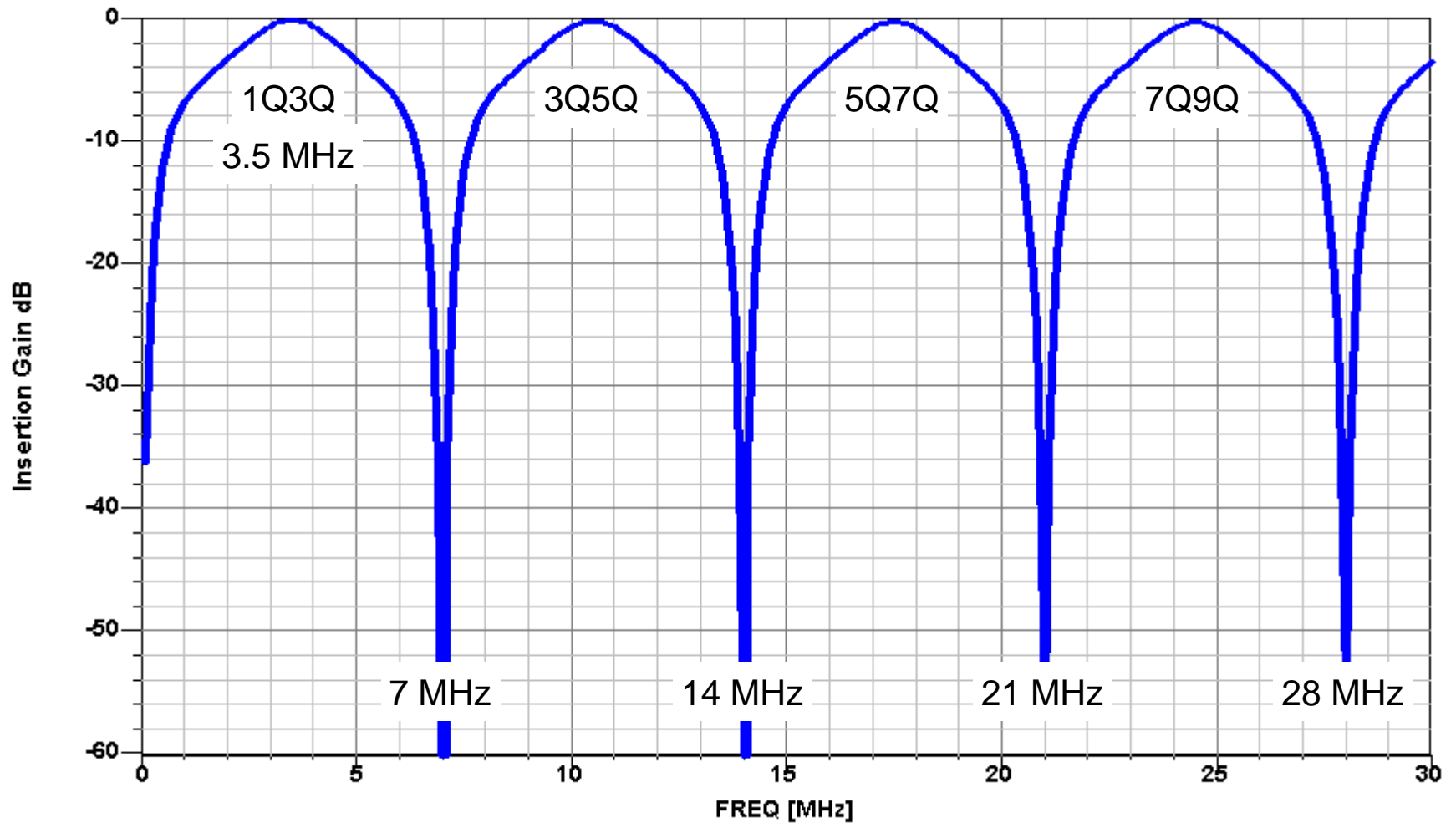

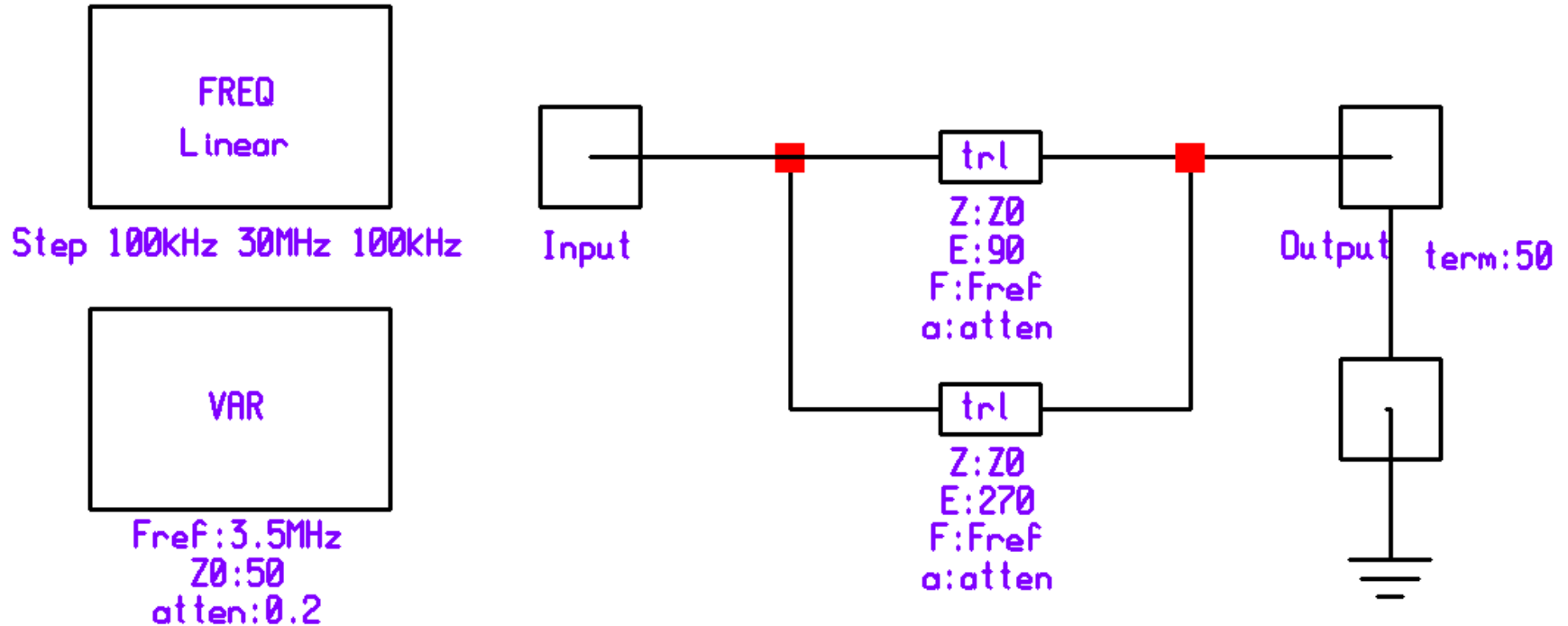
Example 4: Q3Q-PP, Lines Paralleled at Output



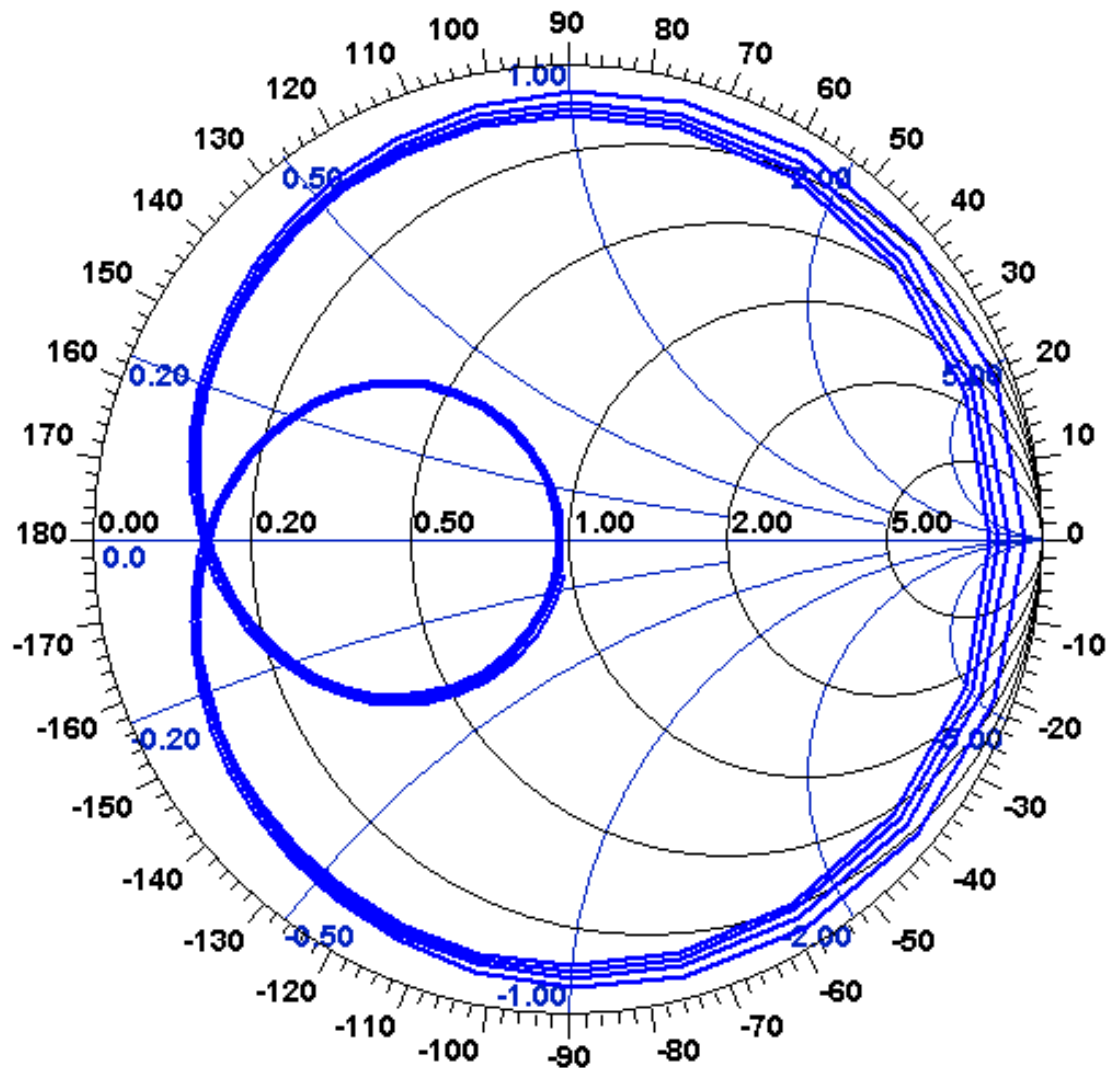
Q3Q-PP Filter Input Impedance on Smith Chart



Q3Q-PP Filter Input SWR vs Frequency


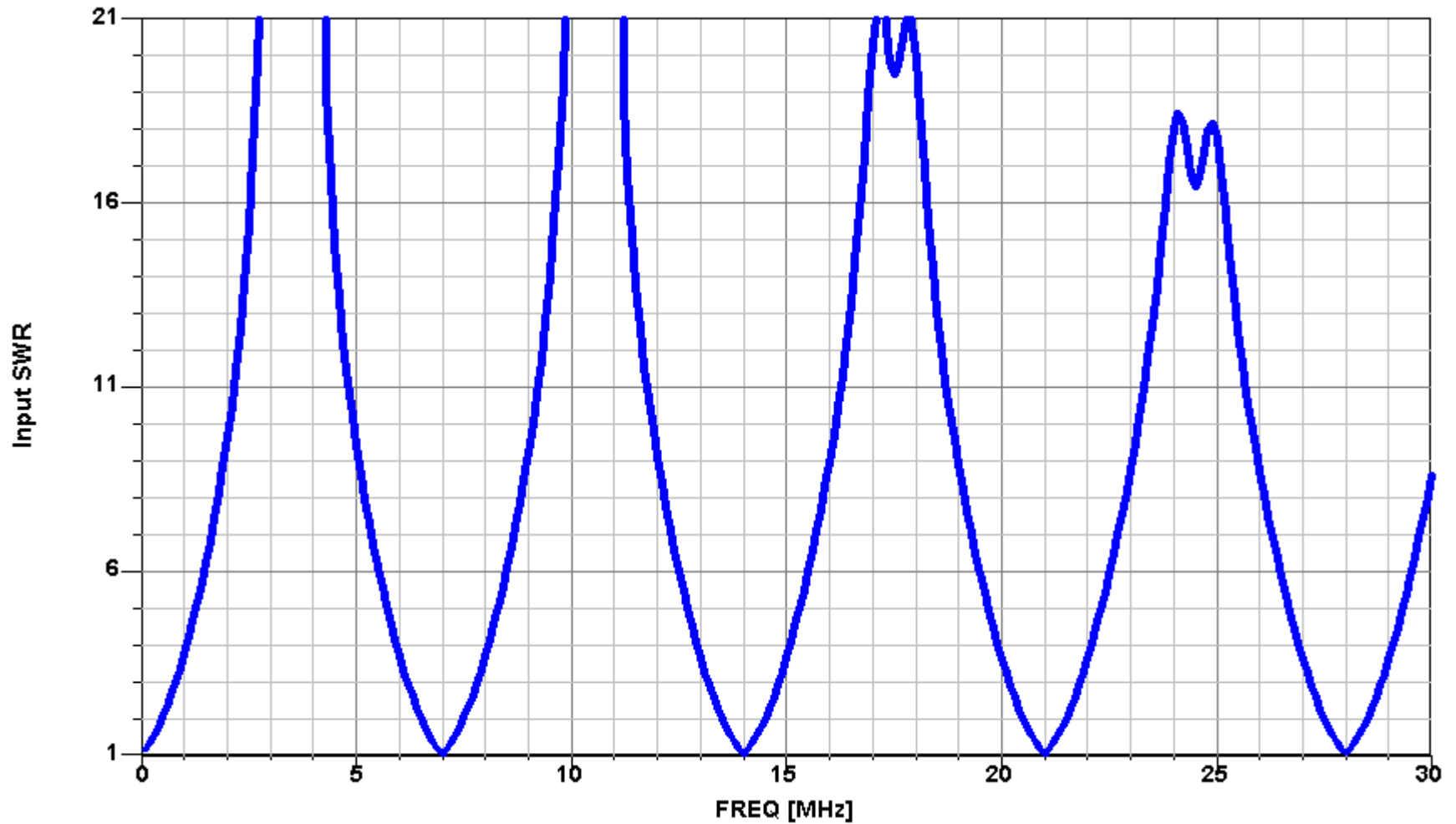


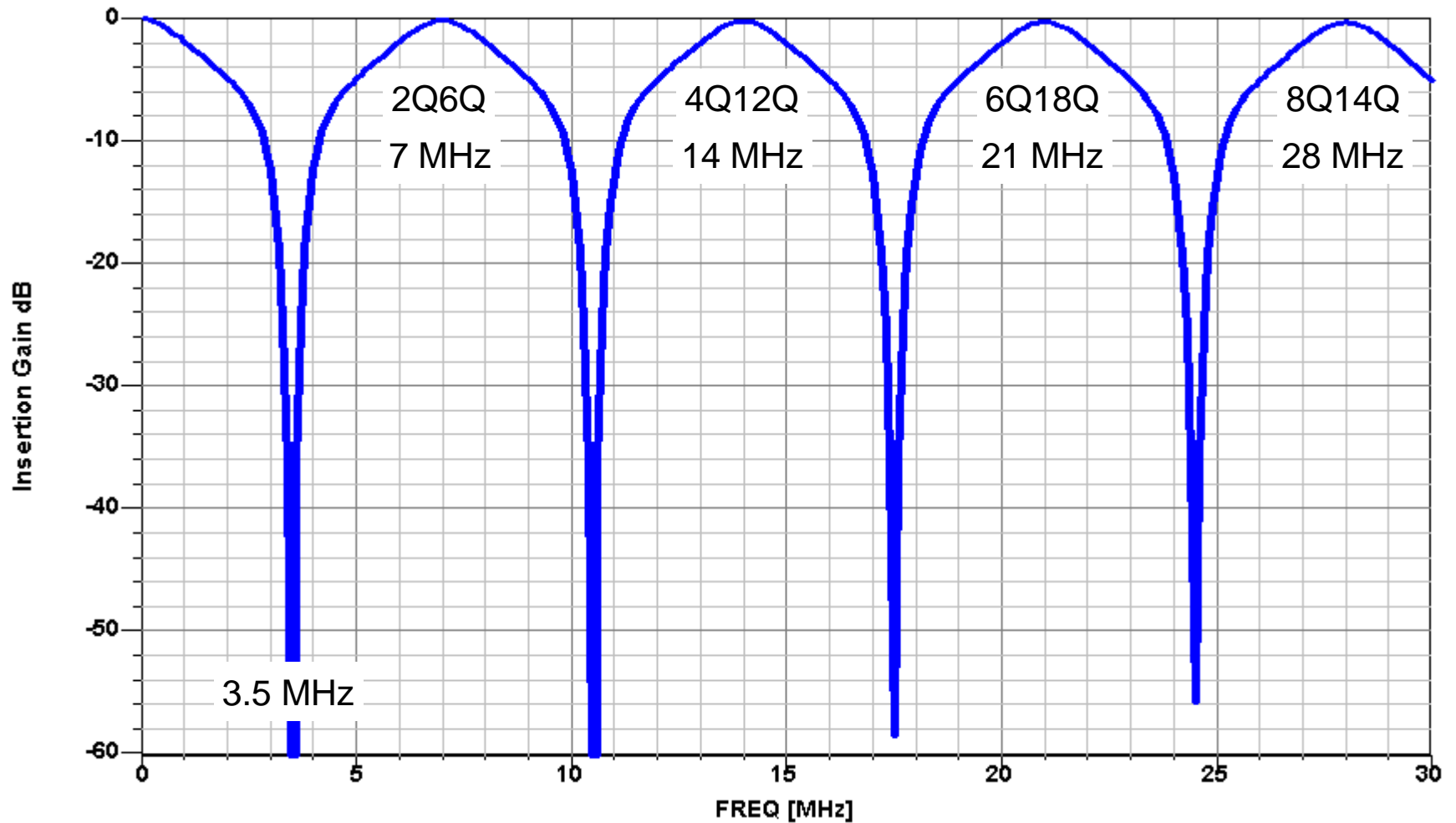Q3Q-PP Filter Insertion Gain vs Frequency




Re-Entrant Filter – Type 2

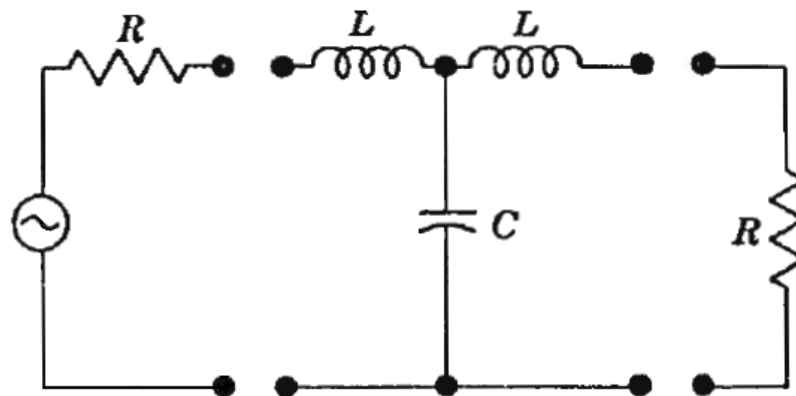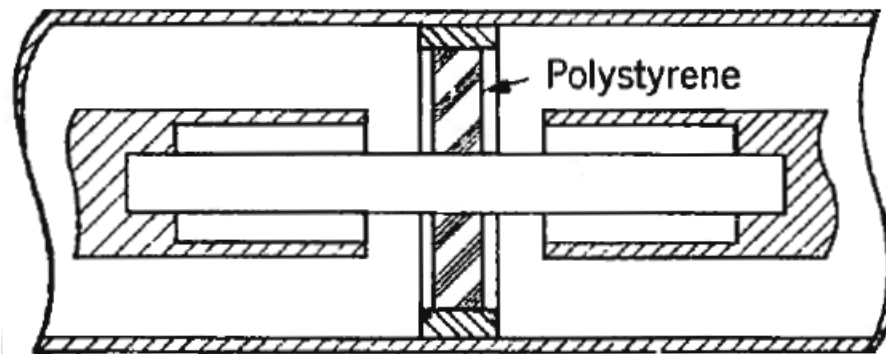- Introduced by S.B. Cohn
- Concentric, coaxial implementation of series stubs
- Example: Low-pass filter





High-Pass Filter

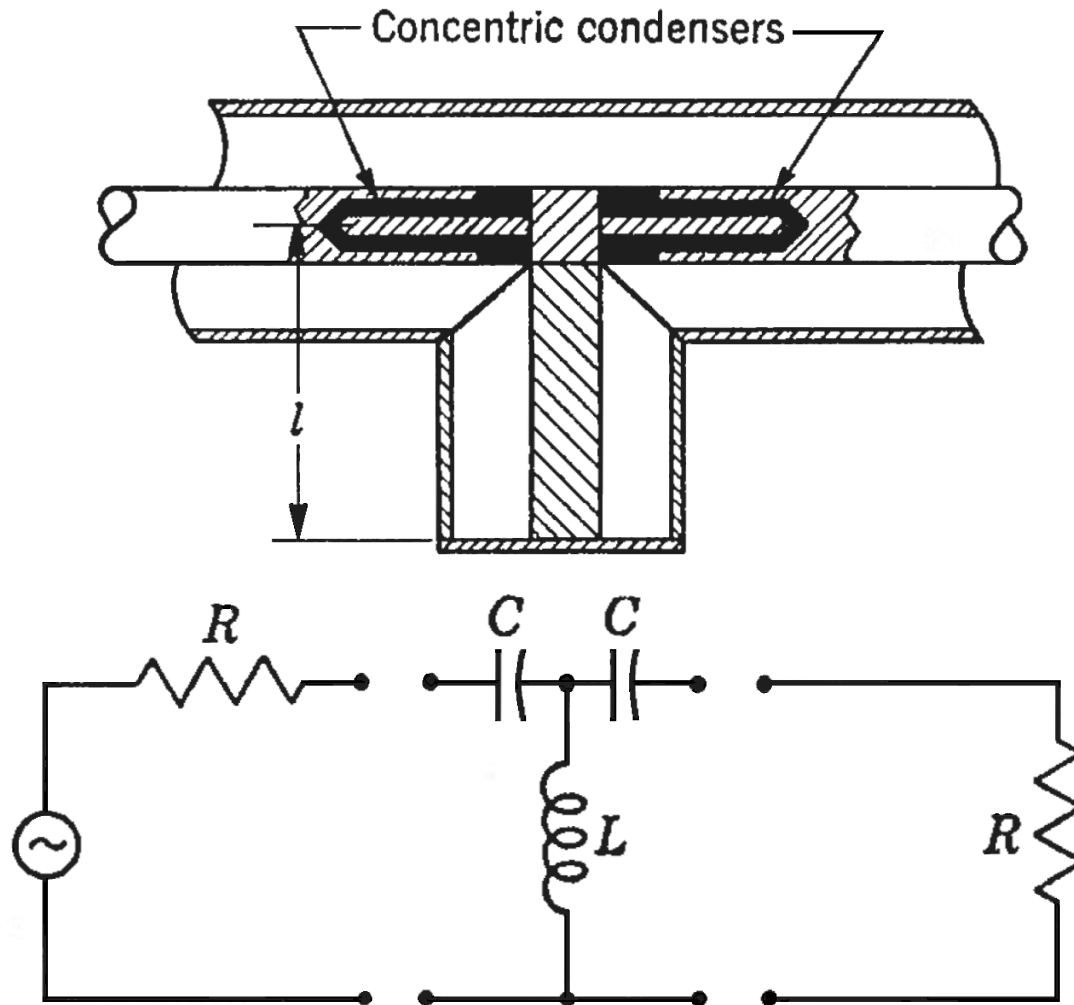


G.L. Ragan, ed., *Microwave Transmission Circuits*, McGraw-Hill, 1948

2-Stage High Pass Filter

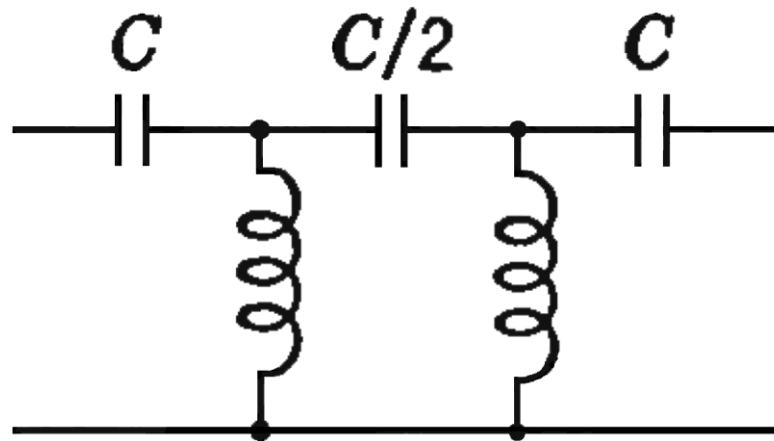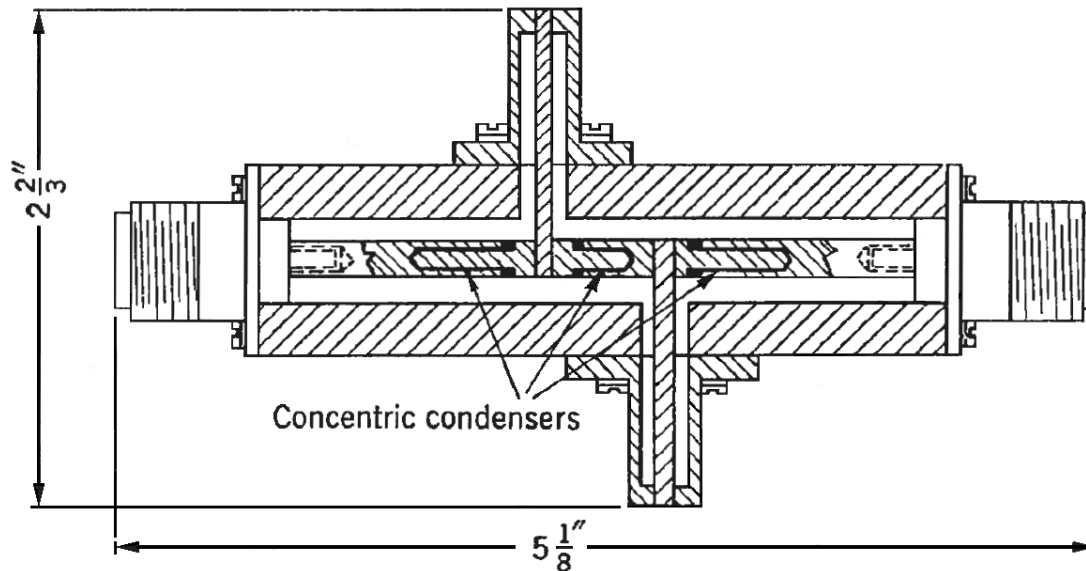


G.L. Ragan, ed., *Microwave Transmission Circuits*, McGraw-Hill, 1948

More Examples

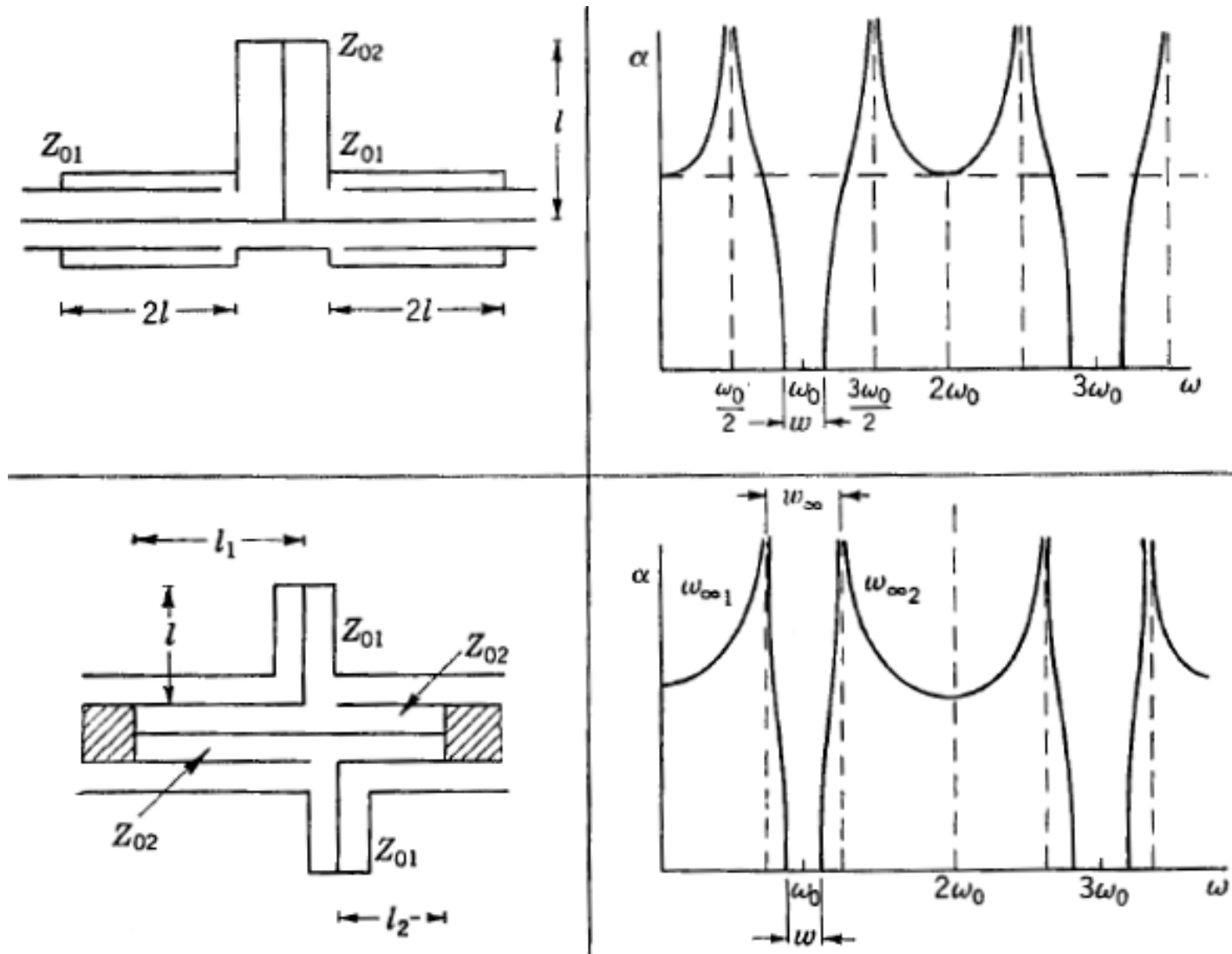

More Examples

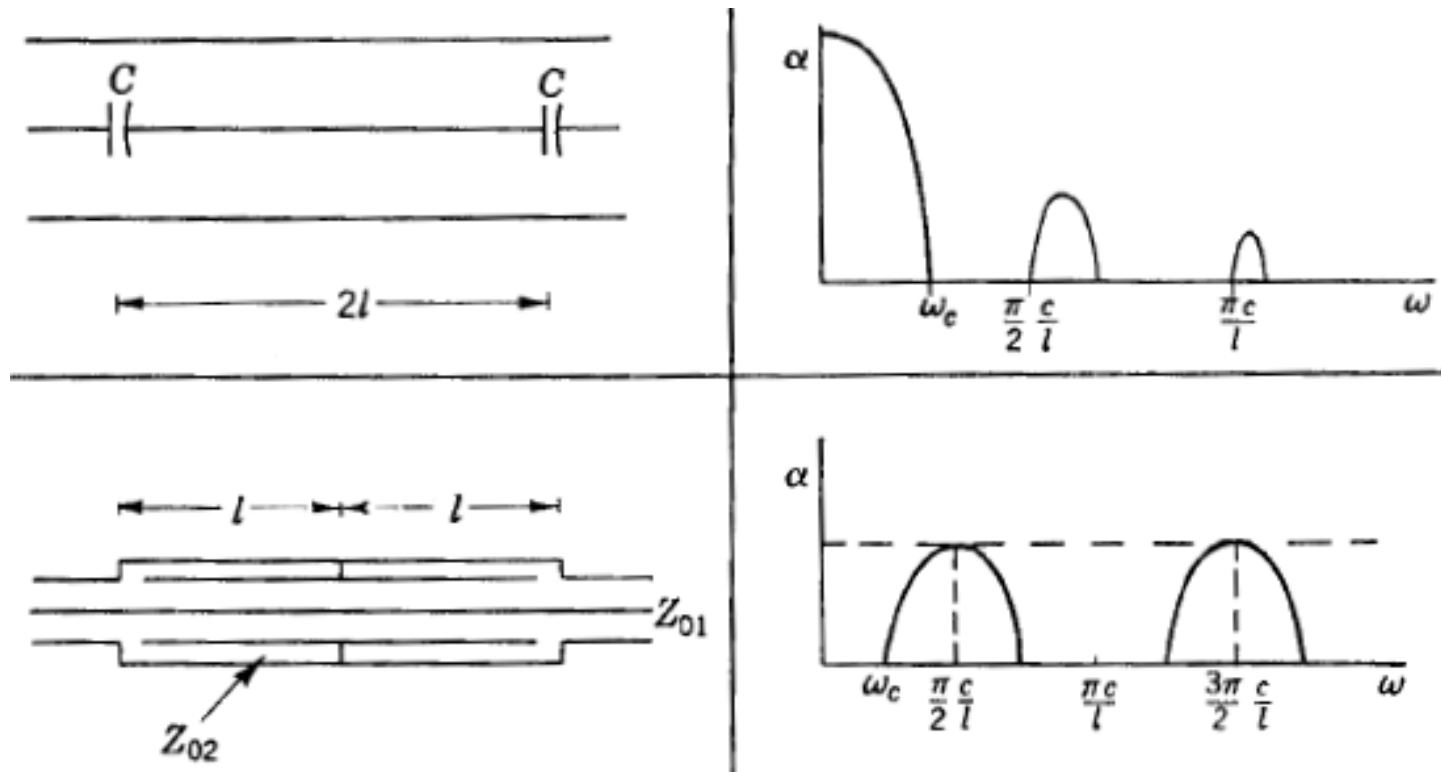

References

- W.P. Mason, *Wave Filter*, U.S. patent 1,781,469, Nov. 11, 1930
- W.P. Mason and R.A. Sykes, "The Use of Coaxial and Balanced Transmission Lines in Filters and Wide-Band Transformers for High Radio Frequencies," *Bell Syst. Tech. J.*, July 1937
- L.M. Leeds, "Concentric Narrow-Band Elimination Filter," *Proc. IRE*, May 1938
- A. Alford, "High Frequency Transmission Line Networks," *Electrical Communication (IT&T)*, Jan. 1939
- A. Alford, "Coupled Networks in Radio-Frequency Circuits," *Proc. IRE*, Feb. 1941
- H. Salinger, "A Coaxial Filter for Vestigial-Sideband Transmission in Television," *Proc. IRE*, March 1941
- P.I. Richards, *Resonant-Section Coaxial Filters*, Tech. Rept. 115, Radio Research Lab., Harvard Univ., Oct. 18, 1944
- P.I. Richards, "Applications of Matrix Algebra to Filter Theory," *Proc. IRE*, March 1946
- S.B. Cohn, "Principles of Transmission-Line Filter Design," ch. 26 and 27 in *Very High-Frequency Techniques*, Vol. II, H.J. Reich, ed., McGraw-Hill, 1947
- P.I. Richards, "Resistor-Transmission-Line Circuits," *Proc. IRE*, Feb. 1948

References continued

- A.W. Lawson and R.M. Fano, "The Design of Microwave Filters," ch. 10 in *Microwave Transmission Circuits*, G.L. Ragan, ed., MIT Rad. Lab Series vol. 9, McGraw-Hill, 1948
- D.E. Mode, "Coaxial Transmission-Line Filters," *Proc. IRE*, Dec. 1952
- H. Ozaki and J. Ishii, "Synthesis of Transmission-Line Networks and the Design of UHF Filters," *IRE Trans. Circuit Theory*, Dec. 1955
- J.M.C. Dukes, "Re-entrant Transmission Line Filter Using Printed Conductors," *Proc. IEE Pt. B*, Nov. 1957
- A.I. Grayzel, "A Synthesis Procedure for Transmission Line Networks," *IRE Trans. Circuit Theory*, Sept. 1958
- E.G. Cristal, "A Frequency Transformation for Commensurate Transmission-Line Networks," *IEEE Trans. Microw. Theory and Techniques*, June 1967
- G. Downs, W1CT, "A Cure for Intermod Alley," *QST*, March 1976
- R. Jansson, WA1QLI, "An ITV Cure for 6 Meters," *QST*, April 1976
- J.E. Fleagle, W0FY, "Traps for VHF Interference," *QST*, March 1988
- J. Regnault, G4SWX, "Stub Filters Revisited," *RadCom (RSGB)*, Nov. 1994
- H.W. Silver, N0AX, "Experiment 116: The Quarter-Three-Quarter Wave Balun," *QST*, Sept. 2012

The End

This presentation will be archived at
<http://www.fars.k6ya.org>